




# **Loop Compensation Basics Buck Converter CCM**

**More Details : AN76**



# Voltage-Mode Control


# Voltage-Mode Controlled Buck Converter

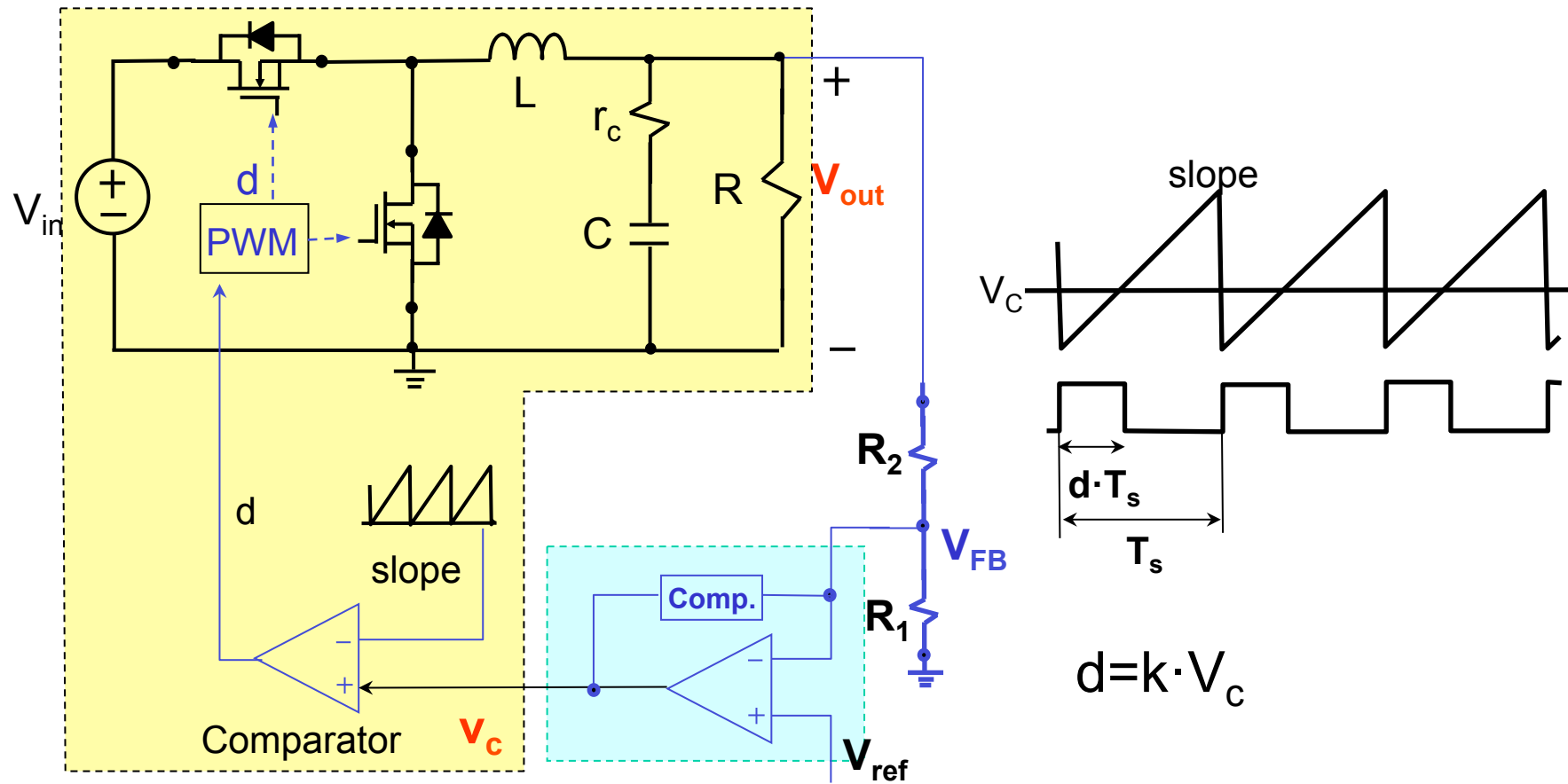

**Power Stage**  
**Control-to-output**

**Error Amp**  
**Compensation  $A(s)$**


# Control Block Diagram and Loop Gain

 

- Loop Gain:  $T(s) = G_{CV}(s) \cdot K_{REF} \cdot A(s)$
- Bandwidth: crossover frequency  $f_c$  @ loop gain  $|T(s)|=1$
- Stability: Total phase  $> -360^\circ$  at crossover frequency  

$$\text{Total Phase} = (-180^\circ + \phi[A(s)] + \phi[G_{CV}(s)])_{f=f_c} > -360^\circ$$


# Control Block Diagram and Loop Gain

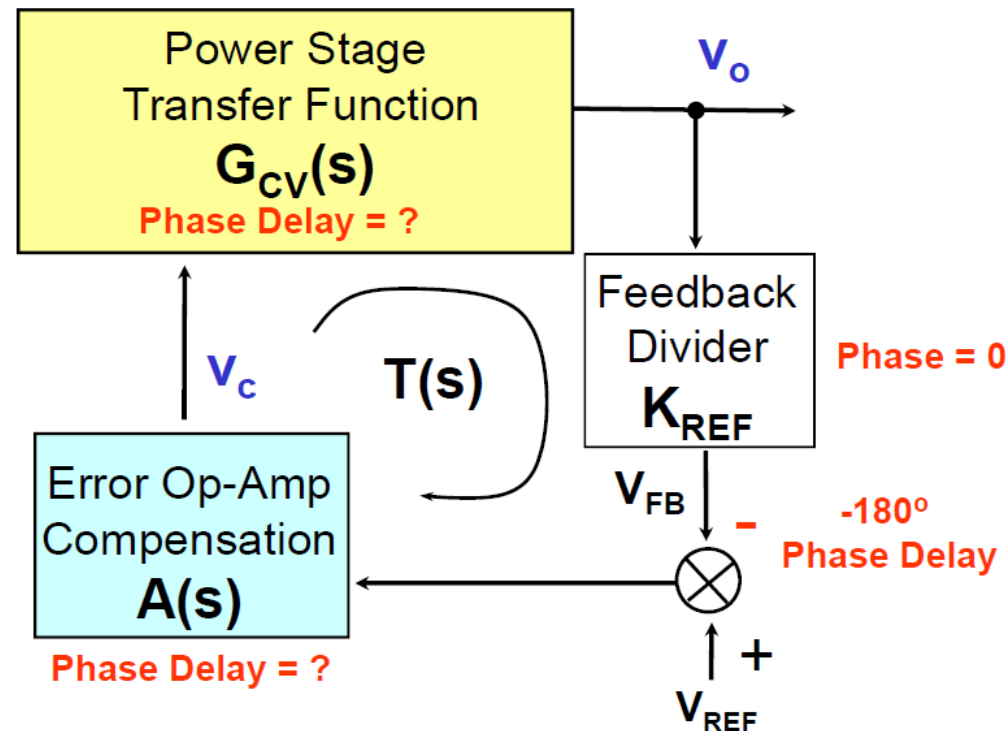

## Design Targets:

- Regulation accuracy, line rejection,  $Z_{OUT}$ :  $|T(s)| \gg 1$  for  $f < f_c$
- Bandwidth: high bandwidth for fast transient response
- Stability: phase margin  $> 45^\circ$
 
# Buck Converter Power Stage Control-to-Output



Control-to-output transfer function:

$$G_{dv}(s) = \frac{\hat{v}_o}{\hat{d}} = \frac{V_{in} \cdot \left(1 + \frac{s}{\omega_{z\_ESR}}\right)}{1 + \frac{s}{\omega_{o\_p} \cdot Q} + \frac{s^2}{\omega_{o\_p}^2}}$$

ESR Zero:


$$f_{z\_ESR} = \frac{1}{2\pi} \cdot \frac{1}{r_c \cdot C}$$

Resonant double poles:

$$f_{o\_p} \approx \frac{1}{2\pi} \cdot \frac{1}{\sqrt{L \cdot C}}$$

**- 1 zero, 2 poles system.**
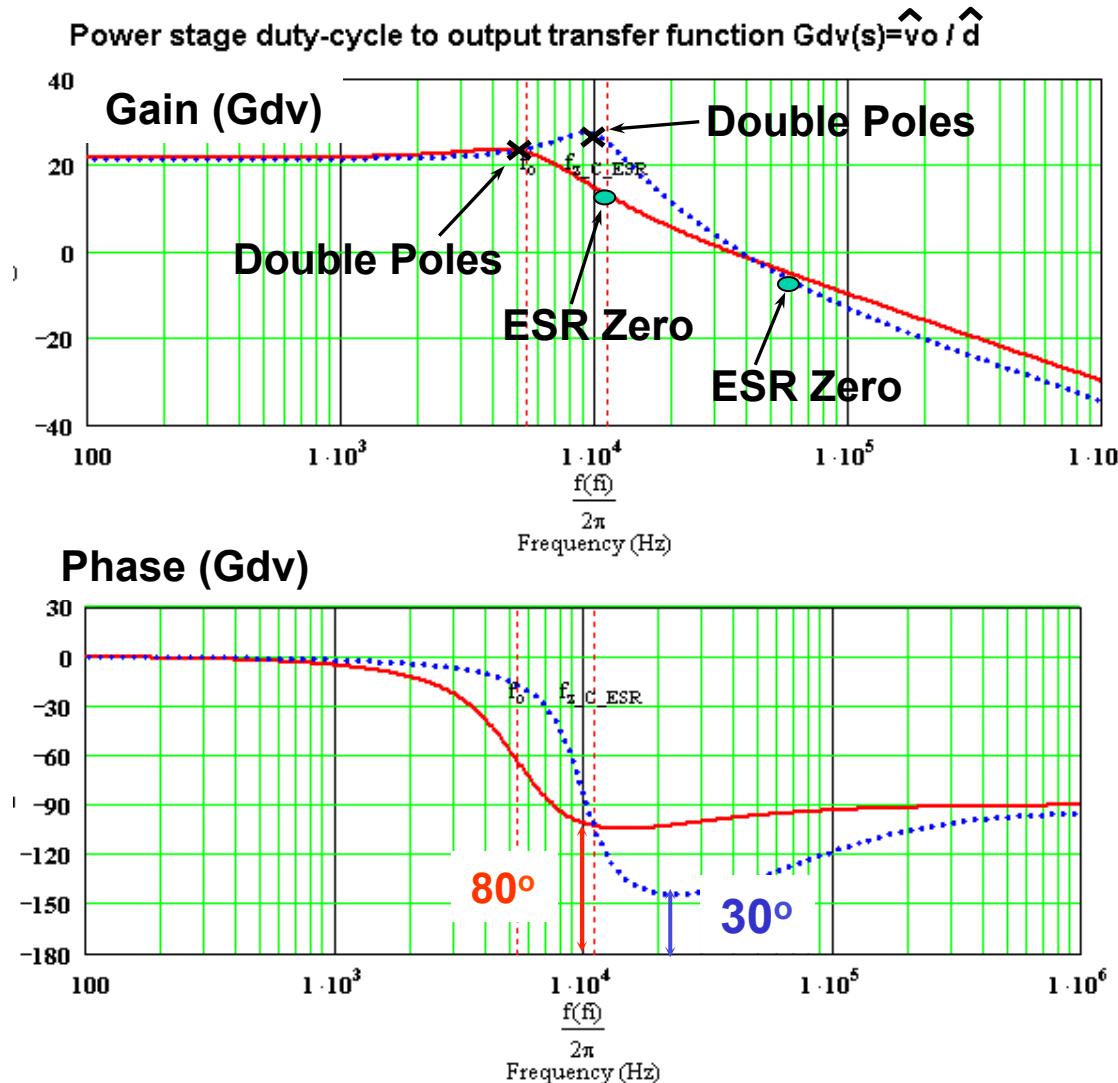
# Power Stage Transfer Function With Voltage Mode Control



- 1 — Reference design  
3X470uF Kemet Tantalum cap.  
 $r_C = 30\text{m}\Omega$
- 2 ..... Customer design  
2 X 220uF Panasonic SP cap.  
 $r_C = 12\text{m}\Omega$

**Double Poles:  $-180^\circ$**   
**ESR Zero:  $+90^\circ$**

**Phase delay is a strong function of output capacitor ESR**

# **Loop Compensation Design Of Voltage Mode Control**



# Voltage Loop Compensation Design

## 1. Select desired crossover frequency $f_c$


$$f_c(\text{min}) > 3 \cdot f_{0\_p}(LC) \quad f_c(\text{max}) < \frac{f_{SW}}{5}$$

## 2. Loop compensation – type 3 compensation network

- 1 pole, low frequency integrator for high DC gain
- 2 zeros located around L-C resonant double poles
- 2 high-frequency poles:
  - to attenuate high frequency noise
  - to ensure the magnitude of the loop gain keeps decreasing after the 0dB crossover
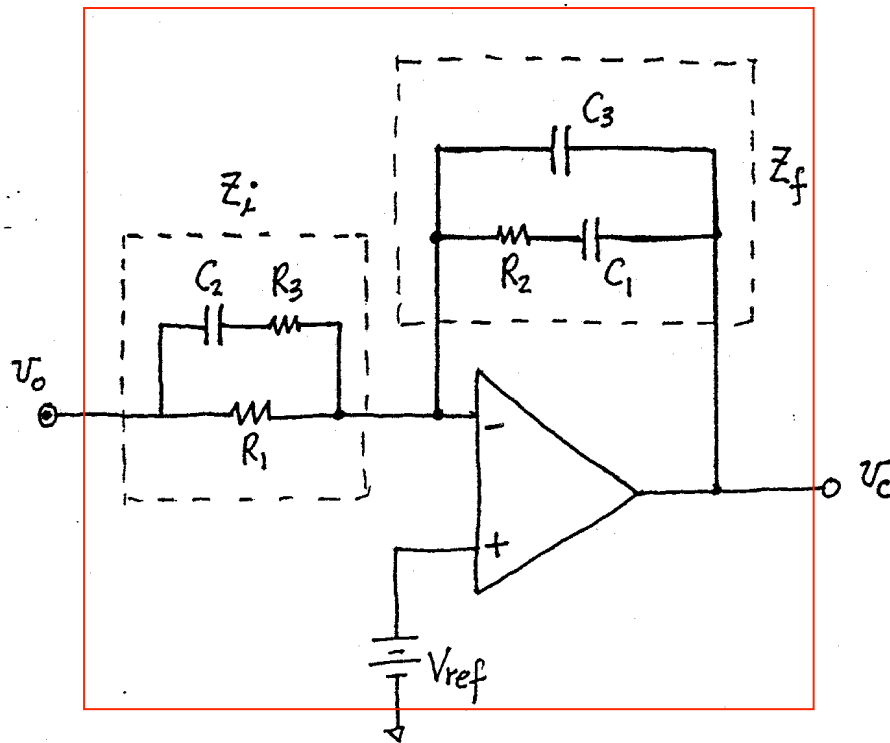
# Type 3 Compensation Network

(Typical 3-Pole, 2-Zero system in Voltage Mode Control)



$$\frac{\hat{v}_c}{\hat{v}_o} = -\frac{Z_f}{Z_i}$$

$$Z_i = R_1 // \left( \frac{1}{sC_2} + R_3 \right)$$

$$Z_f = \frac{1}{sC_3} // \left( \frac{1}{sC_1} + R_2 \right)$$

$$\frac{\hat{v}_c}{\hat{v}_o} = -\frac{\omega_I (1 + s/\omega_{Z1})(1 + s/\omega_{Z2})}{s (1 + s/\omega_{P1})(1 + s/\omega_{P2})}$$

where:

$$\omega_{Z1} = \frac{1}{R_2 C_1}, \quad \omega_{Z2} = \frac{1}{(R_1 + R_3) C_2} \sim \frac{1}{R_1 C_2} \quad R_1 \gg R_3 \quad C_1 \gg C_3$$

$$\omega_I = \frac{1}{R_1 (C_1 + C_3)} \sim \frac{1}{R_1 C_1} \quad \omega_{P1} = \frac{1}{R_3 C_2}, \quad \omega_{P2} = \frac{1}{R_2 \cdot \frac{C_1 C_3}{C_1 + C_3}} \sim \frac{1}{R_2 C_3}$$

## Type 3 Compensation Network

(Typical 3-Pole, 2-Zero system in Voltage Mode Control)

$$\frac{\hat{v}_c}{\hat{v}_o} = - \frac{\omega_I}{s} \frac{(1 + s/\omega_{z1})(1 + s/\omega_{z2})}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

### Quick recommendations :

- $f_{p1} = f_{z\_ESR}$
- $f_{p2} \sim f_c$  to  $10 \times f_c$
- $f_{z1} = f_{z2} = f_{0\_LC}$
- $f_l$  to get desired crossover frequency  $f_c$

# Pros and Cons of Voltage Mode Regulators

## ◆ Pros:


- ◆ Don't need dedicated current sensing R : high efficiency and low cost solution

## ◆ Cons:


- ◆ Loop gain is a function of  $V_{in}$ 
  - ◆ Solution:  $V_{in}$  feed-forward compensation
- ◆ Loop gain is a function of output ESR
  - ◆ Need carefully loop compensation design
- ◆ **Need to compensate for double resonant pole**
- ◆ The current sensing / limit is slow and not accurate
- ◆ Need external loop for current sharing if two supplies / phases are in parallel

# Current Mode Control

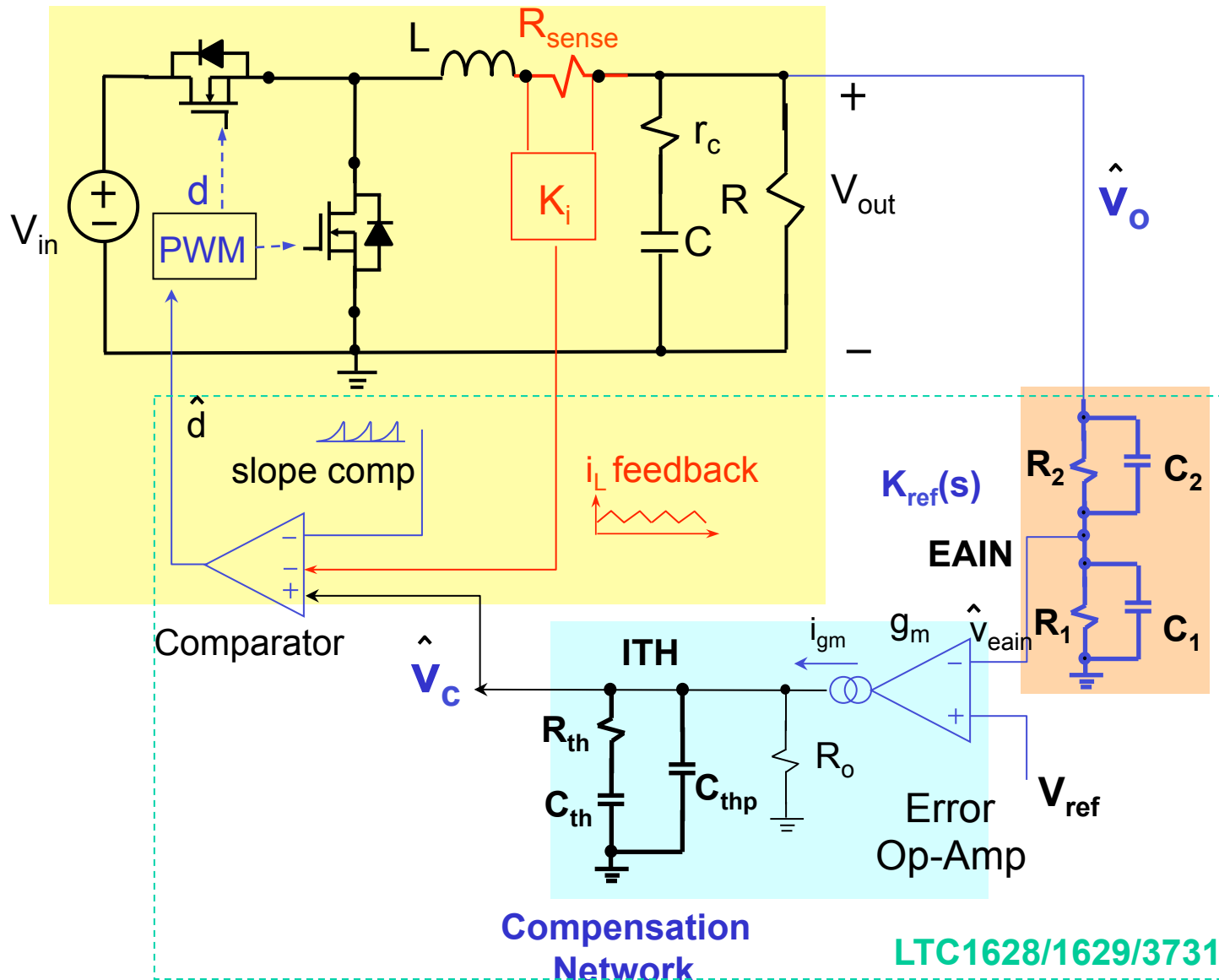
# Simplified Block Diagram of Current Mode IC



# Peak Current Mode Control

 

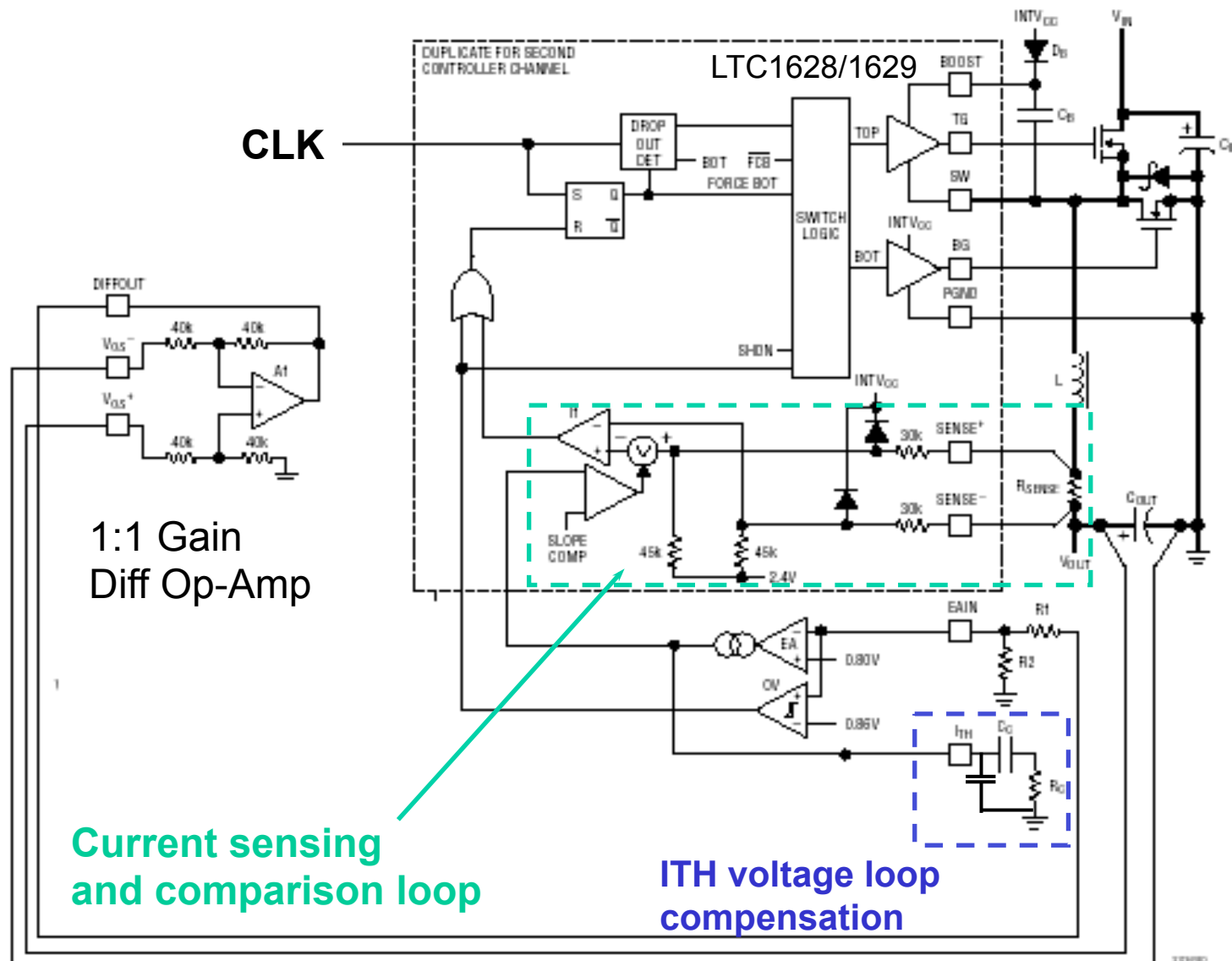
# LTC's Current-Mode Controller Block Diagram





 
# Power Stage Transfer Function With Current Mode Control

Gain (dB) power stage  $G_{cv}(s)$  with current-mode-control:




- 1 — Reference design  
3X470uF Kemet cap.  
 $r_c=30m\Omega$
- 2 ..... Customer design  
2 X 220uF Panasonic cap.  
 $r_c=12m\Omega$

Phase (deg)

 

- Reduce phase delay with different output capacitors
- Stable system with reduced output capacitors / cost.
 
# Buck Converter Power Stage Control-to-Output



Simple small-signal model :  
current source feeding the load

Slope comp to avoid subharmonic  
oscillation not modeled

**Control-to-output transfer function:**

$$G_{cv}(s) = \frac{\hat{v}_o}{\hat{v}_c} = K \frac{(1 + \frac{s}{\omega_z})}{(1 + \frac{s}{\omega_p})}$$

$$f_z = \frac{1}{2\pi} \cdot \frac{1}{R_C \cdot C}$$

$$f_p = \frac{1}{2\pi} \cdot \frac{1}{R \cdot C}$$

**- 1 zero, 1 pole system.**

# Pros and Cons of Current Mode Control

## ◆ Pros:

- ◆ **Accurate / fast cycle-by-cycle current limit**
- ◆ **True soft-start of inductor current**
- ◆ **Easy to parallel phases / converters for high current**
- ◆ **Accurate / fast current sharing**
- ◆ **Very good line ripple rejection**
- ◆ **Simple loop compensation with wide range of COUT, including Ceramic**
- ◆ **High reliability**

## ◆ Cons:

- ◆ **Need current sensing Rsense or RDSON or DCR, noise immunity**
- ◆ **Subharmonic instability (ramp compensation needed)**
- ◆ **Duty cycle limitation ( $t_{ON}$ ,  $t_{OFF}$ ) due to current sensing delay**
- ◆ **Higher output impedance at low frequency**

# **Loop Compensation Design Of Current Mode Control**

# Voltage Loop Compensation Design

1. Select desired cross over frequency  $f_c$


$$f_{C(\max)} < \frac{f_{SW}}{5}$$

2. Choose desired loop phase margin:

Phase margin  $> 45^\circ$  for buck converter



3. Choose optimum values of the resistor divider network  $K_{REF}(s)$  and  $I_{TH}$  compensation network  $A(s)$
 
# Feedback Voltage Divider and Phase Boost




$$K_{REF}(s) = \frac{v_{EAIN}(s)}{v_o(s)} = K_{REF} \cdot \frac{1 + \frac{s}{2\pi \cdot f_{z\_ref}}}{1 + \frac{s}{2\pi \cdot f_{p\_ref}}}$$
  
$$f_{z\_ref} = \frac{1}{2\pi \cdot R_2 \cdot C_2} \quad f_{p\_ref} = \frac{1}{K_{REF}} \cdot \frac{1}{2\pi \cdot R_2 \cdot (C_1 + C_2)}$$



**$C_1$  and  $C_2$  provide phase boost around the crossover frequency.**


# $I_{TH}$ Compensation – High DC Gain

 

$$A(s) = \frac{v_{ITH}(s)}{v_{EAIN}(s)} = -g_m \cdot (Z_{ith}(s))$$

 
## 1. Simple Integrator:

$$A(s) = -g_m \cdot \frac{1}{C_{th} \cdot s}$$



- High low frequency gain for accurate DC  $V_{out}$  regulation
- -90° phase delay @ expected cross-over frequency  $f_c$

# $I_{TH}$ Compensation – LF Pole

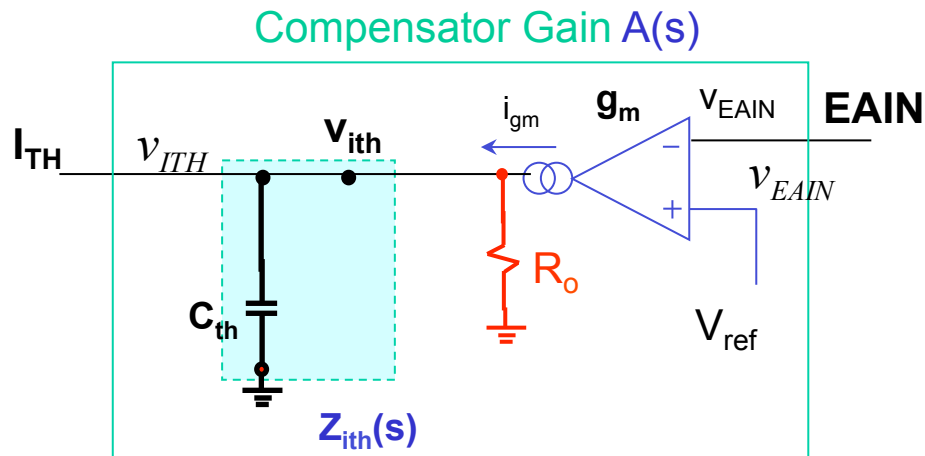


$$A(s) = \frac{v_{ITH}(s)}{v_{EAIN}(s)} = -g_m \cdot (Z_{ith}(s))$$
 
## 2. Simple Integrator with $g_m$ Op-Amp Output Impedance $R_o$ :


$$A(s) = -g_m \cdot R_o \cdot \frac{1}{(1 + \frac{s}{s_{po}})} \quad s_{po} = \frac{1}{R_o \cdot C_{th}}$$

- $g_m$  Op-Amp adds a low frequency pole
- Still  $-90^\circ$  phase delay @  $f_c$




 
# $I_{TH}$ Compensation – Add Zero for Phase




3. Add zero for Phase Compensation at cross over frequency:

$$A(s) = -g_m \cdot R_o \cdot \frac{1 + \frac{s}{s_{thz}}}{\left(1 + \frac{s}{s_{po}}\right)}$$


$$s_{thz} = \frac{1}{R_{th} \cdot C_{th}}$$

 - Adds a zero before / around  $f_c$  to boost up phase
- Increased gain @ high frequency



# $I_{TH}$ Compensation – HF Pole


Compensator Gain  $A(s)$

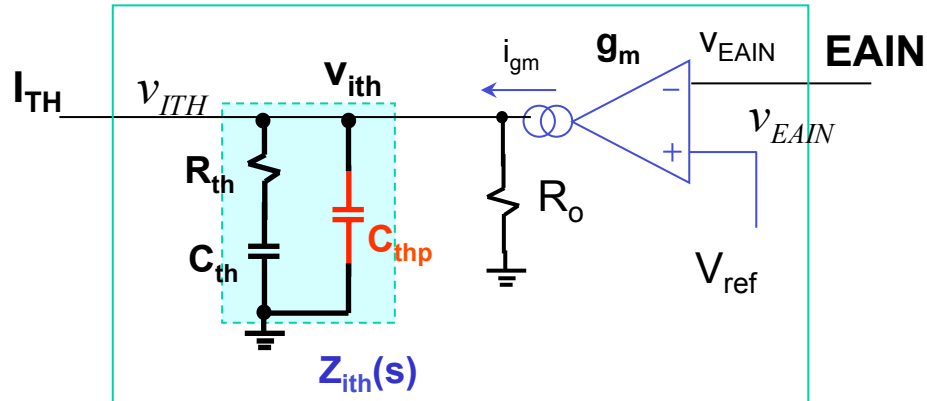

 4. Add a high frequency pole to attenuate high frequency noise:

$$A(s) = -g_m \cdot R_o \cdot \frac{1 + \frac{s}{s_{thz}}}{\left(1 + \frac{s}{s_{po}}\right) \cdot \left(1 + \frac{s}{s_{thp}}\right)}$$


$$s_{thp} = \frac{1}{R_{th} \cdot \frac{C_{th} \cdot C_{thp}}{C_{th} + C_{thp}}} \approx \frac{1}{R_{th} \cdot C_{thp}} \quad (C_{th} \gg C_{thp})$$


 
# How much phase margin is necessary?


For a second-order system (good approximation near  $f_c$ )

Closed-loop peaking factor  $Q$  vs.  
loop-gain phase margin  $\phi_m$



$Q < 0.5$  over-damping  
 $Q = 0.5$  critical damping  
 $Q > 0.5$  under-damping

 Unit-step response for various  
values of  $Q$



No overshoot  $\Rightarrow Q \leq 0.5 \Rightarrow \phi_m \geq 76^\circ$

# How much phase margin is necessary?

Changes in line, load and temperature tend to degrade phase margin from the nominal value.

For commercial equipment, where the temperature variations are mild, a nominal phase margin of  $60^\circ$  is usually enough to accommodate manufacturing tolerances.

If external factors such as use of remote sensing or variable amounts of filter capacitance can affect phase margin then more than  $60^\circ$  of nominal phase margin may be desirable.

Military designs with their wide temperature swings should start with a higher nominal value, such as  $75^\circ$ , to try to maintain  $20\text{-}30^\circ$  of phase margin in the worst case.

The penalty for high phase margin is reduced gain at low frequency (reducing the line-frequency ripple rejection) and slower transient response time.

The optimum choice of phase margin and bandwidth is determined by the application.

The important thing is to measure the bandwidth and margins rather than estimate them or ignore them.

*(Source : VENABLE technical paper # 2)*

# How to choose crossover frequency $f_c$ ?

In closed loop,  $|Z_{OUT}| \sim |Z(C_{OUT})|_{f=f_c}$  :  $\Delta V_{OUT} \sim \frac{\Delta I_{OUT}}{2 \cdot \pi \cdot f_c \cdot C_{OUT}}$

Valid only for :  $ESR(C_{OUT}) < \frac{1}{2 \cdot \pi \cdot f_c \cdot C_{OUT}}$


$\Delta I_{OUT}$  : output load step

$\Delta V_{OUT}$  : output voltage undershoot

# Compensators type 1, 2, 3


Type 1:

- DC pole only (integrator)
- No phase boost
- Used for power stage with small phase shift

 


Type 2:

- DC pole + 1 pole + 1 zero
- Phase boost  $< 90^\circ$  ( $< 75^\circ$  in practice)
- Used for CCM current-mode and voltage-mode converters in DCM

 

Type 3:

 - DC pole + 2 pole + 2 zero
- Phase boost  $< 180^\circ$  ( $< 160^\circ$  in practice)
- Used for CCM voltage-mode buck or boost-derived types of converters




# How to define compensation network

## Simulation :

- Use LTspice to generate Bode plot
- Check:
  - crossover frequency ( $f_c$ )
  - phase margin ( $\phi_m$ )
- Adjust compensation values manually or use Venable K-Factor method

# Extract from datasheet

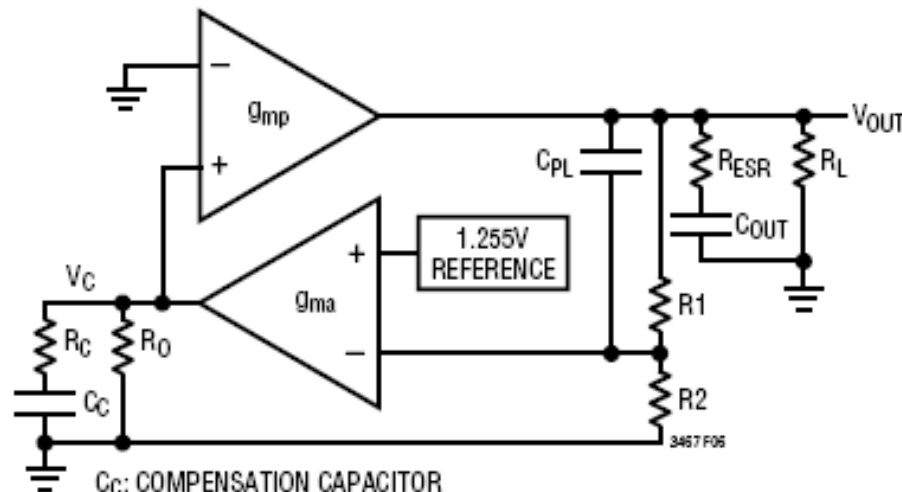


$C_C$ : COMPENSATION CAPACITOR  
 $C_{OUT}$ : OUTPUT CAPACITOR  
 $C_{PL}$ : PHASE LEAD CAPACITOR  
 $g_{ma}$ : TRANSCONDUCTANCE AMPLIFIER INSIDE IC  
 $g_{mp}$ : POWER STAGE TRANSCONDUCTANCE AMPLIFIER  
 $R_C$ : COMPENSATION RESISTOR  
 $R_L$ : OUTPUT RESISTANCE DEFINED AS  $V_{OUT}$  DIVIDED BY  $I_{LOAD(MAX)}$   
 $R_O$ : OUTPUT RESISTANCE OF  $g_{ma}$   
 $R_1, R_2$ : FEEDBACK RESISTOR DIVIDER NETWORK  
 $R_{ESR}$ : OUTPUT CAPACITOR ESR

Parameter	Value	Units
$R_L$	10.4	$\Omega$
$C_{OUT}$	15	$\mu F$
$R_{ESR}$	10	m $\Omega$
$R_O$	0.4	M $\Omega$
$C_C$	60	pF
$C_{PL}$	3.3	pF
$R_C$	100	k $\Omega$
$R_1$	402	k $\Omega$
$R_2$	133	k $\Omega$
$V_{OUT}$	5	V
$V_{IN}$	3.3	V
$g_{ma}$	35	$\mu mho$
$g_{mp}$	7.5	mho
$L$	2.7	$\mu H$
$f_S$	1.3*	MHz




# LTspice to generate Bode plot


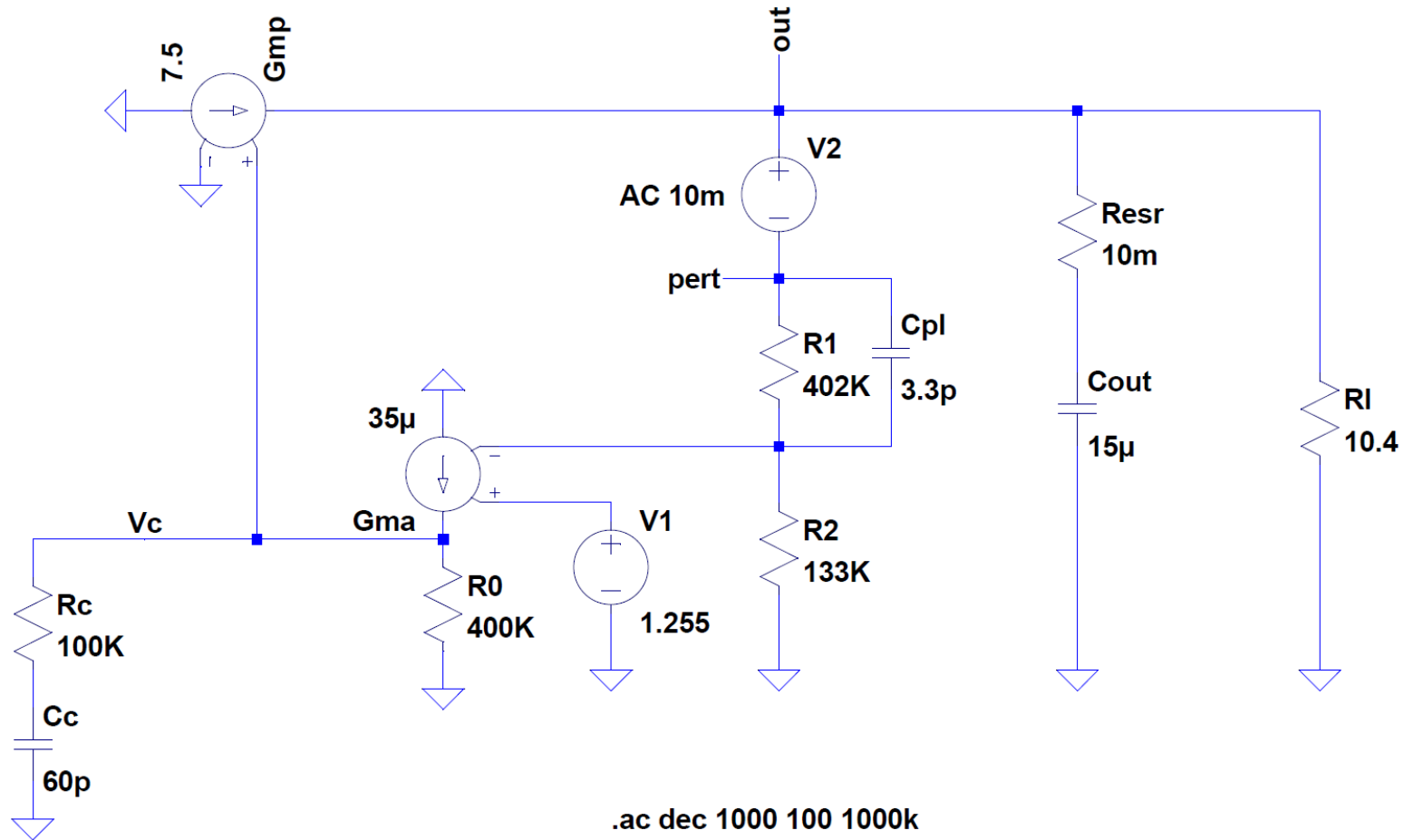


# LTspice to generate Bode plot

$V(\text{out}) / V(\text{pert})$

 


# Input Filter & Cascaded DC/DC

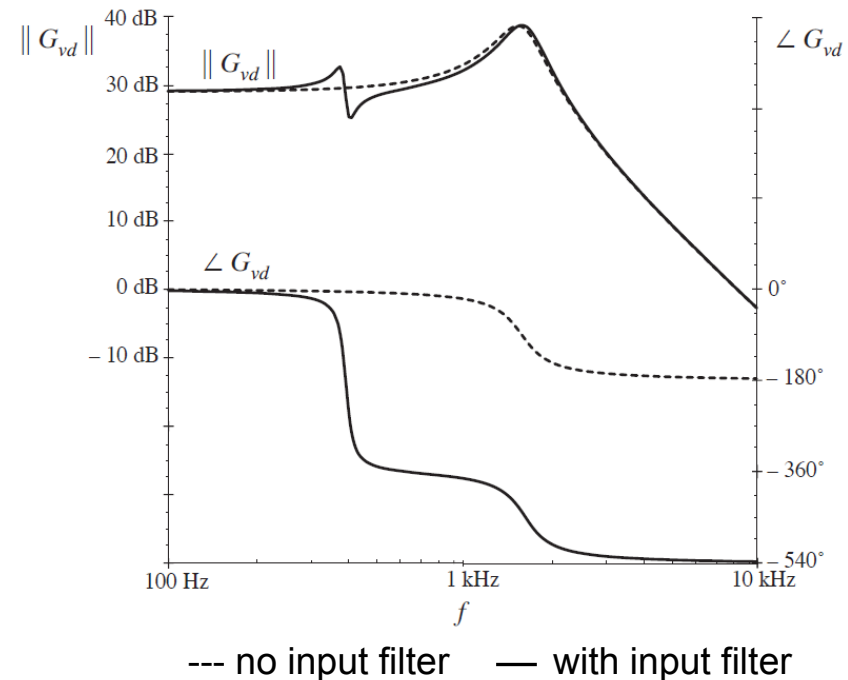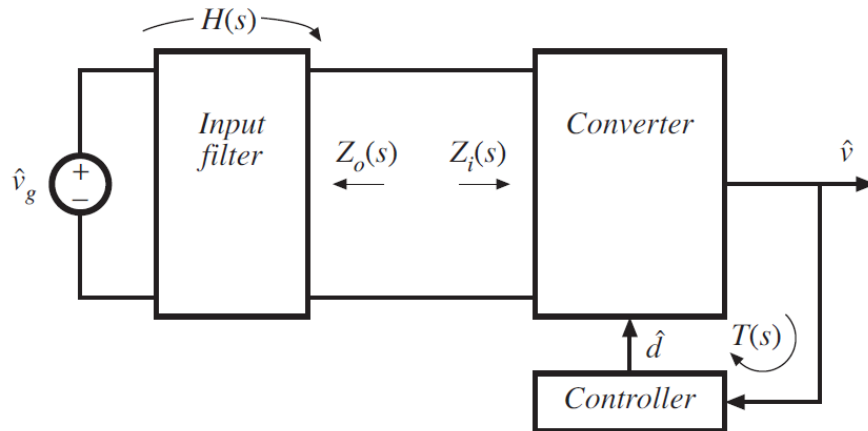

- Filter can seriously degrade converter control system behavior
- Check that converter dynamics is not affected by input filter
- Not affected if  $|Z_o(s)| < |Z_i(s)|$  at all frequencies
- Also check stability of cascaded DC/DC
- 2 stable converters can make an unstable system when cascaded


# Practical Tests

# Measure the Voltage Loop Gain

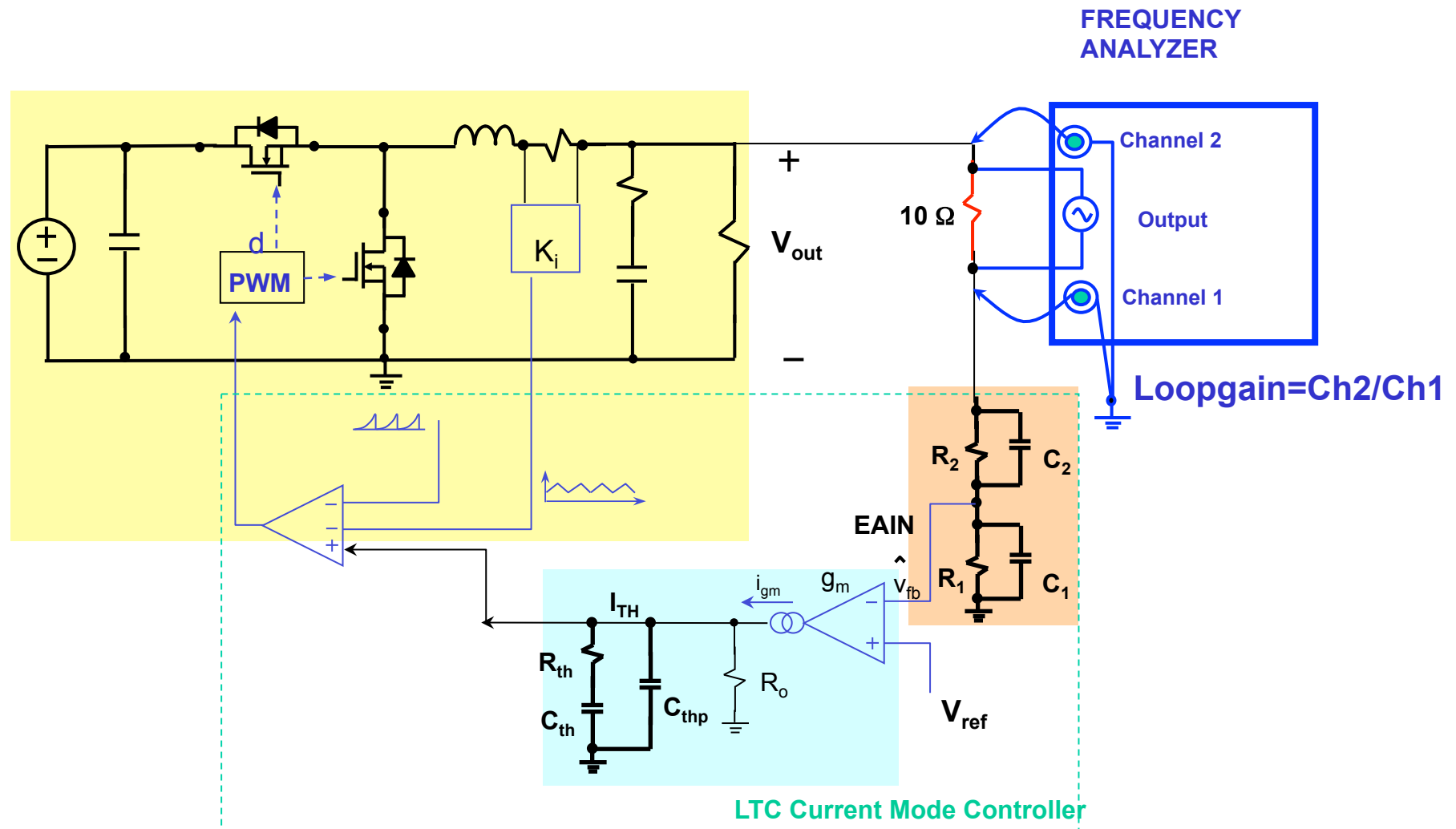


# Typical Loop Gain and Phase Margin

## LTC3729 Current Mode Buck Converter

 
 
# Frequency Analyser - Bode 100 by Omicron Lab



1Hz to 40MHz frequency range