



# A Tutorial Introduction to Switching Converters

---

Christophe Basso

Business Development Manager

IEEE Senior Member


# Agenda

---

- Power Conversion Mechanisms
- Switching Cells and Control Schemes
- The Buck
- The Boost
- The Buck-Boost
- Introduction to Control Loop Design
- EMI Filter Interaction
- Introduction to Simulation
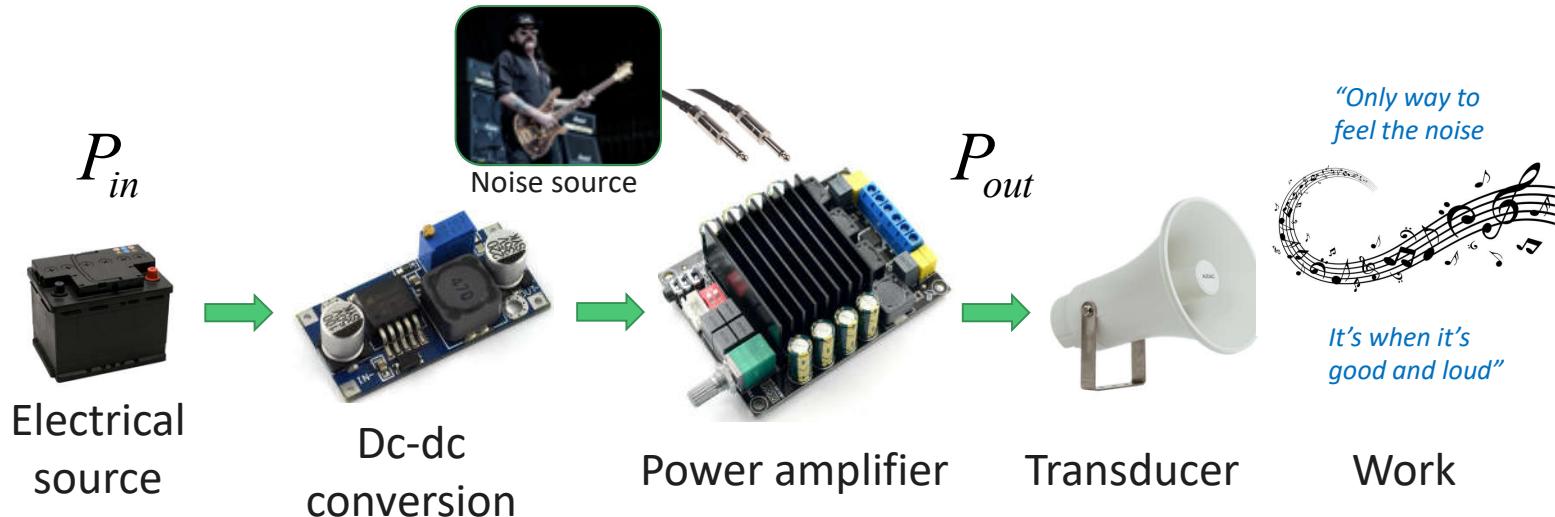
# The Goal of a Converter is to Deliver Power

- A converter transforms the energy from a source into a physical work
- The conversion mechanism generates losses and heat which must be evacuated



- ✓ Energy efficiency is about minimizing the losses in the conversion chain
- ✓ A highly-efficient converter implies lower-size heatsink and improved reliability

# No Loss in a Perfect World

- In an ideal system, all the energy coming from the source converts into work
- The ratio between the delivered power and the input power is efficiency
- ✓ The Greek letter “eta” designates a unitless number less than 1 or 100%

$$\eta = \frac{P_{out}}{P_{in}}$$


$$P_{loss} = P_{in} - P_{out} = \frac{P_{out}}{\eta} - P_{out} = P_{out} \left( \frac{1}{\eta} - 1 \right)$$

A 50% efficiency means  $P_{loss} = P_{out}$



e.g.  $P_{out} = 100 \text{ W} \rightarrow P_{loss} = 100 \text{ W}$

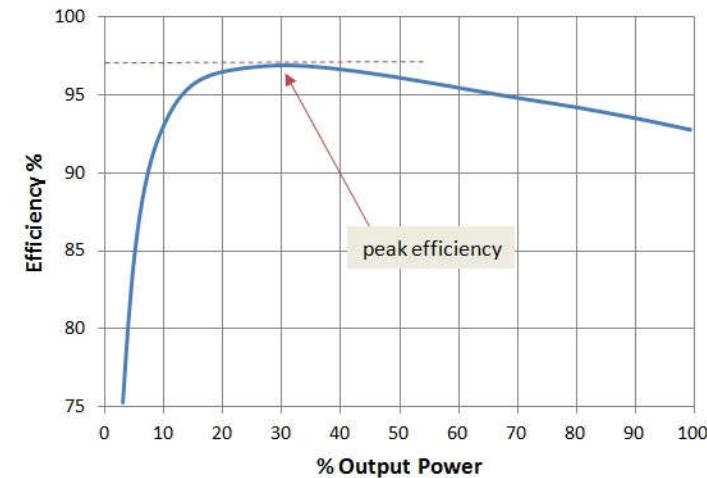$P_{in} = 150 \text{ W}, P_{out} = 100 \text{ W} \rightarrow \eta = 66\%$



- ✓ Efficiency is not constant and often peaks at a level different than nominal power
- ✓ Challenge is to keep losses low across a wide load range

# Efficiency Across the Load Range



- Computers are rarely used at their full power capability
- Depending on the active program, computational burden affects consumption
- The 80+ standard established in 2004 defines efficiency at different load conditions



80 PLUS Test Type	115 V Internal Non-Redundant			230 V Internal Redundant			
	20 %	50 %	100 %	10 %	20 %	50 %	100 %
80 PLUS	80 %	80 %	80 %	Not defined			
80 PLUS Bronze	82 %	85 %	82 %	---	81 %	85 %	81 %
80 PLUS Silver	85 %	88 %	85 %	---	85 %	89 %	85 %
80 PLUS Gold	87 %	90 %	87 %	---	88 %	92 %	88 %
80 PLUS Platinum	90 %	92 %	89 %	---	90 %	94 %	91 %
80 PLUS Titanium	Inexistant			90 %	94 %	96 %	91 %

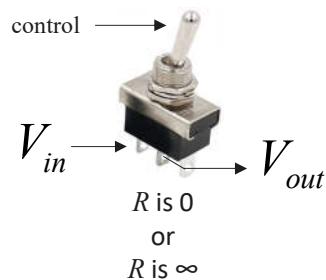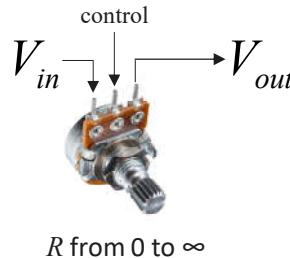
# Performing Power Conversion

- Power conversion can be done in two ways, linear or switched
- The linear approach relies on a controlled resistance to regulate the flow
- The switching approach uses a power switch either open or closed



The **linear** approach:


- efficiency is poor
- good noise performance
- acceptable when  $(V_{out} - V_{in})$  is small
- can only decrease the input level

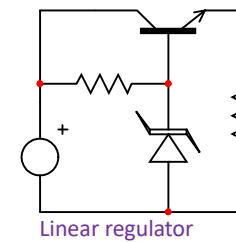

MC7805

The **switching** approach:



- efficiency is high
- noise performance is poor
- works with large  $(V_{out} - V_{in})$
- increase/decrease/invert the input level
- requires energy-storing elements

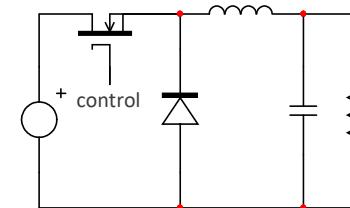

MC34063
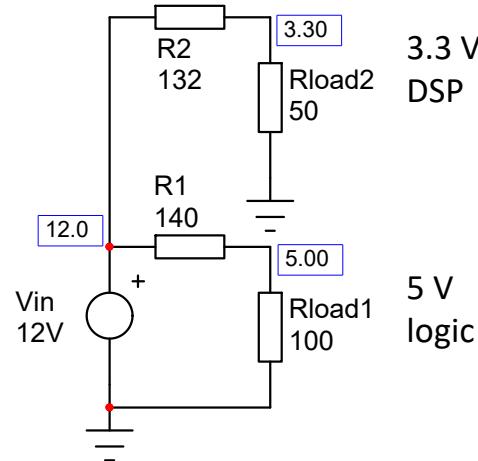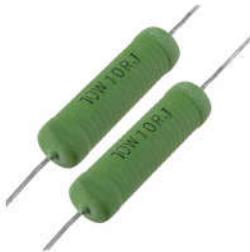
# Associating Resistors to Lower the Voltage

- Associating resistors together is a way to reduce the voltage
- It is however difficult to keep a stable value when operating conditions change



$$P_{out} = \frac{5^2}{100} + \frac{3.3^2}{50} = 468 \text{ mW}$$


$$P_{in} = \frac{12^2}{100+140} + \frac{12^2}{50+132} = 1.39 \text{ W}$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{0.468}{1.39} \times 100 = 33.6\%$$

- ✓ Efficiency is poor and power dissipation can be high
- ✓ Not suited for highly-variable output currents
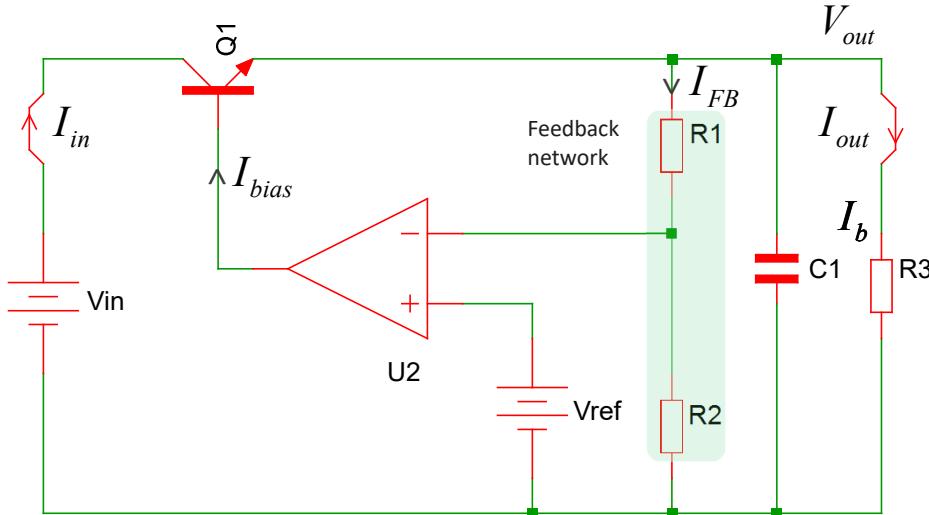
# A Controlled Resistance

- The series resistance can be replaced by a controlled element such as a transistor
- An error amplifier monitors the output voltage and adjusts the driving bias



❖ If the feedback current is neglected:




$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_{out} I_{out}}{V_{in} I_{in}} \approx \frac{V_{out}}{V_{in}} = M$$

Conversion ratio

- The efficiency depends on the difference between input and output voltages

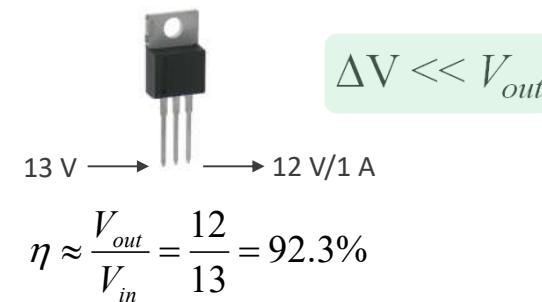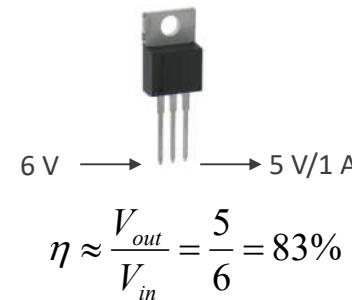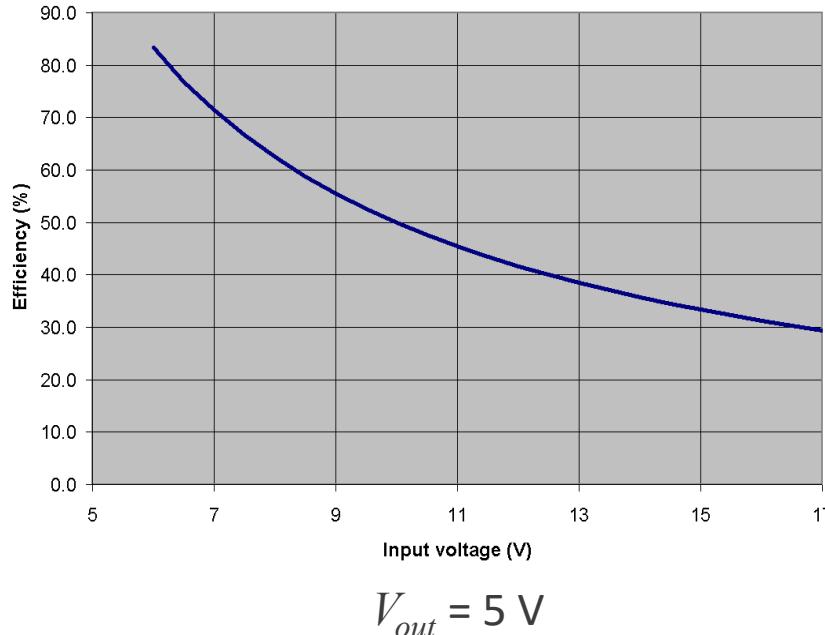
# Linear Regulators can be Efficient

- A small difference  $\Delta V$  between  $V_{in}$  and  $V_{out}$  brings good efficiency
- Efficiency betters if the  $\Delta V$  drop is reduced compared to  $V_{out}$


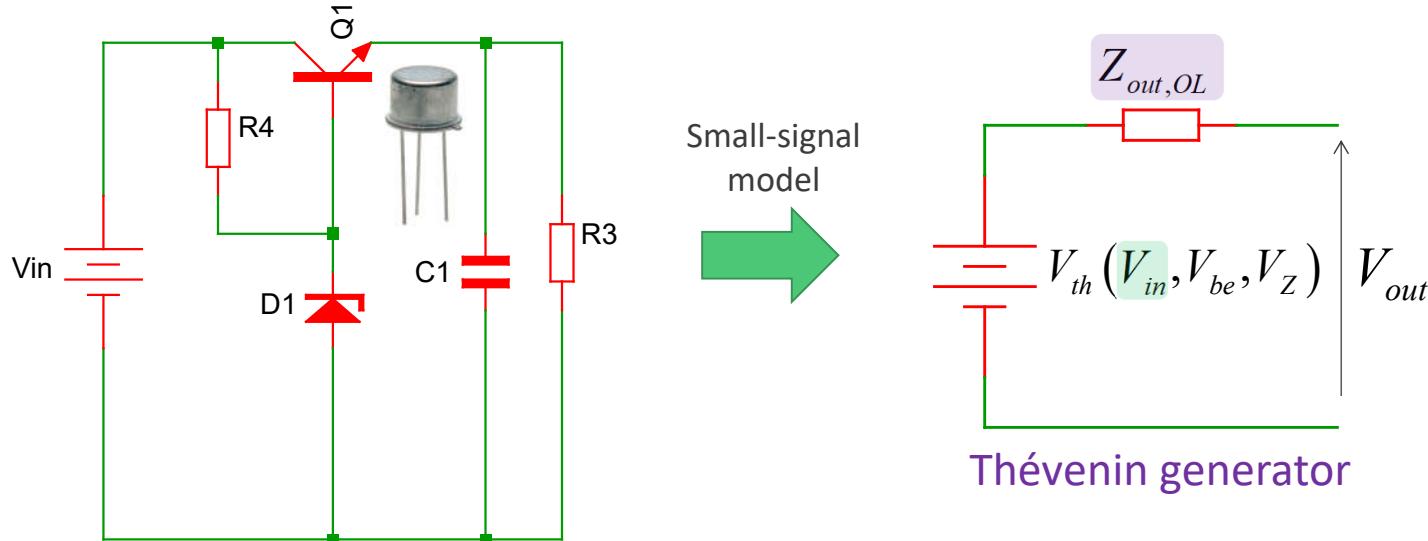
# Modeling a Linear Regulator


- Any linear system can be reduced to its equivalent Thévenin generator
- A voltage source  $V_{th}$  is affected by an output resistance  $R_{th}$



- The output voltage is made of three contributors:  $V_{in}$ ,  $I_{out}$ ,  $V_{be}$  and  $V_Z$
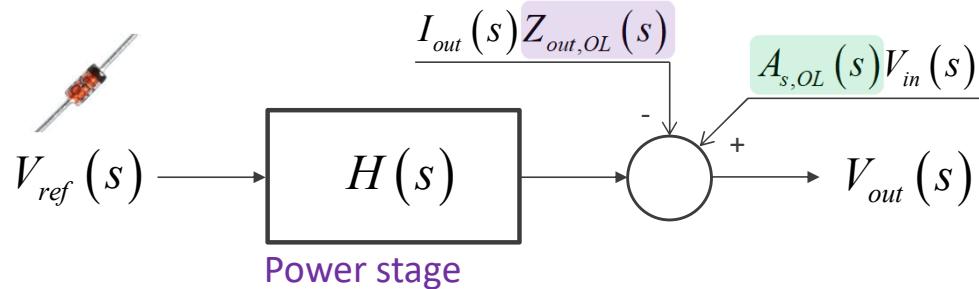
# Description by Block Diagrams

- It is possible to represent the linear regulator with blocks
- The  $H$  stage describes the bipolar transistor power stage transfer function




- We can easily write the equation describing the output voltage expression

$$V_{out}(s) = \underbrace{V_{ref}(s)H(s)}_{\text{Power stage}} - \underbrace{I_{out}(s)Z_{out,OL}(s)}_{\text{Open-loop output impedance contribution}} + \underbrace{A_{s,OL}(s)V_{in}(s)}_{\text{Open-loop input voltage contribution}}$$
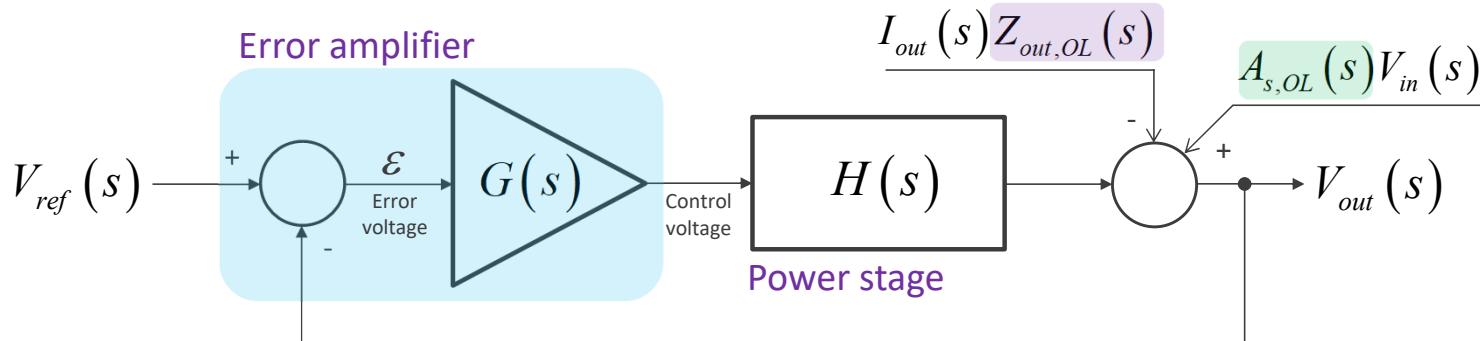
# Benefits of closing the Loop

- The deviation between the reference and the output generates an error  $\varepsilon$
- The error is then amplified and shaped by the compensator



$$V_{out}(s) = [V_{ref}(s) - V_{out}(s)]T(s) - I_{out}(s)Z_{out,OL}(s) + A_{s,OL}(s)V_{in}(s)$$

Loop gain  $\rightarrow$



$$T(s) = G(s)H(s)$$

Theoretical output  $V_{out}(s) = V_{ref}(s) \underbrace{\frac{T(s)}{1+T(s)}}_{\text{Theoretical output}} - I_{out}(s) \underbrace{\frac{Z_{out,OL}(s)}{1+T(s)}}_{\text{Closed-loop output impedance}} + V_{in}(s) \underbrace{\frac{A_{s,OL}(s)}{1+T(s)}}_{\text{Closed-loop input rejection ratio}}$

# Sensitivity Function


- A converter robustness qualifies its ability to reject perturbations
  - The input voltage, the output current or temperatures are perturbations
  - ✓ A high loop gain guarantees efficient perturbation rejection and improves robustness

$$V_{out}(s) = V_{ref}(s) \frac{T(s)}{1+T(s)} - I_{out}(s) Z_{out,CL}(s) + V_{in}(s) A_{s,CL}(s)$$

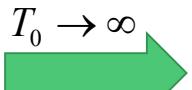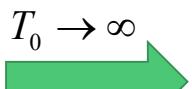 Static error	$V_{out}(s) = V_{ref}(s) \frac{T(s)}{1+T(s)}$	 $T_0 \rightarrow \infty$	$\varepsilon \rightarrow 0$	$V_{out}(s) \approx V_{ref}(s)$	No static error
 Output impedance	$Z_{out,CL}(s) = Z_{out,OL} \frac{1}{1+T(s)}$	 $T_0 \rightarrow \infty$	$R_{0,CL} \rightarrow 0 \Omega$	No output drop	
 PSRR	$A_{sc,CL}(s) = A_{sc,OL} \frac{1}{1+T(s)}$	 $T_0 \rightarrow \infty$	$A_{sc,CL} \rightarrow 0$	Infinite input rejection	
	Sensitivity function				
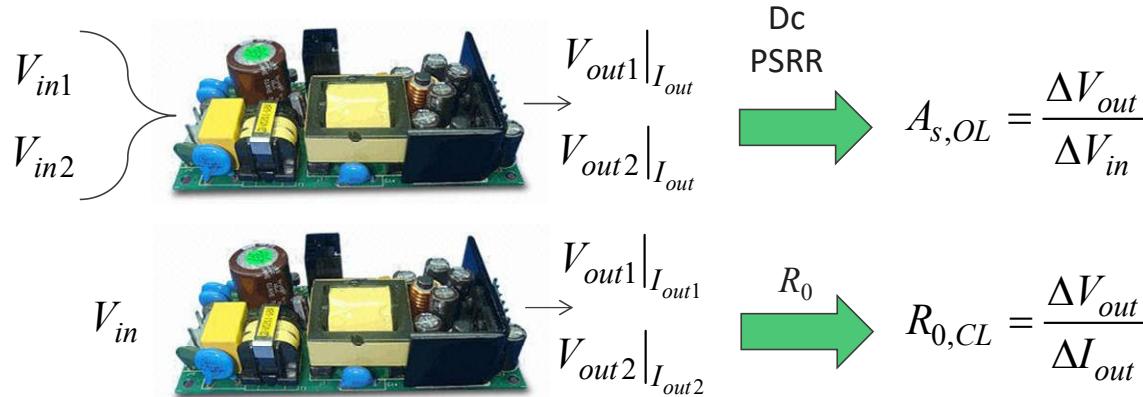
# Small-Signal Parameters



- The output impedance and the rejection ratio are all small-signal parameters
- The static values can be measured in a two-step approach



- Keep the input voltage or output current variations small for a linear behavior
- ✓ A small variation means a differentiation:  $R_{0,CL} = \frac{V_{out2} - V_{out1}}{I_{out2} - I_{out1}}$        $R_{0,CL} = \frac{dV_{out}}{dI_{out}} \Big|_{I_{out}}$
- ✓ Small-signal representation only
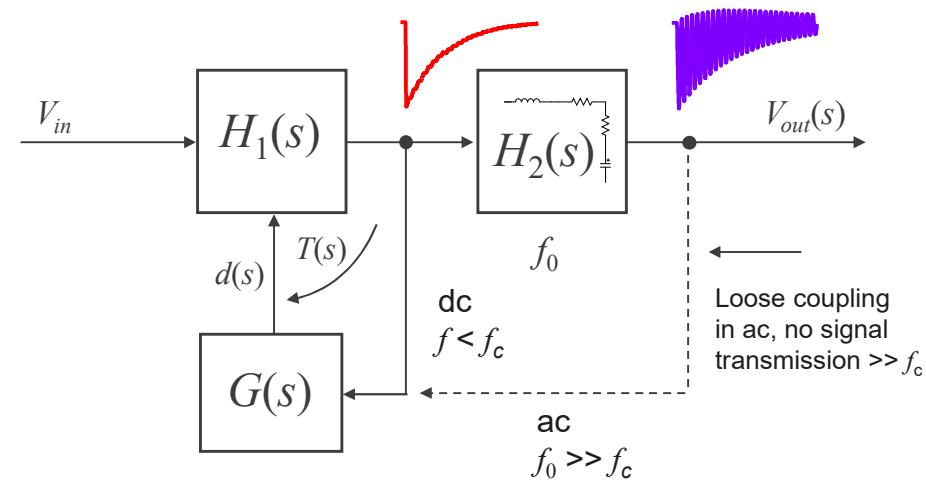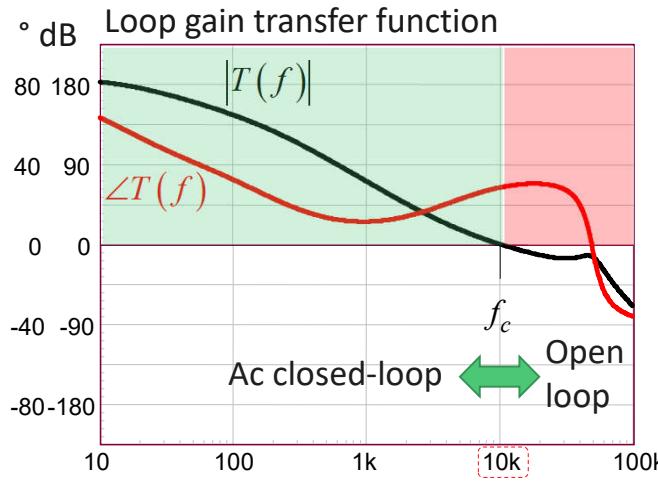
# No Gain, no Feedback!

- We know the loop gain must drop to force crossover at a given frequency
- Crossover determines the dynamic behavior of the converter: speed, reaction time
- As long as the perturbation frequency is before crossover, correction occurs
- ❖ When perturbation frequency is beyond crossover, ac feedback is gone: open loop!



# Agenda

---

- Power Conversion Mechanisms
- Switching Cells and Control Schemes
- The Buck
- The Boost
- The Buck-Boost
- Introduction to Control Loop Design
- EMI Filter Interaction
- Introduction to Simulation


# Core Switching Cells

- The basic switching cells consist of three different converters

- ✓ The buck converter – it reduces the input voltage


- ✓ The boost converter – it increases the input voltage

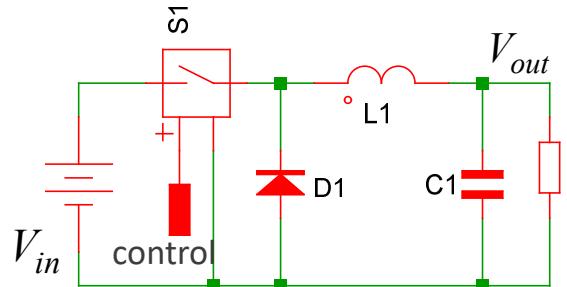- ✓ The buck-boost converter – it can increase or decrease the input voltage




$$V_{out} < V_{in}$$

Buck

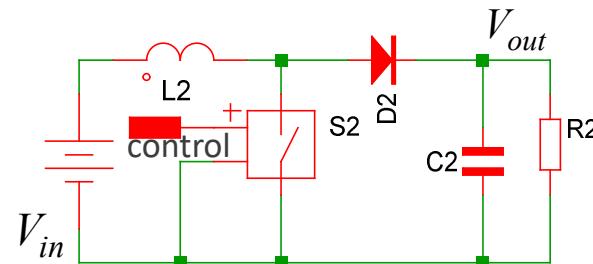

$$V_{out} > V_{in}$$

Boost



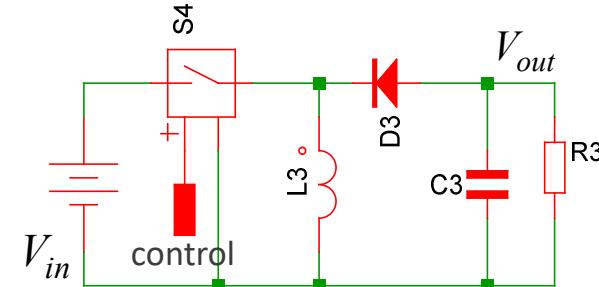


$$|V_{out}| < \text{or} > V_{in}$$


Buck-boost
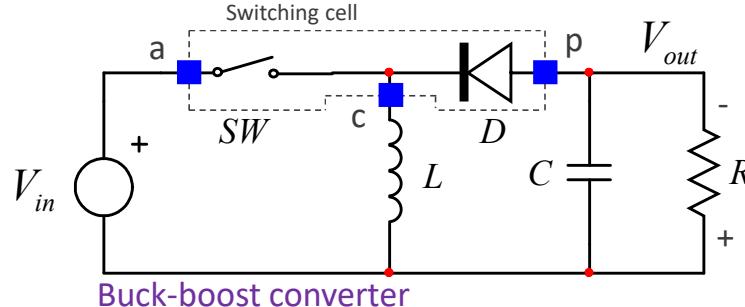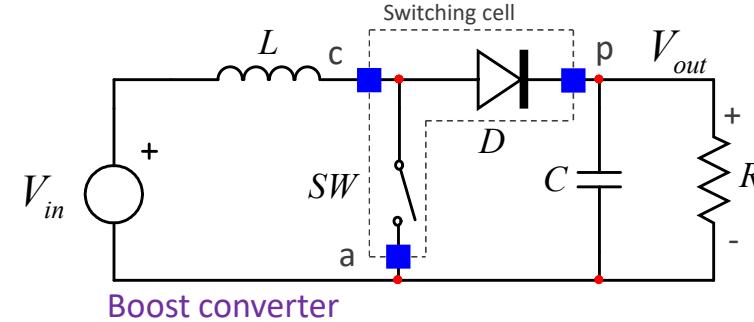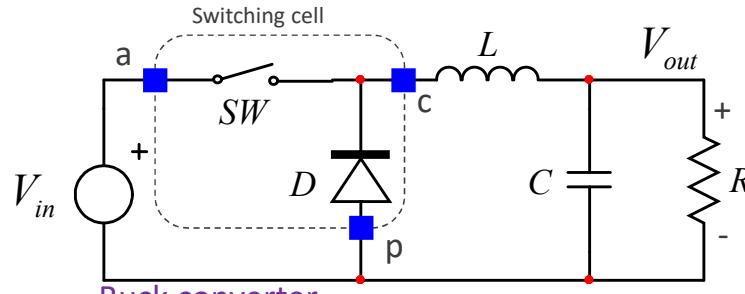
# A Two-Switch Model

- Each basic structure shares a common switch + diode arrangement
- The switching cell is actually a single-pole double-throw power switch




PWM switch  
model

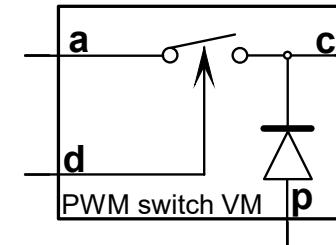

a: active  
c: common  
p: passive
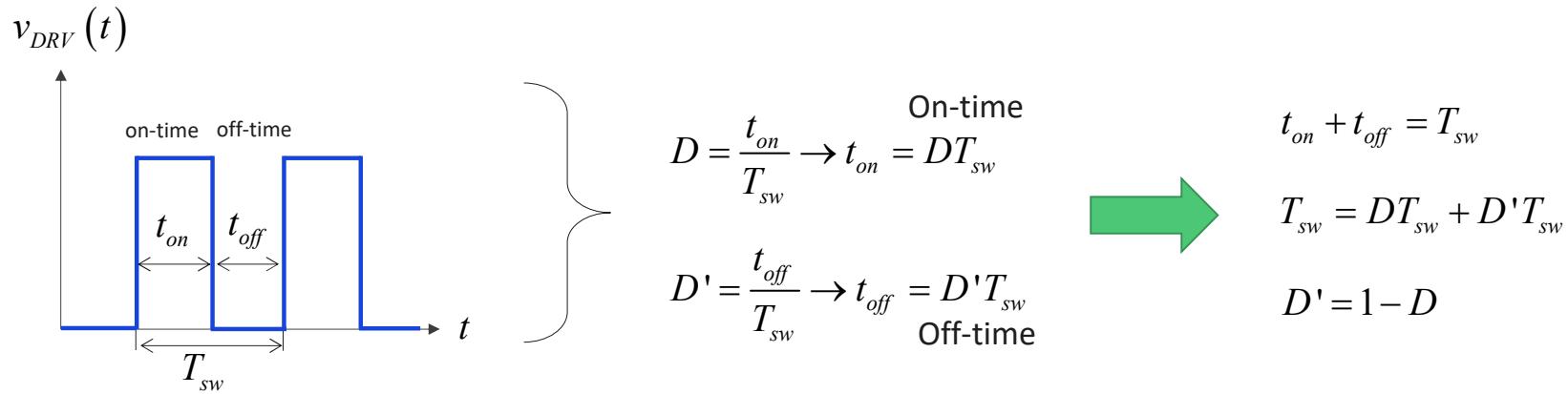
# Frequency and Duty Ratio

- The duty ratio  $D$  defines the on-time duration divided by the switching period  $T_{sw}$




- There are two events in the switch activation: one switch is off while the other is off
- This is typical of a converter operated in continuous conduction mode or CCM
- A third event with all switches off occur in discontinuous conduction mode or DCM

For all basic cells, the duty ratio  $D$  controls the output voltage

# Inductive Current

- The current in an inductor ramps up and down during the switching period
- The current slope  $S$  in A/s depends on the voltage applied across the inductor:
  - > The inductor energizes (stores energy) during the on-time
  - > The inductor de-energizes (releases energy) during the off-time

$$S = \frac{V}{L} \frac{[A]}{[s]}$$

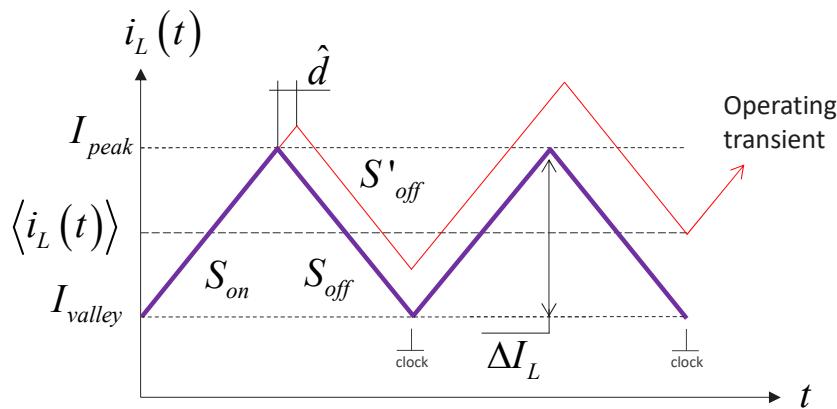


- ✓ The distance between  $I_{peak}$  and  $I_{valley}$  defines the ripple current  $\Delta I_L$
- ✓ Current starts from  $I_{valley}$  and returns to the same level within the switching cycle
- ❖ If current keeps increasing: saturation



If valley current is the same within one cycle: steady-state operation
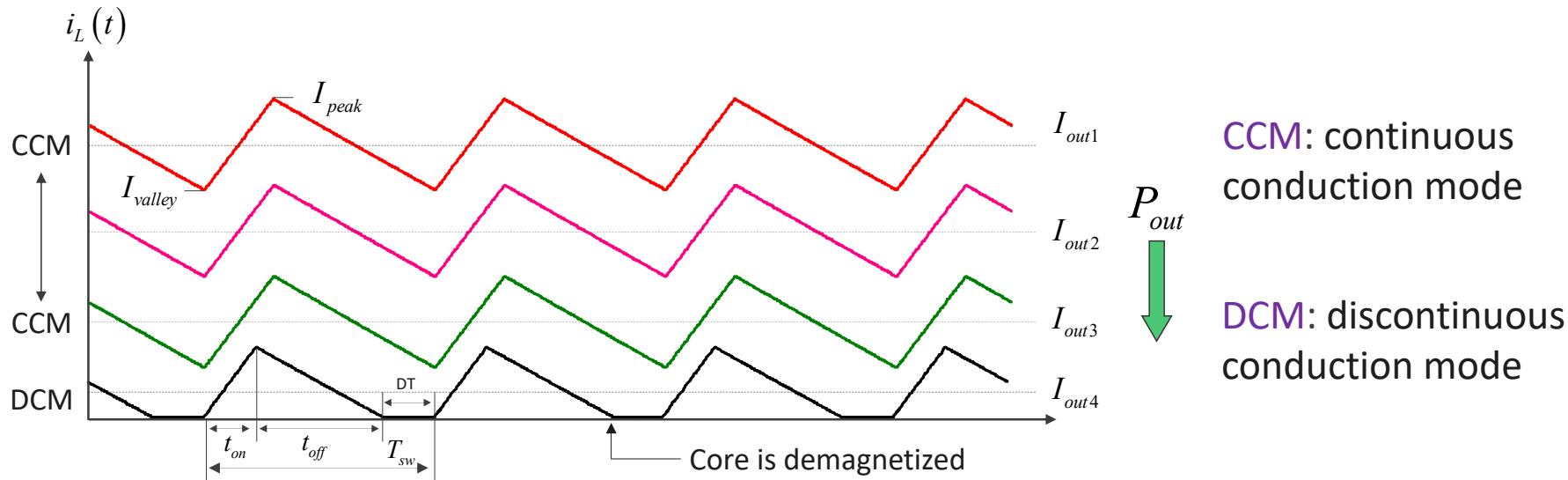
# Conduction Mode


- The peak and valley currents determine the amount of processed energy
- Their levels depend on operating conditions set by input and output values



- ✓ The converter operates in heavy CCM then goes into lighter CCM as  $P_{out}$  decreases
- ✓ In light-load conditions, the valley current disappears and DCM is entered
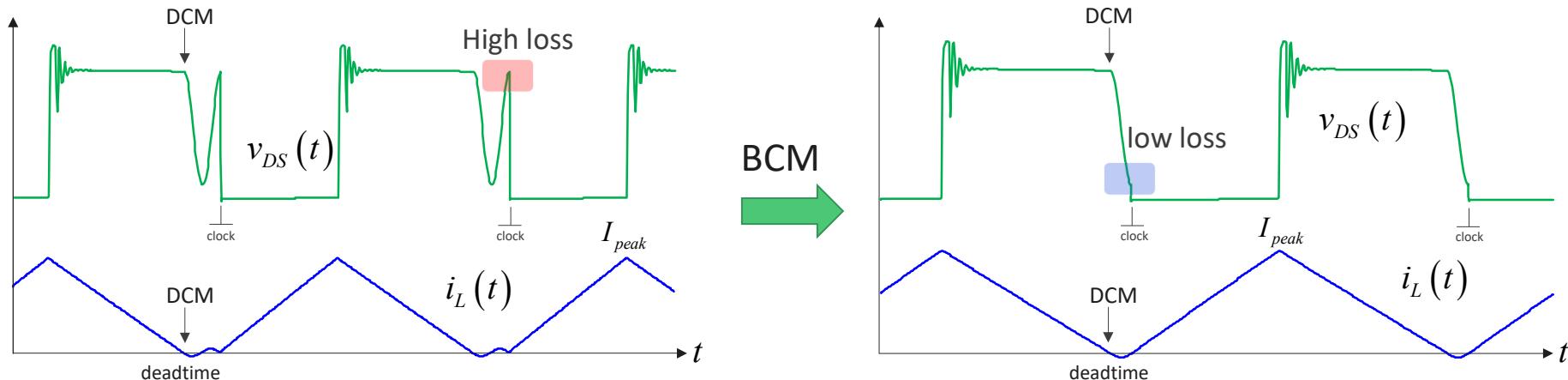
# Borderline Conduction Mode

- A deadtime appears in DCM where both switches are blocked
- A specific control scheme restarts the main switch when the valley is 0 A




- ✓ Inserting a smaller deadtime in BCM leads to reducing the turn-on losses
- ❖ A BCM-operated converter offers a highly variable switching frequency


# Control Techniques

- A switching converter can be controlled in different ways
- The most classical solutions are fixed-frequency voltage- and current-mode control

## Voltage mode

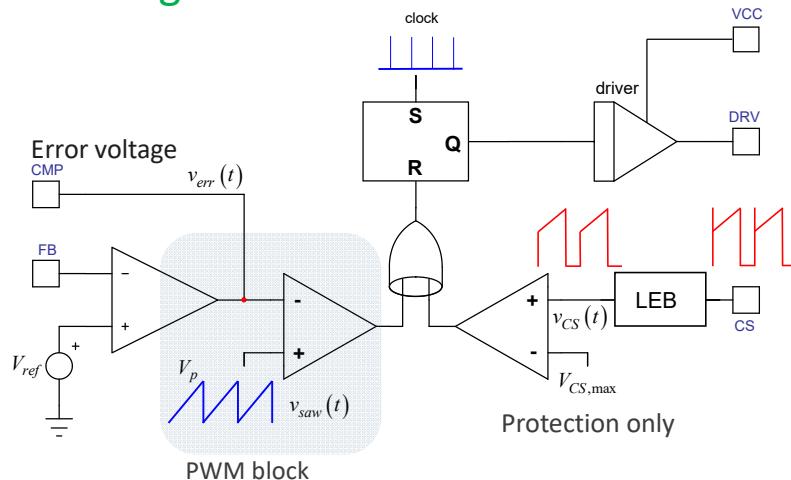

## Current mode

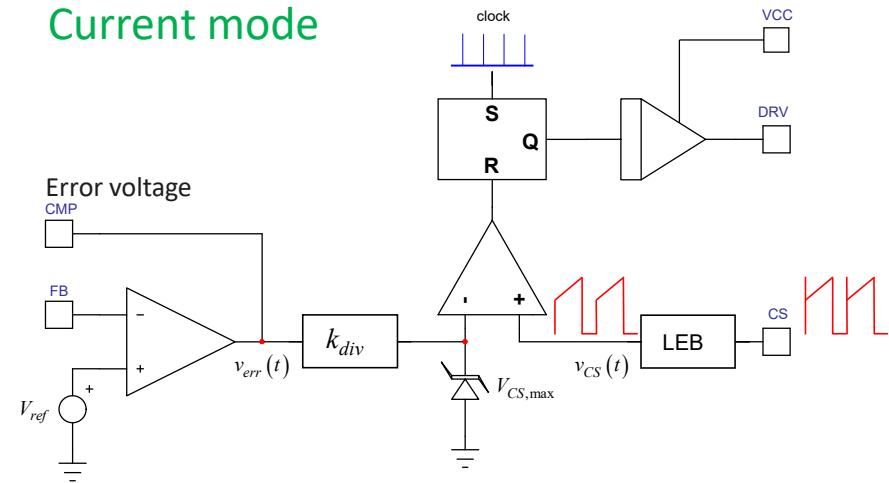

- ✓ In VM control, the error voltage *directly* determines the duty ratio
- ✓ In CM control, the error voltage controls the peak current and *indirectly* the duty ratio

# Voltage- and Current-Mode Control

- Each control technique presents advantages and drawbacks

## Voltage-mode control:

- Ease of implementation: no need to sense inductor current
- Can operate down to very low duty ratio
- Large-amplitude artificial voltage brings good noise immunity
- Inherently-low output impedance
  - Poor input rejection: any perturbation must first propagate before correction
  - Second-order response complicates compensation

## Current-mode control:

- Natural input feedforward brings excellent input voltage rejection
- Inherent cycle-by-cycle overcurrent protection
- First-order response eases feedback loop design
  - Inherently-high output impedance requires high loop gain
  - Sub-harmonic instability in CCM needs slope compensation
  - Difficult to operate at very low duty ratio




many controllers operate in voltage-mode control



Mostly current-mode control
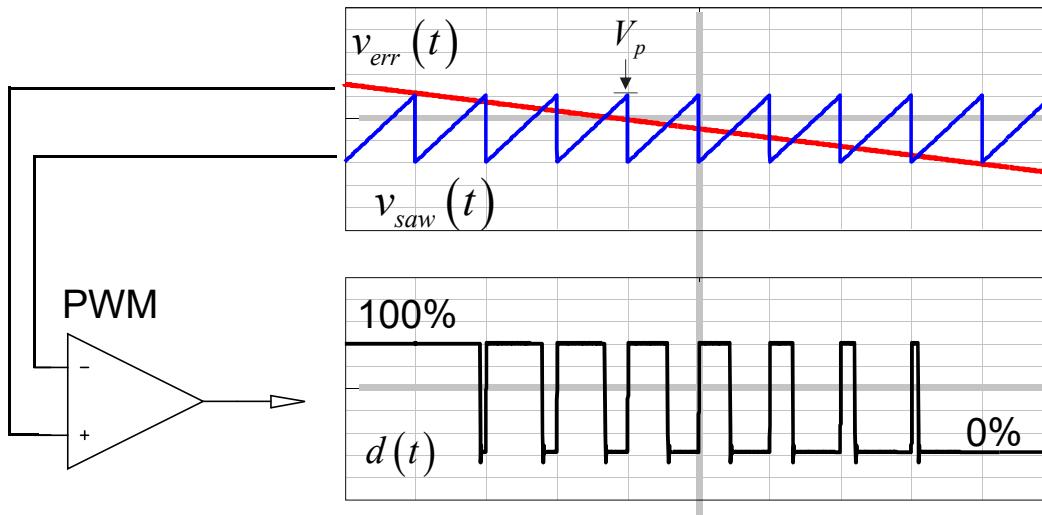
# Voltage-Mode Control – Duty Ratio Generator

- The duty ratio is obtained by comparing a sawtooth and the error voltage
- When the two signals intersect, the comparator toggles



$$v_{saw}(t) = V_p \frac{t}{T_{sw}}$$

$$v_{err}(t) = V_p d(t)$$

↓


$$d(t) = \frac{v_{err}(t)}{V_p}$$

Discrete value!


- This is a *naturally sampled* modulator
- The small-signal gain of this PWM block is  $G_{PWM} = \frac{1}{V_p}$
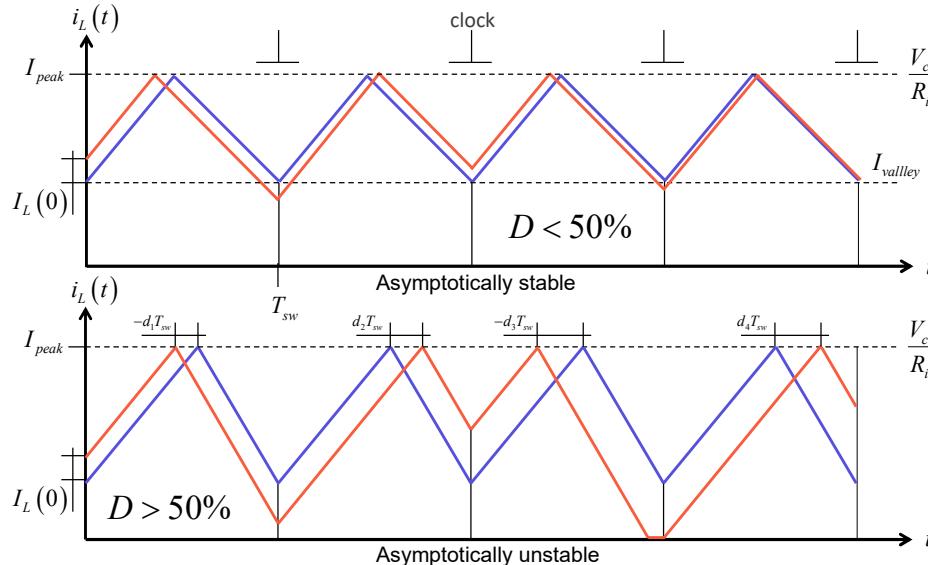
# Current-Mode Control – Subharmonic Oscillations

- Current-mode-controlled converters can become unstable in CCM
- When the duty ratio approaches 50% subharmonic oscillations can appear






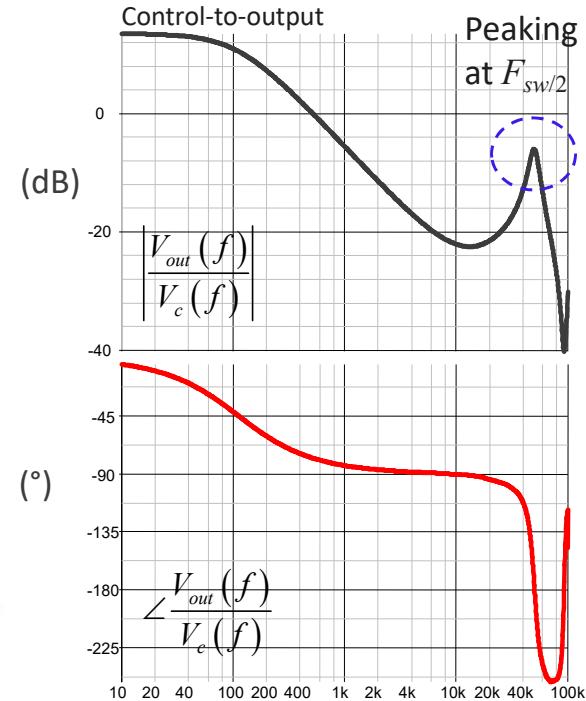- ✓ The inner current loop can bring instability
- ✓ Slope compensation helps stabilizing the loop


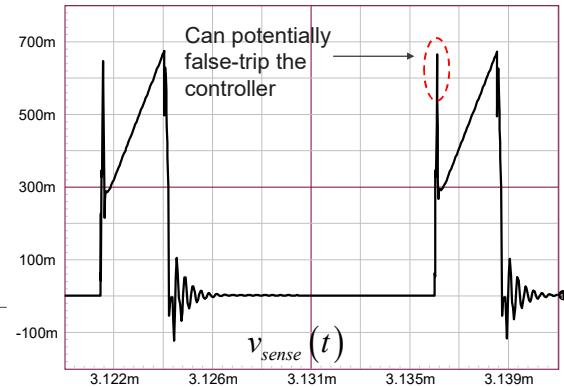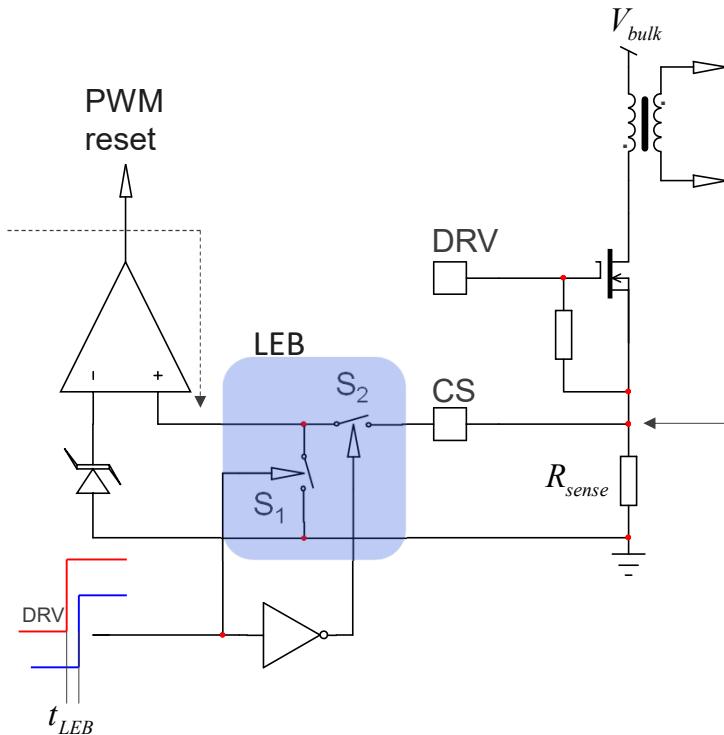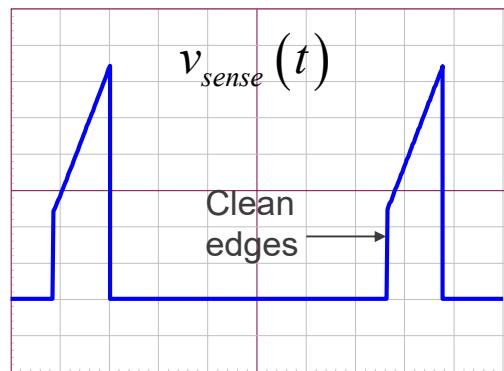
# Leading-Edge Blanking

- For reliable operations it is important to sense the switch current cycle by cycle
- Regardless of the control mode, the inductor current needs to be cleaned up




✓ The LEB cleans the signal up and ensures reliable operation


✓ The voltage image of the current is polluted by spikes
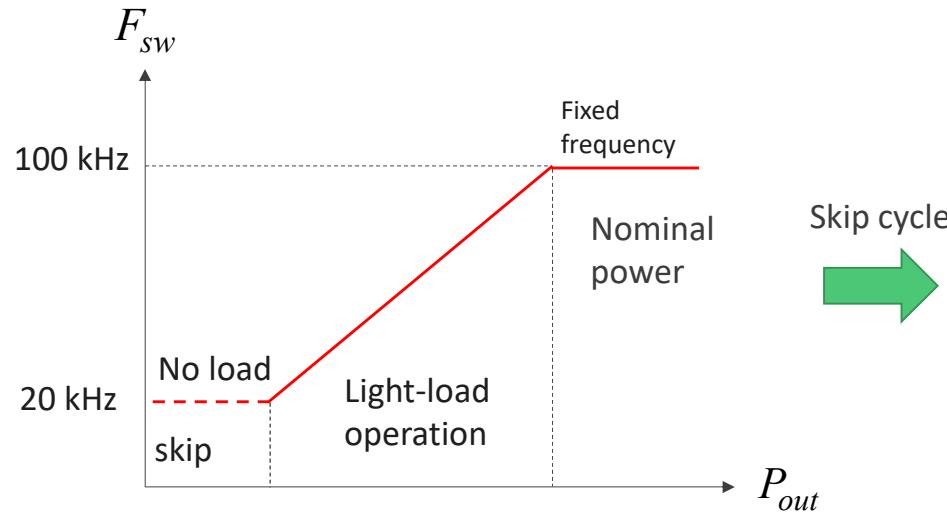
# Skip Cycle and Frequency Reduction

- For efficient light-load operations, frequency foldback can be implemented
- In no-load conditions the part can enter skip cycle to further improve standby





Skip cycle

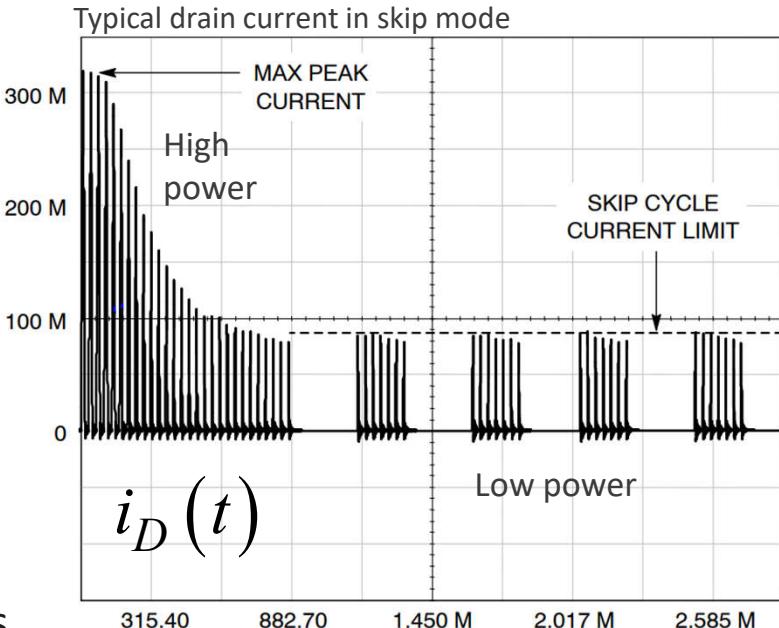

✓ Frequency linearly reduces as power decreases
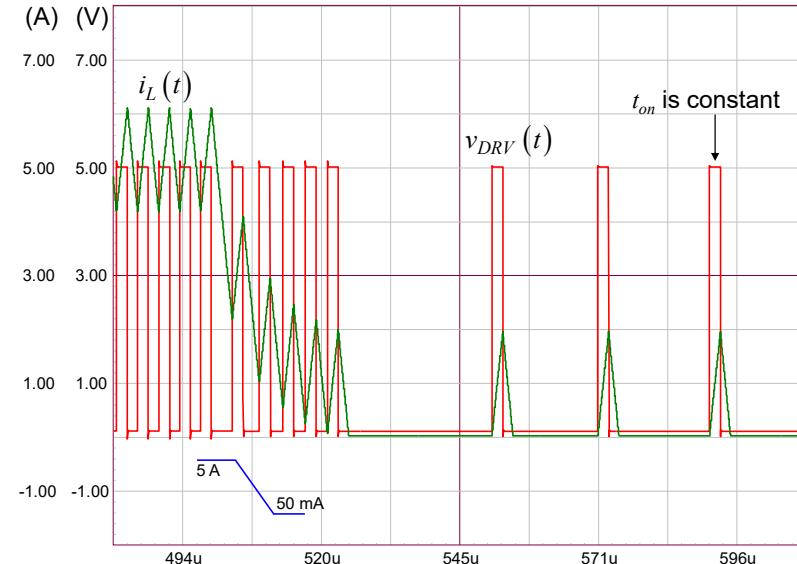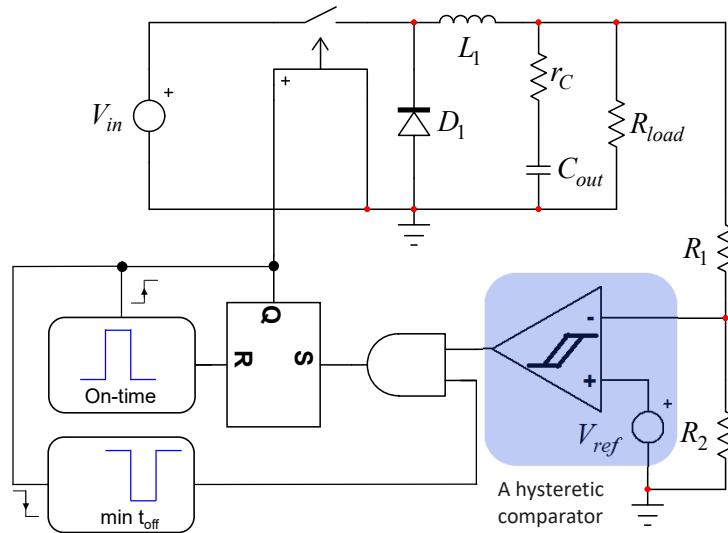
# Hysteretic Converters


- A comparator affected by a hysteresis band trips a constant-on-time circuit
- The circuit is intrinsically unstable and does not require compensation



- ✓ The frequency adapts to the input and output conditions
- ✓ The circuit naturally enters a low-frequency mode in light-load conditions
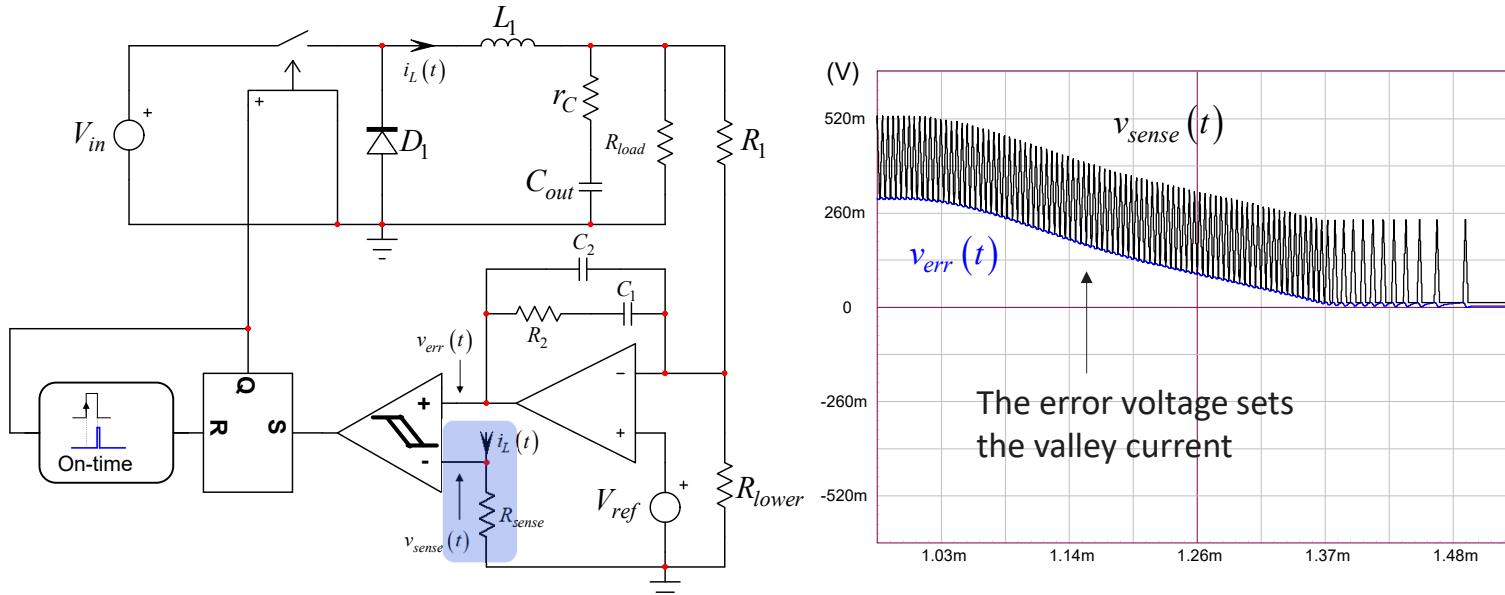
# Hysteretic Converters with an Op-Amp

- The hysteretic constant-on-time converter can be supplemented with an op-amp
- The converter operates in current-mode control with a valley setpoint adjustment



- ✓ Immune to sub-harmonic oscillations
- ✓ Naturally goes in standby mode in light-load



# Agenda

---

- Power Conversion Mechanisms
- Switching Cells and Control Schemes
- The Buck
- The Boost
- The Buck-Boost
- Introduction to Control Loop Design
- EMI Filter Interaction
- Introduction to Simulation


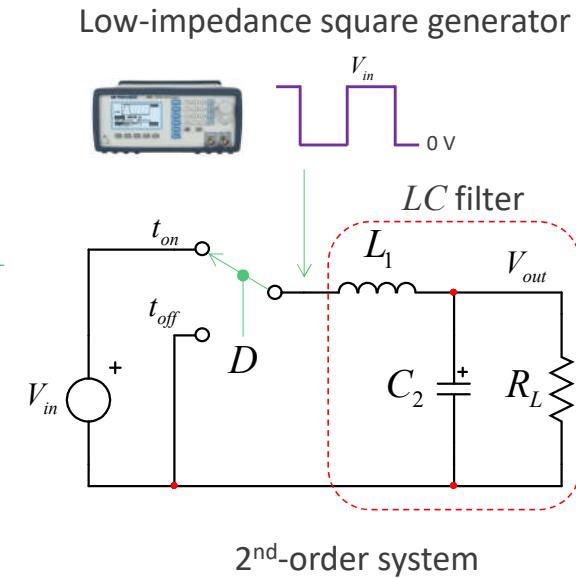
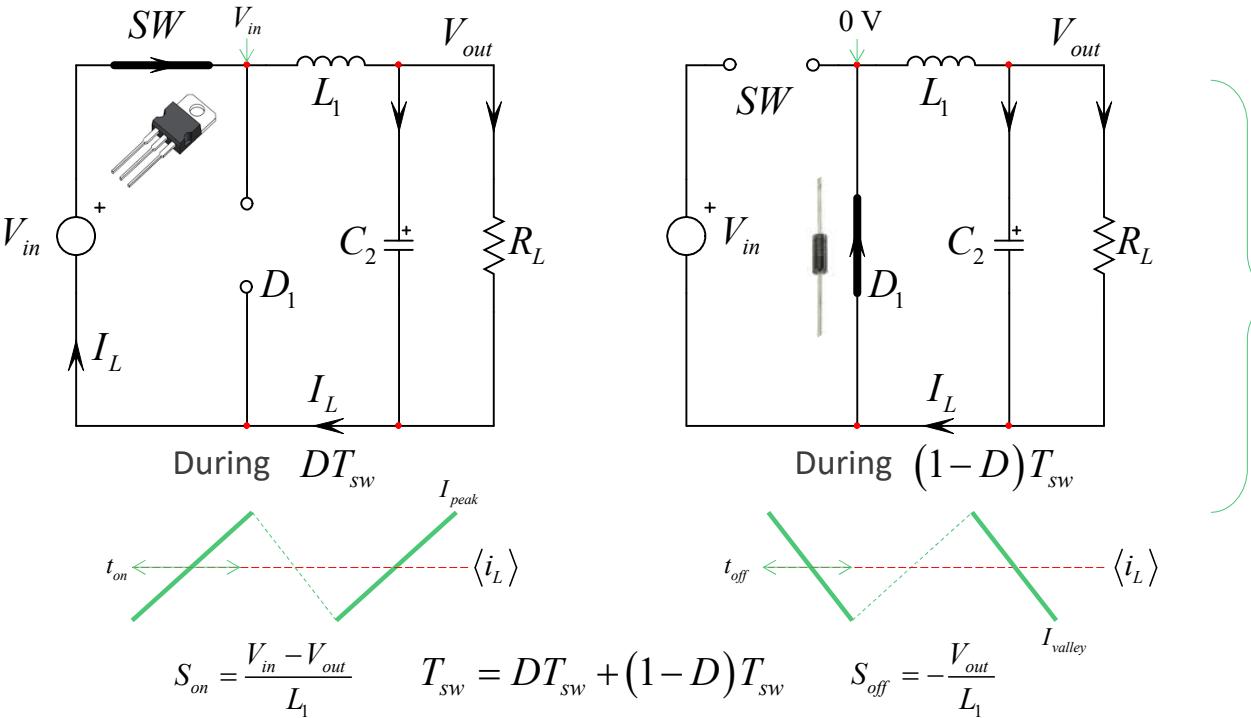
# The Buck Converter

- The buck converter reduces the input voltage and operates up to 100% duty ratio
- The common SW-D node swings between  $V_{in}$  and 0 V


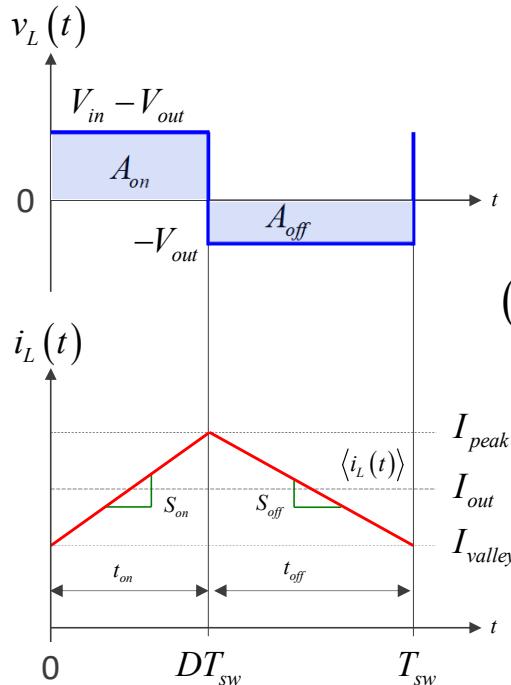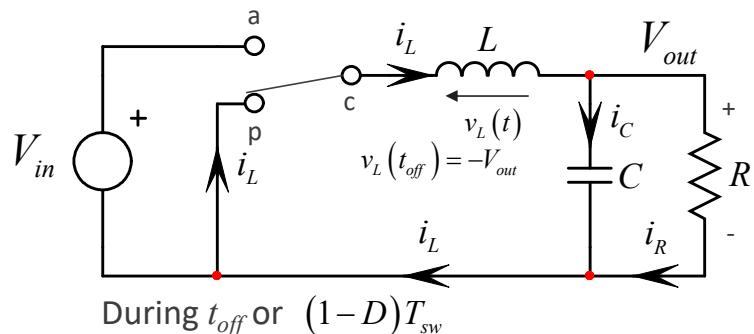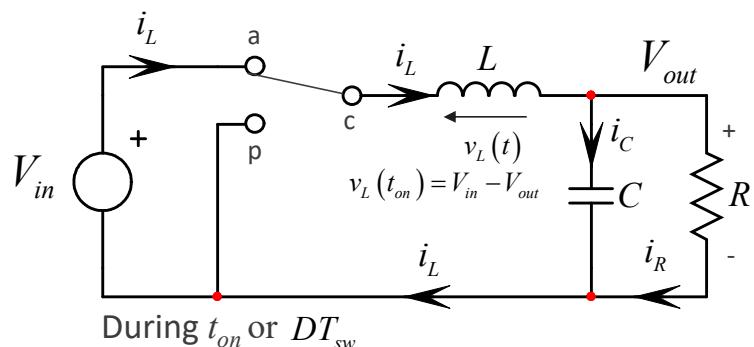
# Transfer Characteristic of the CCM Buck

- Consider the average inductor voltage to determine the dc transfer characteristic
- Express the volt-seconds of the inductor during the on- and off-times



V-s balance

$$\langle v_L(t) \rangle_{T_{sw}} = 0 \text{ V}$$


$$(V_{in} - V_{out})DT_{sw} = V_{out}(1-D)T_{sw}$$

$$V_{out} = DV_{in}$$

$$M = \frac{V_{out}}{V_{in}} = D$$

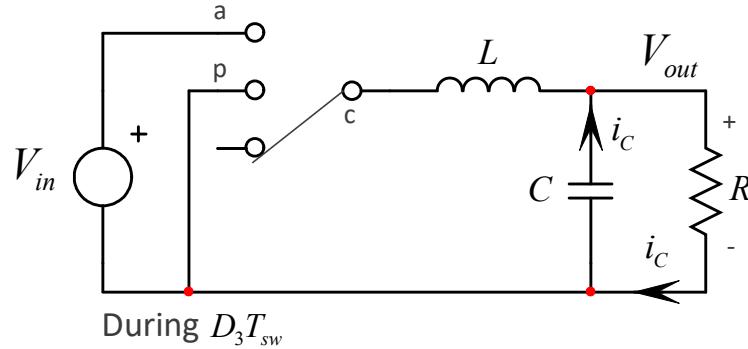
# Transfer Characteristic of the DCM Buck

- When the load current decreases, the valley current goes to 0 A and deadtime appears
- The condition at which DCM occurs is determined by the *critical* input or load value



$$R_{critical} = \frac{2LF_{sw}}{1-D}$$

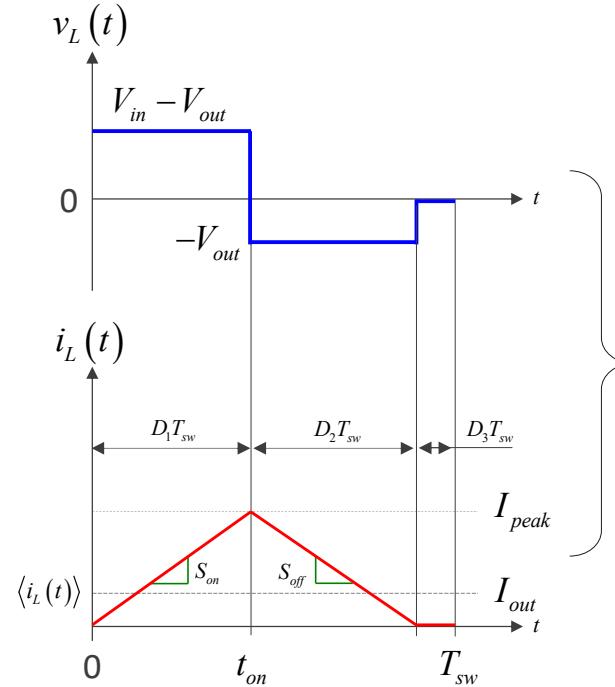$R < R_{critical} \rightarrow \text{CCM}$   
 $R = R_{critical} \rightarrow \text{BCM}$   
 $R > R_{critical} \rightarrow \text{DCM}$




$$M = \frac{2}{1 + \sqrt{1 + \frac{8LF_{sw}}{RD_1^2}}}$$

- ✓ Depends on  $F_{sw}$
- ✓ Depends on  $R$
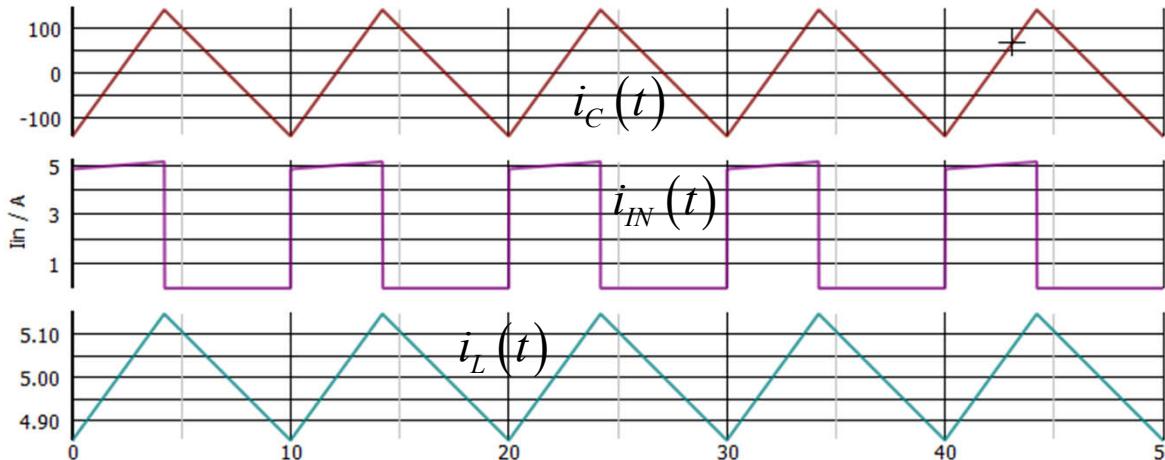
# Input and Output Currents

- It is important to know the nature of the circulating input and output currents
- The inductance located in the output naturally smooths current which is *non-pulsating*
- The input current is *pulsating* and highly discontinuous: high ac component




- ✓ The output capacitor is non-pulsating and is of low rms value
- ✓ The input current is highly discontinuous and contributes a high rms value
- ✓ The inductor current is a smooth triangular waveform

- The buck converter is quiet on the output and noisy on the input: difficult EMI
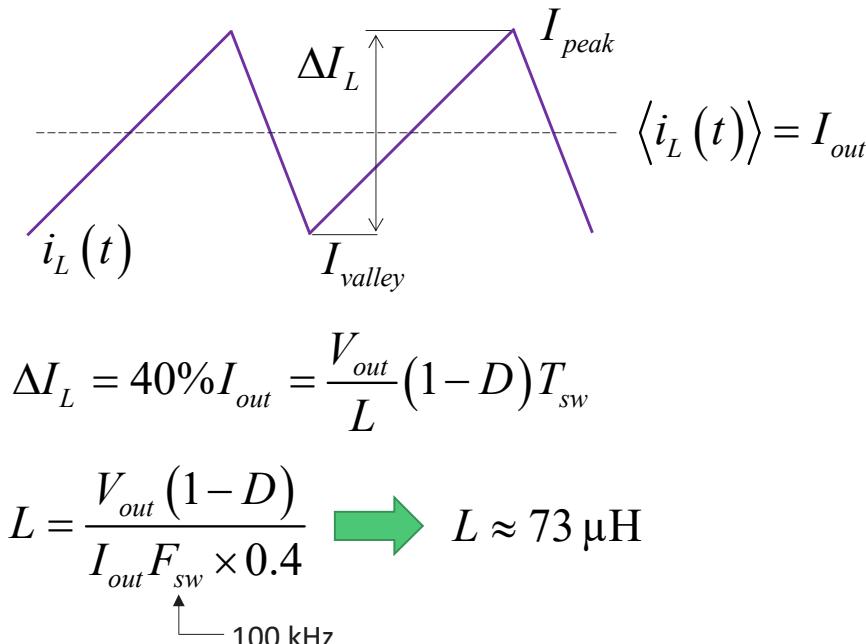
# Peak Current and Inductor Value

- From the output current and the acceptable ripple you can pick the right switcher
- The sweet spot of the inductor ripple current is around 40% with modern core
- How to select the switcher maximum peak current?



- ✓ Assume  $V_{in} = 12 \text{ V}$ ,  $V_{out} = 5 \text{ V}$ ,  $I_{out} = 1 \text{ A}$
- ✓ Select a ripple of 40%

$$I_{peak} = I_{out} + \frac{\Delta I_L}{2}$$

$$I_{peak} = I_{out} + \frac{40\% I_{out}}{2} = I_{out} \left(1 + \frac{0.4 \times 1}{2}\right)$$


↓

$$I_{peak} = 1 \times \left(1 + \frac{0.4 \times 1}{2}\right) = 1.2 \times I_{out} = 1.2 \text{ A}$$


Choose a switcher with at least this peak
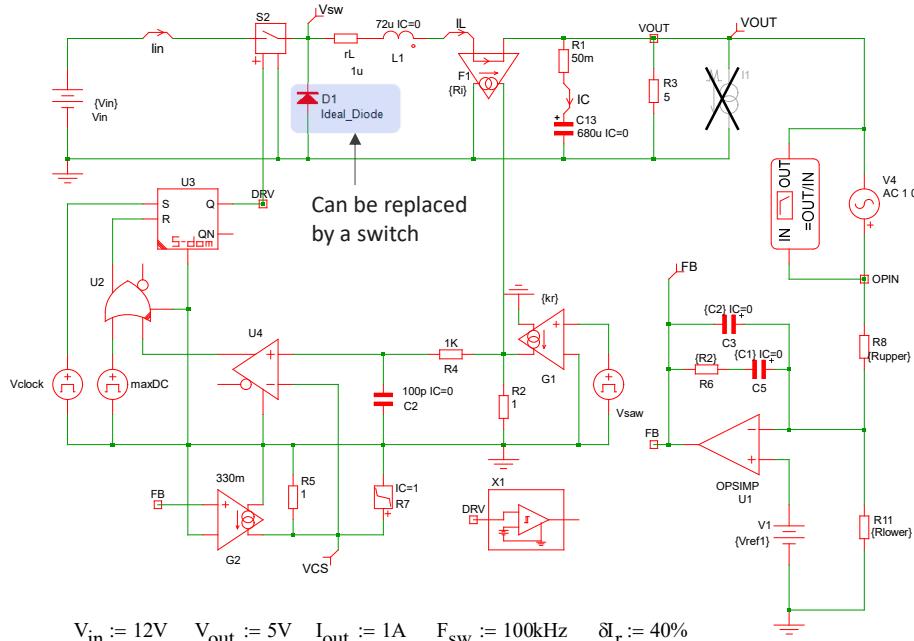
# Simulation Gives Immediate Results

- It is interesting to run a quick SIMPLIS simulation to verify the calculated values
- The buck can be operated at its nominal conditions 5 V/1 A from the 12-V input



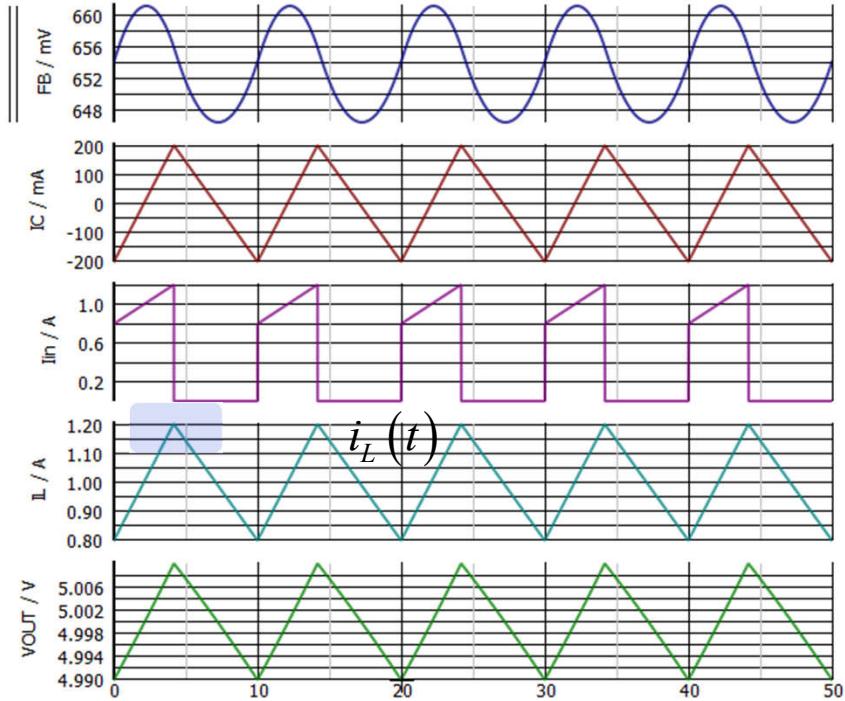
$$D := \frac{V_{out}}{V_{in}} = 41.667\% \quad L_1 := \frac{V_{out} \cdot (1 - D)}{F_{sw} \cdot I_{out} \cdot \delta I_r} = 72.917 \mu H$$


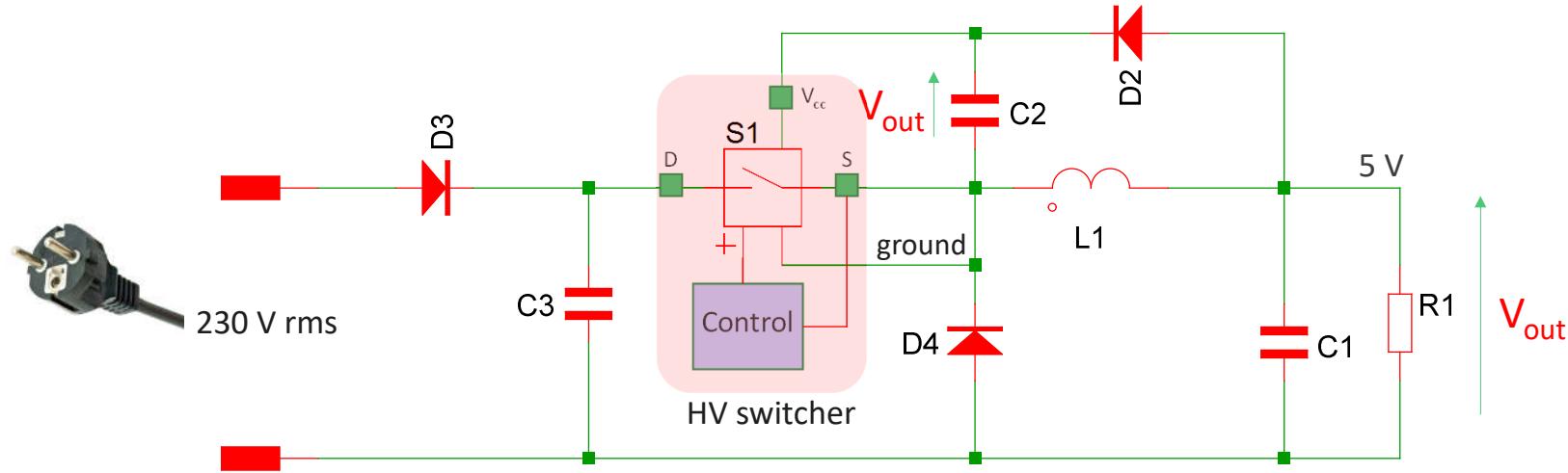
# High-Side Buck


- The control section can be ground-referenced or floating for high-voltage switchers
- The output voltage is rectified and referenced to the source of the switcher



- ✓ Any low- or high-voltage switcher can be used in a floating configuration
- Watch for feedback polarity which should allow duty ratio reduction with bias increase
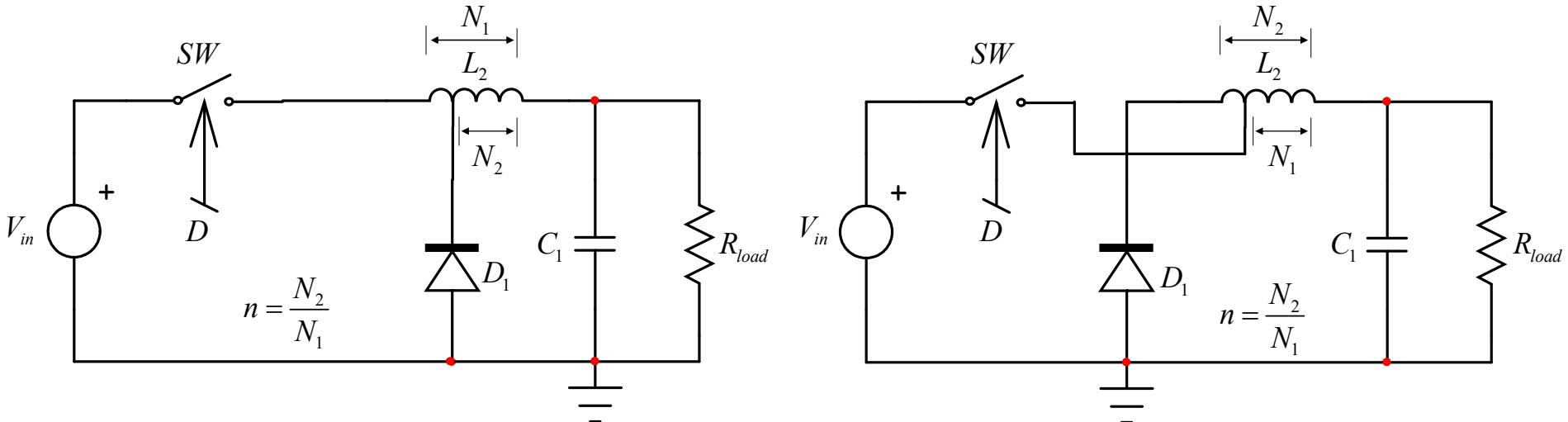
# Buck-Derived Topologies


- The tapped-buck converter can be used for large differences between  $V_{out}$  and  $V_{in}$
- It brings a higher duty ratio despite a low output voltage



✓ The transfer characteristic of the tapped buck is  $M = \frac{D}{D + \frac{1-D}{n}}$
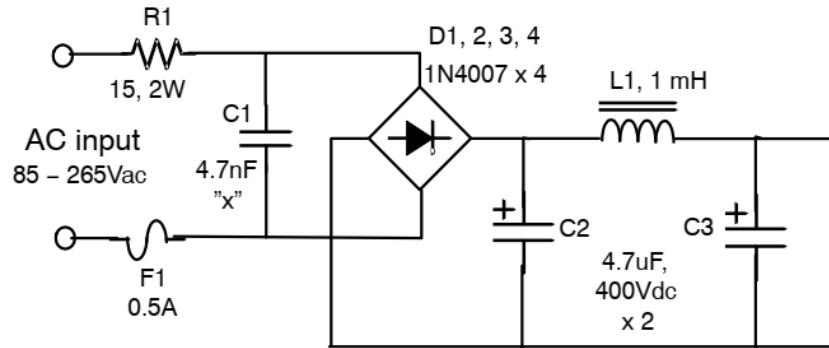
# Typical Tapped Buck Application


- A tapped buck lends itself well to high-voltage non-isolated converters
- The duty ratio is increased owing to the tap in the inductor



$$D = \frac{V_{out}}{V_{in}} = \frac{12}{330} = 3.6\%$$


With a tapped inductor
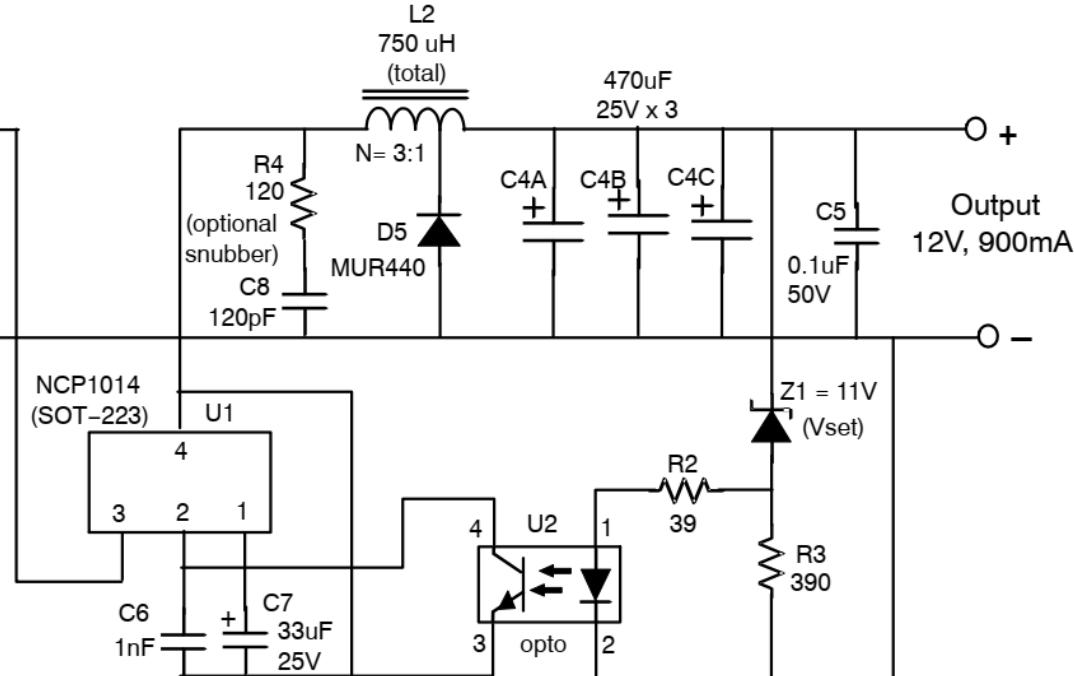
$$D = \frac{M}{M + n(1-M)} = \frac{12/330}{12/330 + \frac{1}{3}\left(1 - \frac{12}{330}\right)} \approx 10\%$$



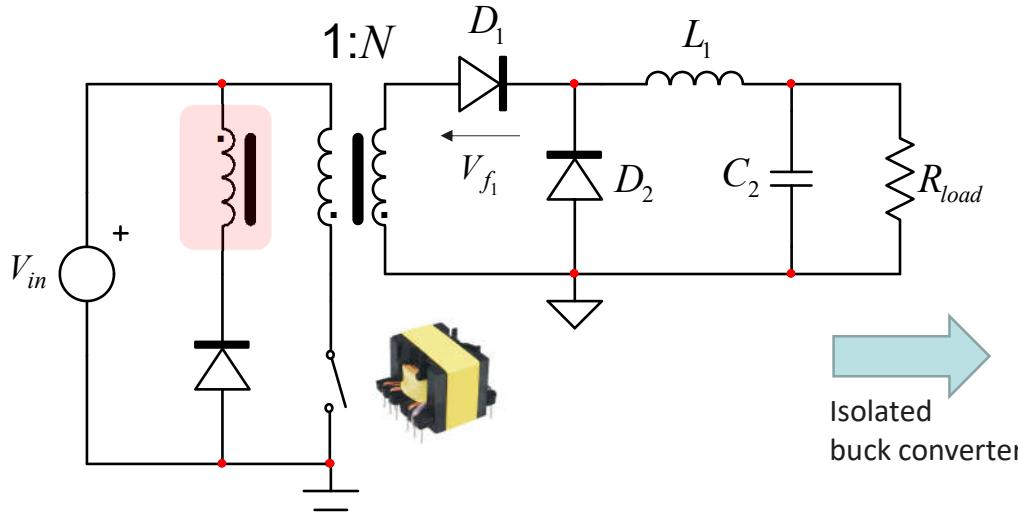
# The Forward Converter

- A transformer provides the necessary galvanic isolation for safe operations
- The transformer features 3 windings and one of them performs core reset



Isolated  
buck converter

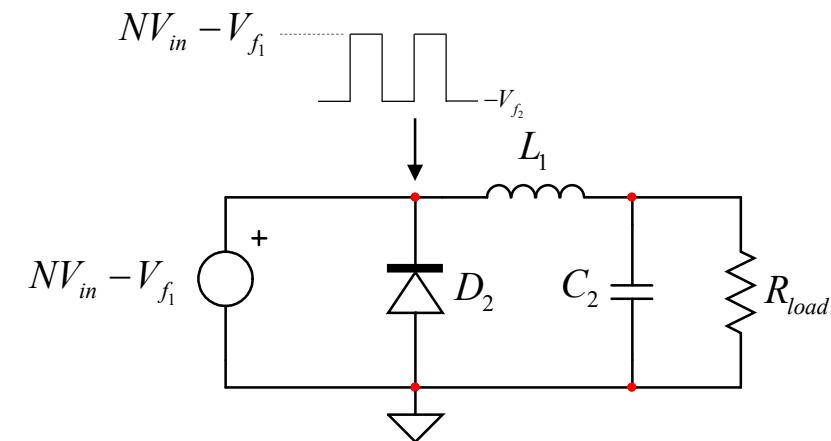

- ✓ Well suited for low output voltage with strong output currents
- ✓ Very popular in multi-output coupled-inductors silver boxes for computers





# Agenda

---

- Power Conversion Mechanisms
- Switching Cells and Control Schemes
- The Buck
- The Boost
- The Buck-Boost
- Introduction to Control Loop Design
- EMI Filter Interaction
- Introduction to Simulation

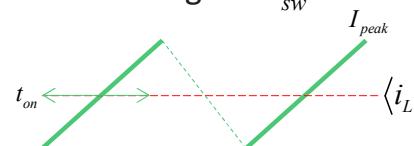
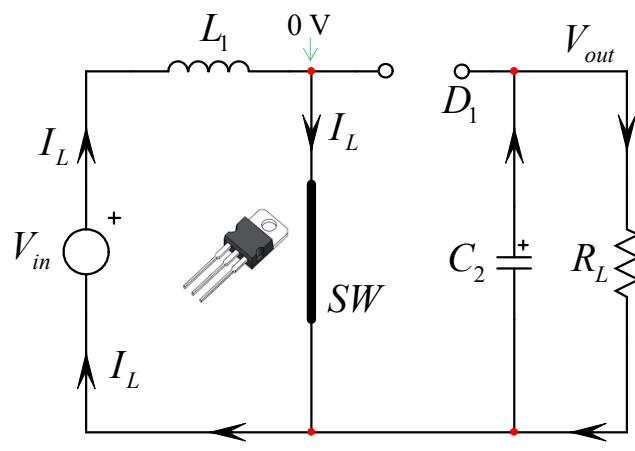
# The Boost Converter

- The boost converter increases the input voltage up to a certain limit
- The common SW-D node swings between 0 V and  $V_{out}$



$$S_{on} = \frac{V_{in}}{L_1}$$



$$T_{sw} = DT_{sw} + (1-D)T_{sw}$$

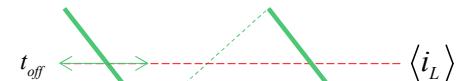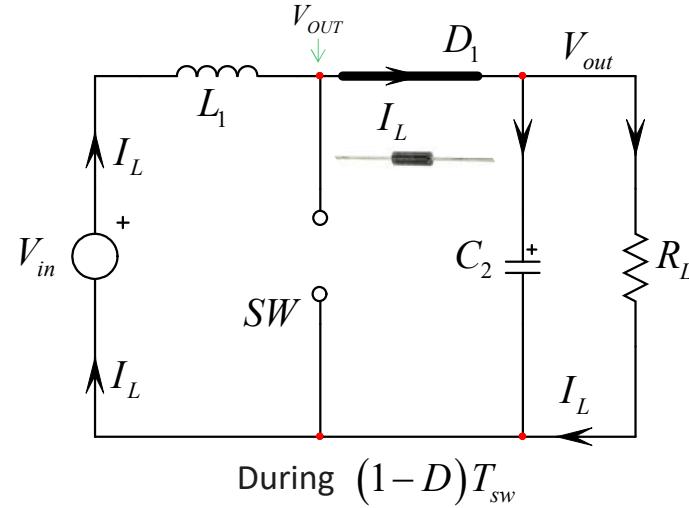

$$S_{off} = -\frac{V_{out} - V_{in}}{L_1}$$
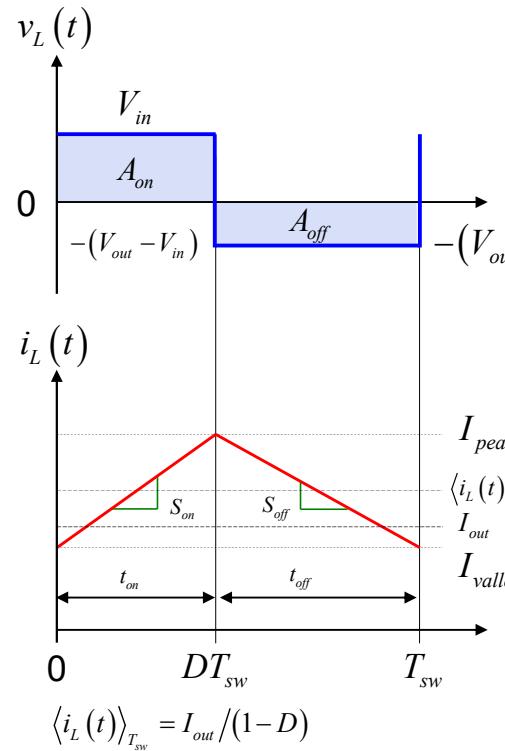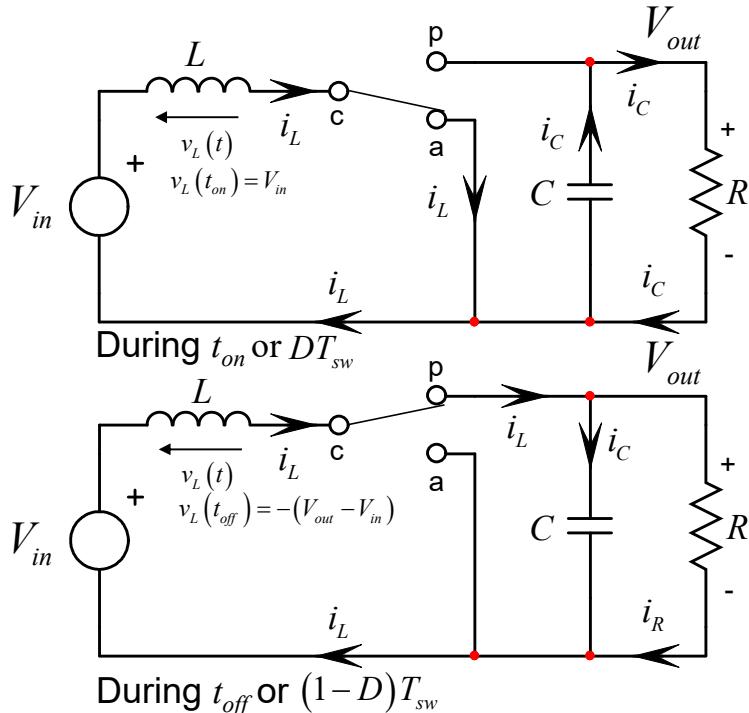
# Transfer Characteristic of the CCM Boost

- Consider the average inductor voltage to determine the dc transfer characteristic
- Express the volt-seconds of the inductor during the on- and off-times



$$\text{V-s balance} \quad \langle v_L(t) \rangle_{T_{sw}} = 0 \text{ V}$$



$$V_{in}DT_{sw} = (V_{out} - V_{in})(1-D)T_{sw}$$

$$V_{out} = \frac{V_{in}}{1-D}$$


$$M = \frac{1}{1-D}$$
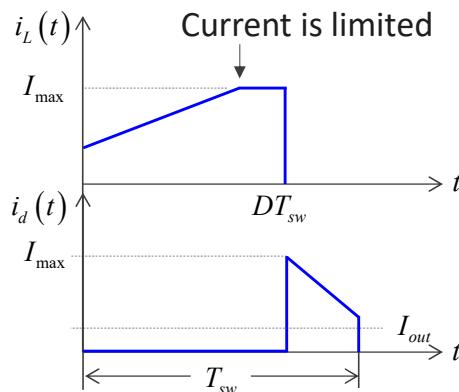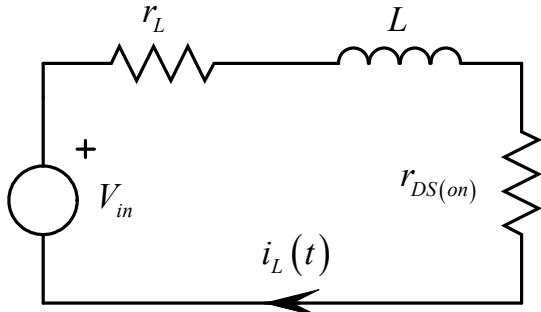
# A Finite Conversion Ratio

- The conversion ratio is limited by ohmic losses in the circuit
- The output can fall if duty ratio keeps increasing past a limit: this is the latch-up effect




**Latch-up effect**

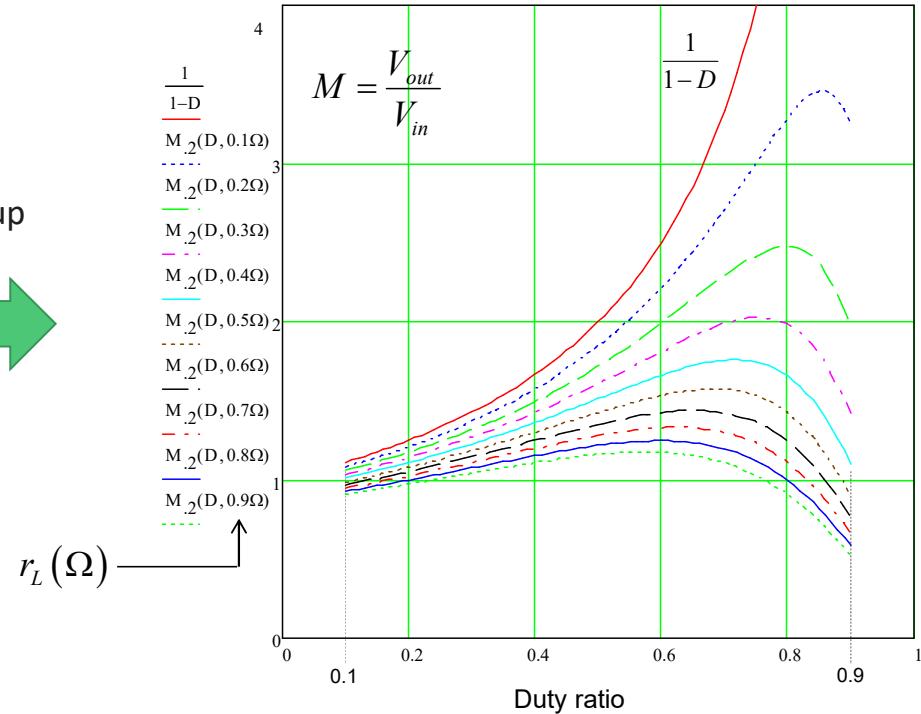

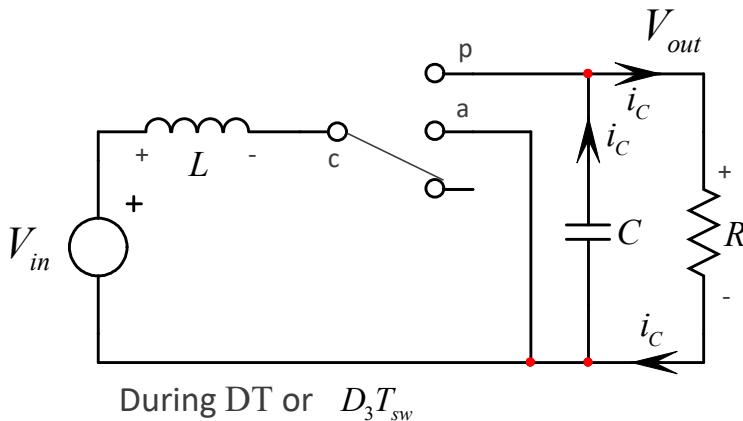
# Transfer Characteristic of the DCM Boost

- As the load current decreases, the converter enters discontinuous conduction mode
- The catch diode spontaneously blocks when the inductor current reaches 0 A



$$R_{critical} = \frac{2LF_{sw}}{D(1-D)^2}$$

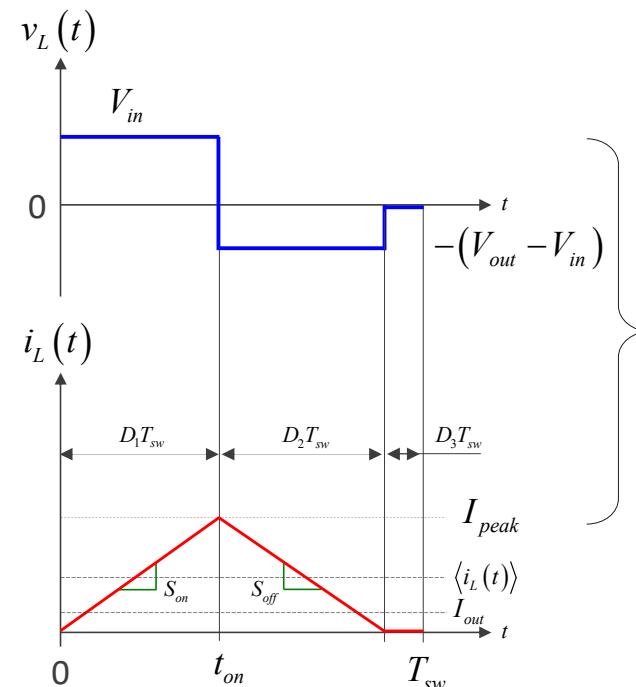$R < R_{critical} \rightarrow \text{CCM}$   
 $R = R_{critical} \rightarrow \text{BCM}$   
 $R > R_{critical} \rightarrow \text{DCM}$




$$M = \frac{1 + \sqrt{1 + \frac{2D_1^2}{\tau_L}}}{2}$$

- ✓ Depends on  $F_{sw}$
- ✓ Depends on  $R$

$$\tau_L = \frac{L}{RT_{sw}}$$
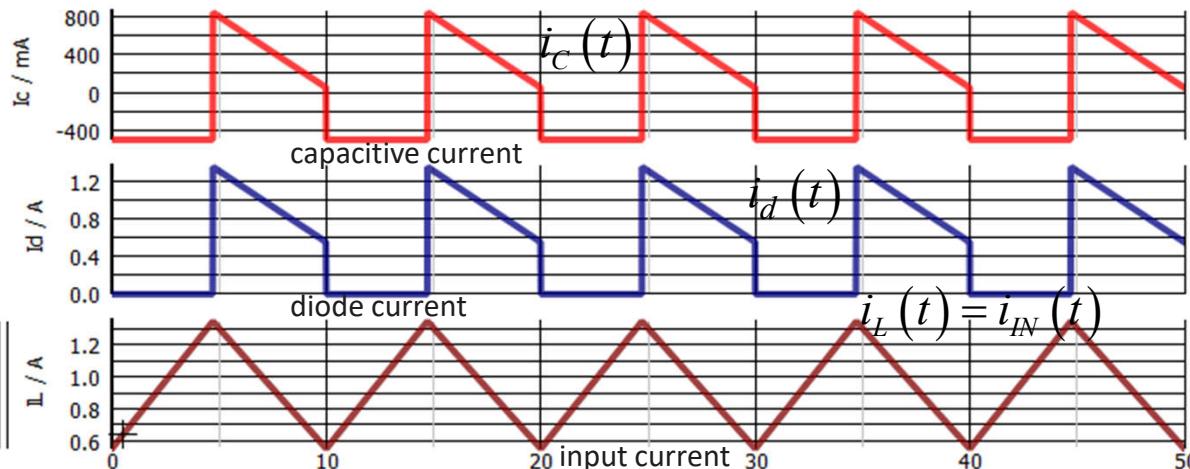
# Input and Output Currents

- It is important to know the nature of the circulating input and output currents
- The inductance located in the input naturally smooths current which is *non-pulsating*
- The output current is *pulsating* and highly discontinuous: high rms component





- The boost converter is quiet on the input and noisy on the output

- ✓ The output capacitor is highly pulsating and is of strong rms value
- ✓ The input current is very smooth and presents a good EMI signature
- ✓ The inductor current is a smooth triangular waveform
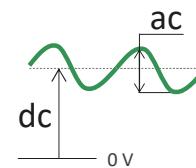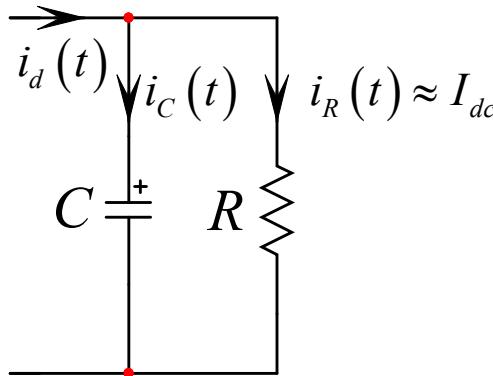
# Rms Current in the Output Capacitor


- The output current is highly discontinuous and stresses the output capacitor
- It is important to determine the worst-case rms current in this capacitor
- Make sure the selected type accepts this stress at the highest operating temperature



$$I_{rms} = \sqrt{I_{ac}^2 + I_{dc}^2}$$



$$I_{C,rms} = \sqrt{I_d^2 - I_{dc}^2}$$


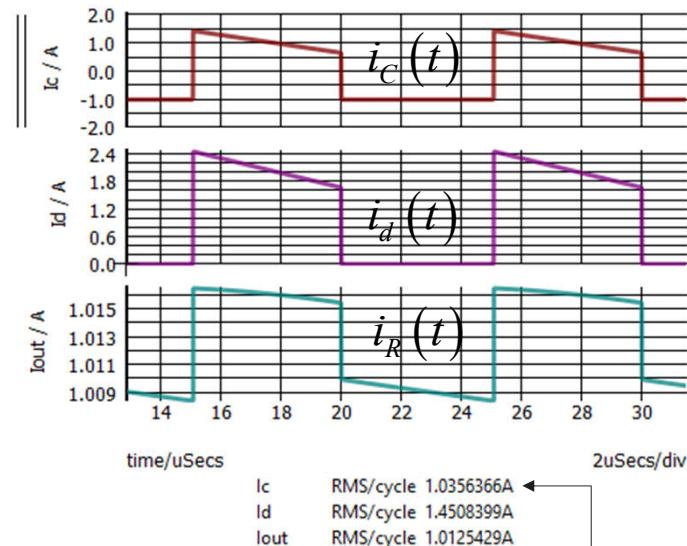


$$i_{C,rms} = \sqrt{1.45^2 - 1.021^2} = 1.03 \text{ A}$$



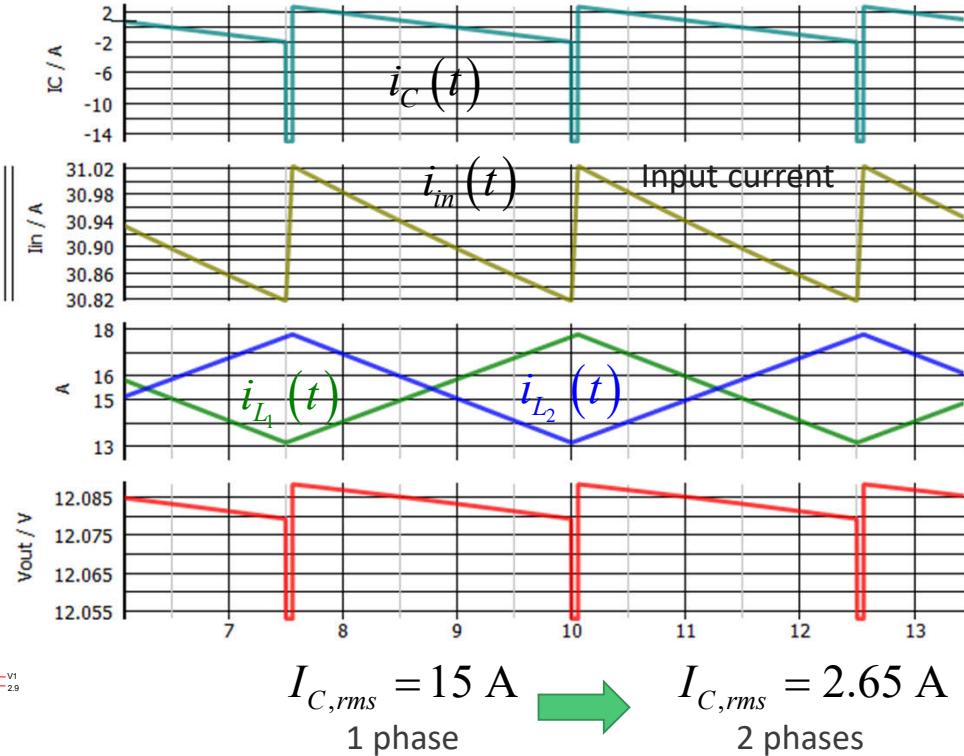
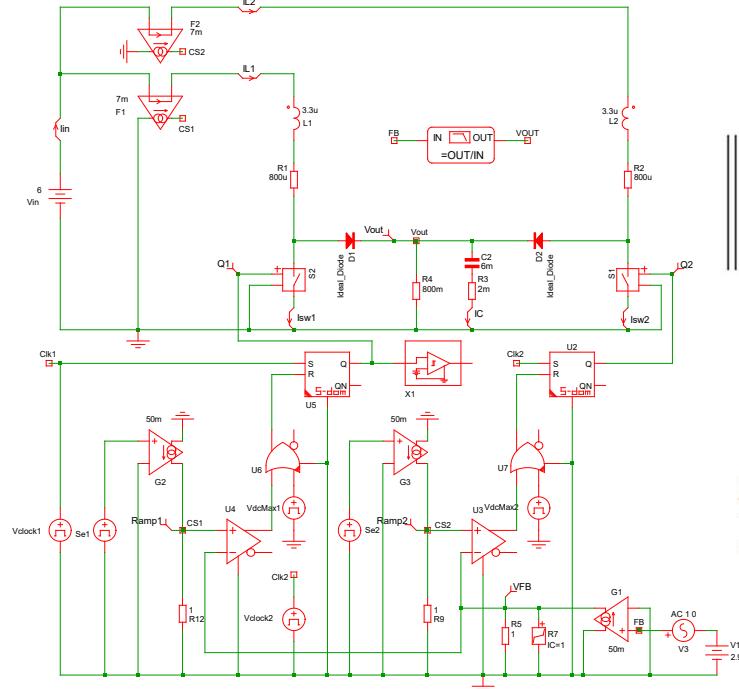
# Multiphase to Reduce Ripple Currents

- High-power types of boost converters impose a heavy rms burden to the capacitor
- Adding extra switching phases reduces the input and output ripple currents


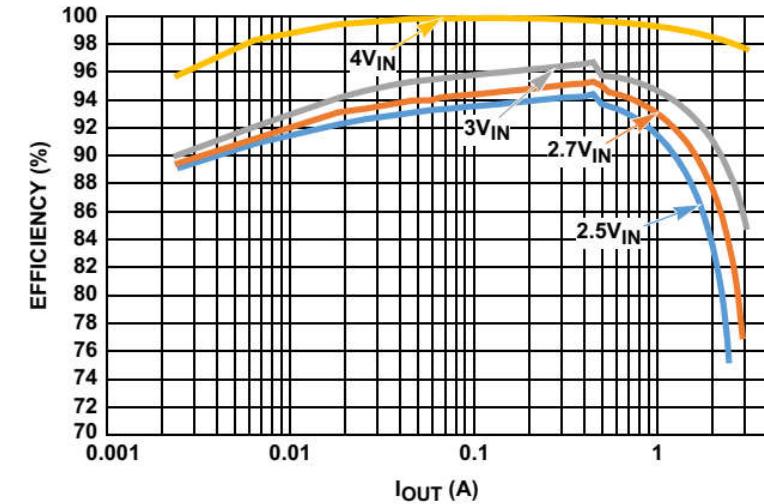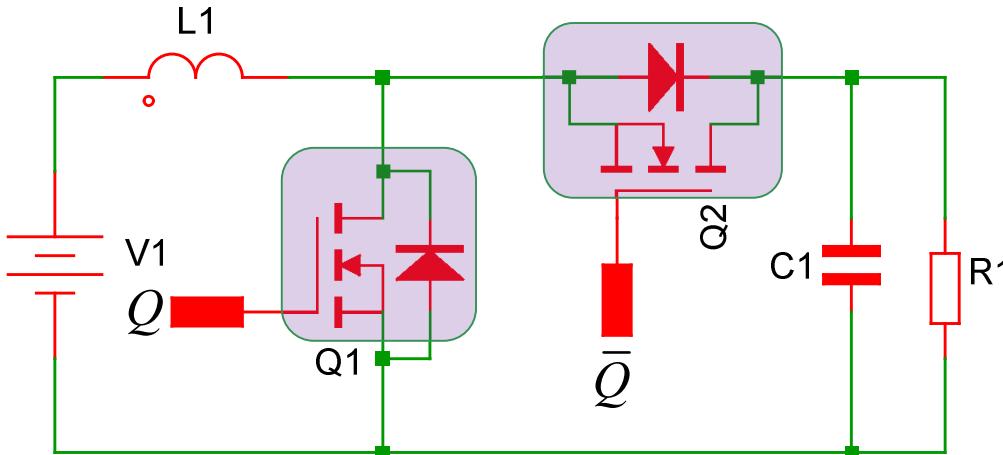
# Synchronous Rectification

- Efficiency depends on the difference between output and input voltages
- Synchronous rectification further helps improving performance at low  $V_{out}$





Typical curve for the ISL91133

- ✓ A second switch is added to short the catch diode
- ✓ Some dead-time is inserted between transitions to avoid shoot-through
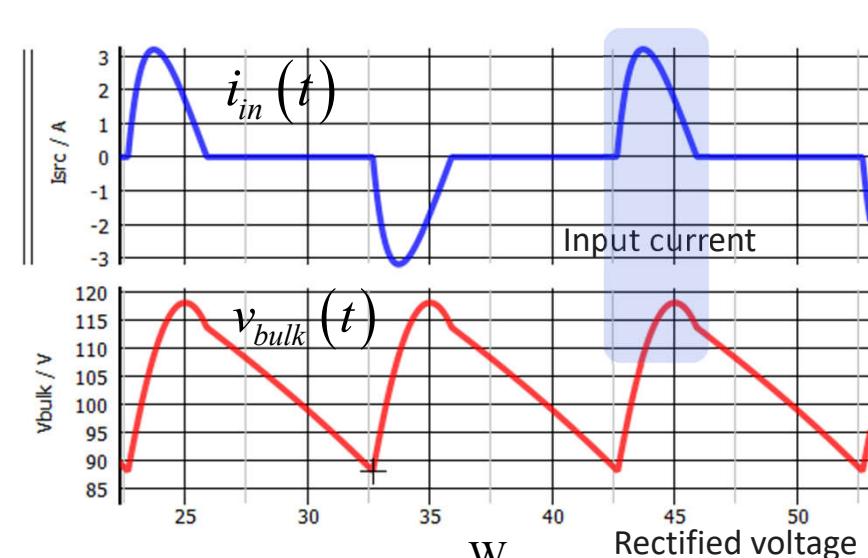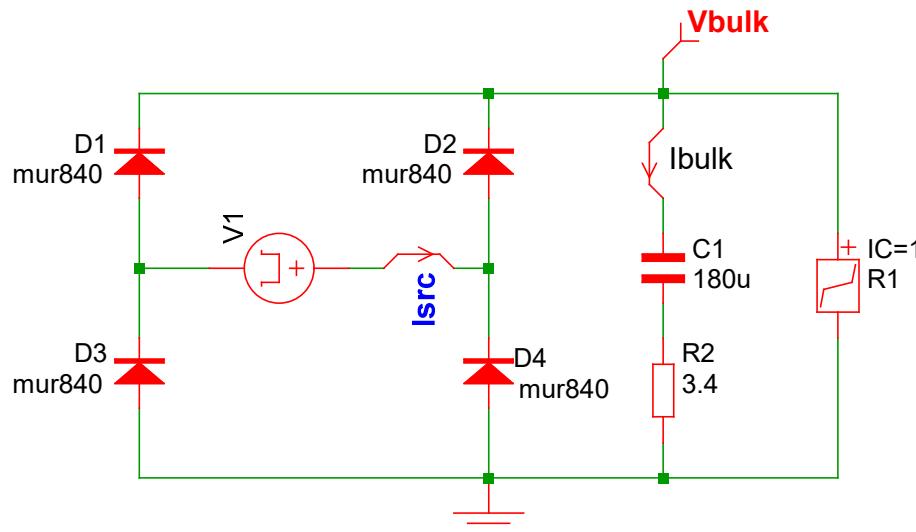
# Full-Wave Rectification

- A resistor supplied by the mains absorbs a sinusoidal current in phase with the voltage
- A full-wave rectifier connected to the mains absorbs a non-sinusoidal current
- ✓ International standards impose regulatory limits for a power greater than 75 W





- ❖ The capacitor refueling occurs only at the voltage peak  $\rightarrow PF = \frac{W}{V \cdot A} < 1$

PF: power factor
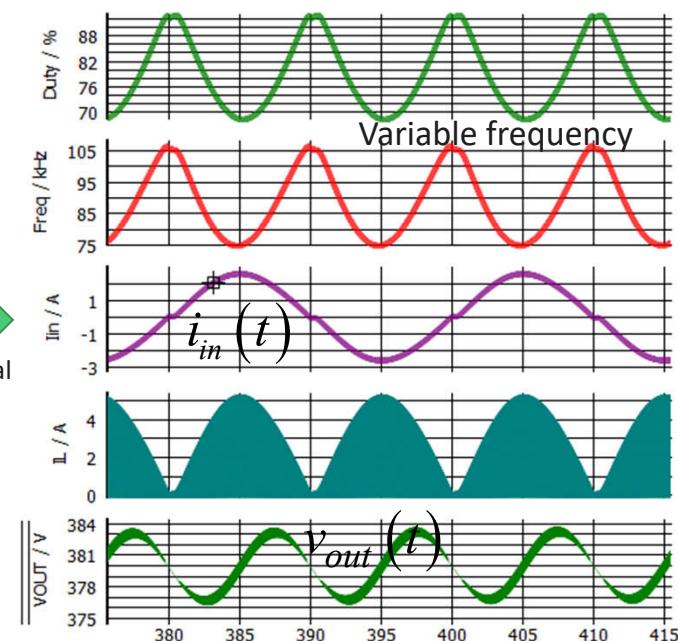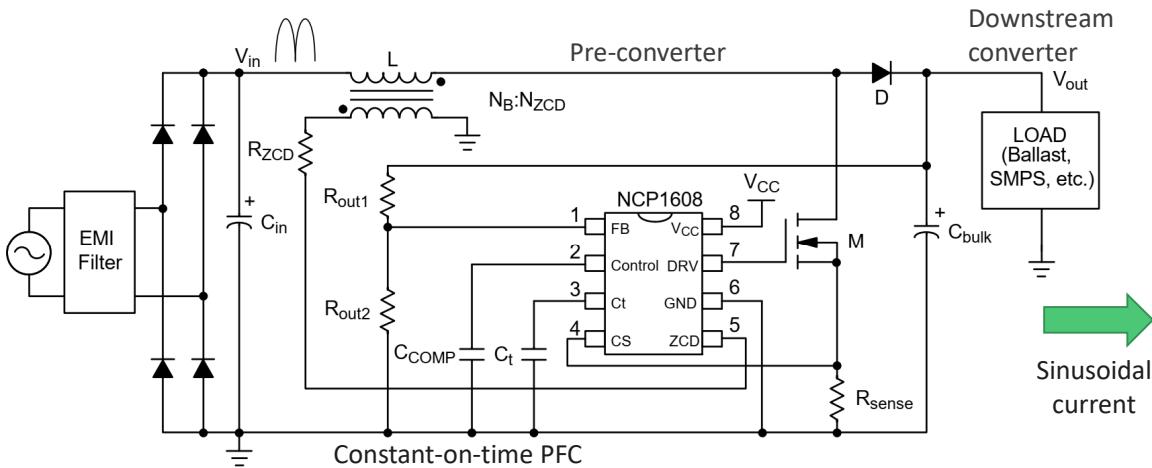
# Power Factor Correction

- A power factor corrector forces the absorption of a sinusoidal current
- The boost structure is the most popular converter for this application
- Low-power PFCs operate in BCM while high-power pre-converters run in CCM



- ❖ Output ripple limits crossover frequency



# Agenda

---

- Power Conversion Mechanisms
- Switching Cells and Control Schemes
- The Buck
- The Boost
- The Buck-Boost
- Introduction to Control Loop Design
- EMI Filter Interaction
- Introduction to Simulation

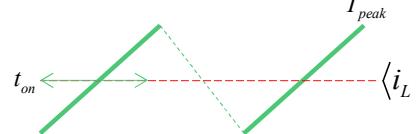
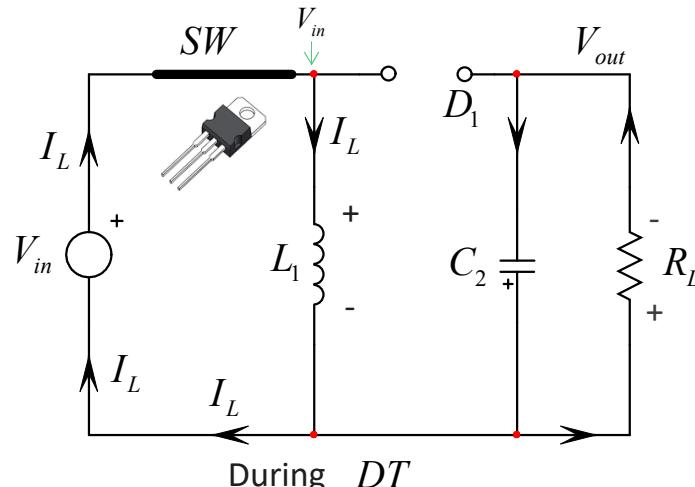
# The Buck-Boost Converter

- The buck-boost converter increases or decreases the output voltage
- The converter inverts the input and the delivered voltage is negative



$$S_{on} = \frac{V_{in}}{L_1}$$

$$T_{sw} = DT_{sw} + (1-D)T_{sw}$$



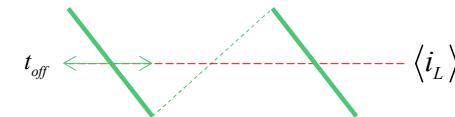
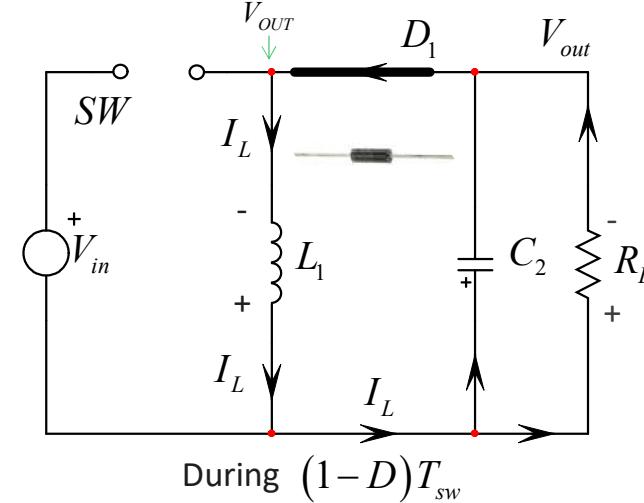


$$S_{off} = \frac{V_{out}}{L_1}$$

$V_{out}$  is negative
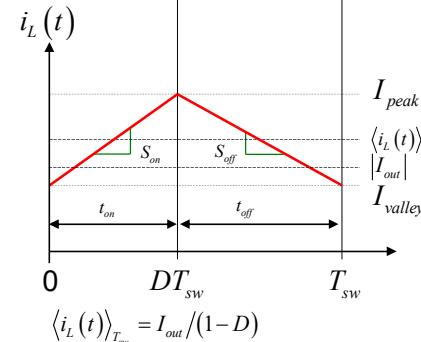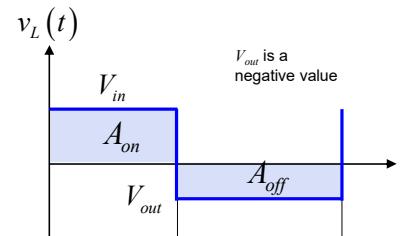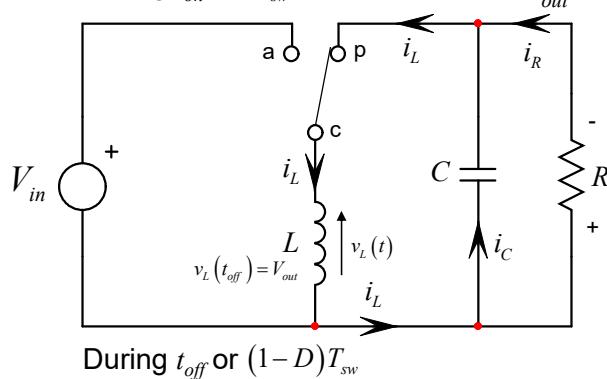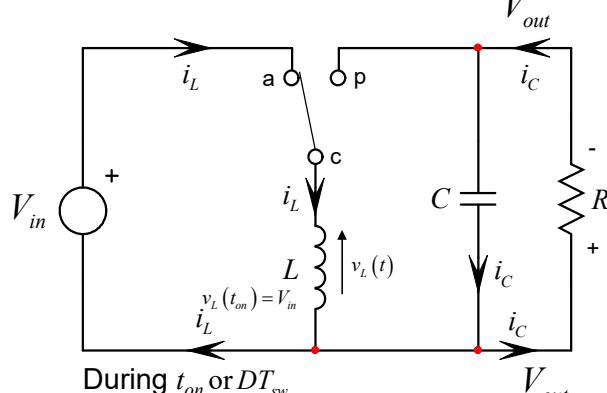
# Transfer Characteristic of the CCM Buck-Boost

- Consider the average inductor voltage to determine the dc transfer characteristic
- Express the volt-seconds of the inductor during the on- and off-times



V-s balance

$$\langle v_L(t) \rangle_{T_{sw}} = 0 \text{ V}$$

$\downarrow$

$$V_{in}DT_{sw} = -V_{out}(1-D)T_{sw}$$

$\downarrow$



$$V_{out} = -V_{in} \frac{D}{1-D}$$

$\downarrow$

$$M = -\frac{D}{1-D}$$

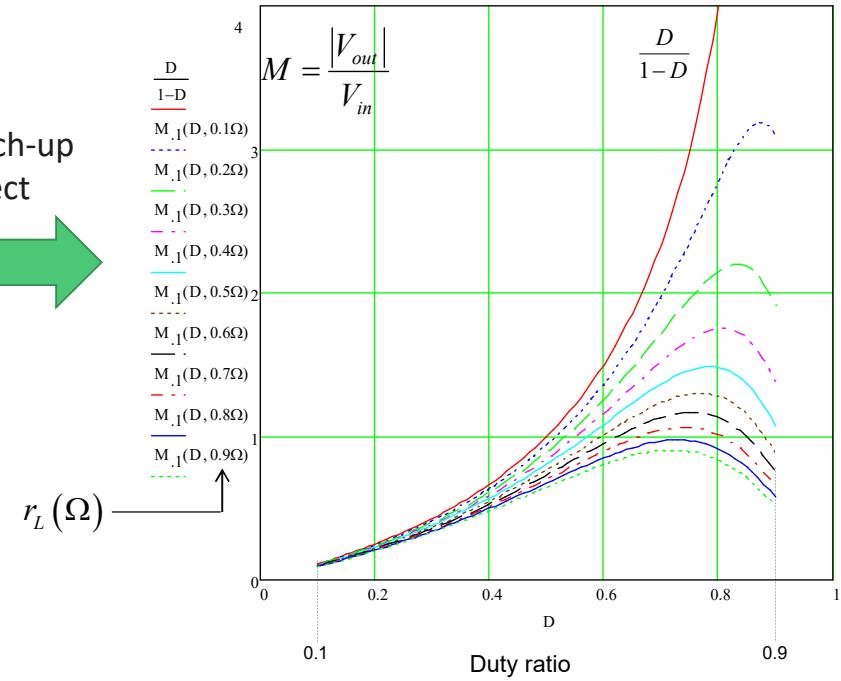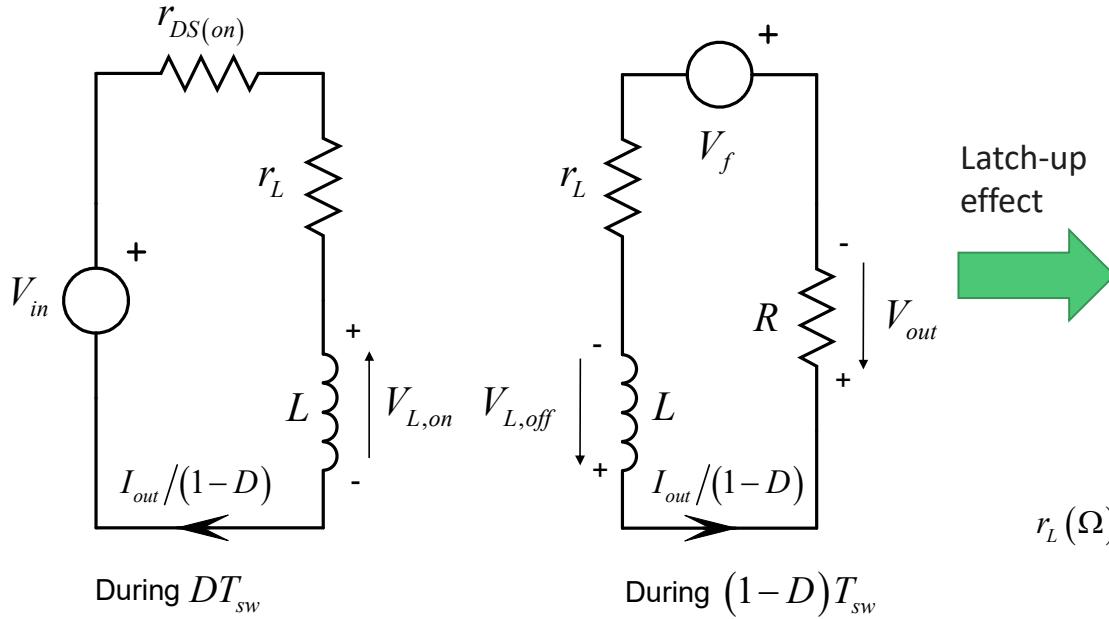
# A Finite Conversion Ratio

- Resistances in series limit the maximum peak current in the inductor
- The conversion ratio is thus limited as in the boost converter case


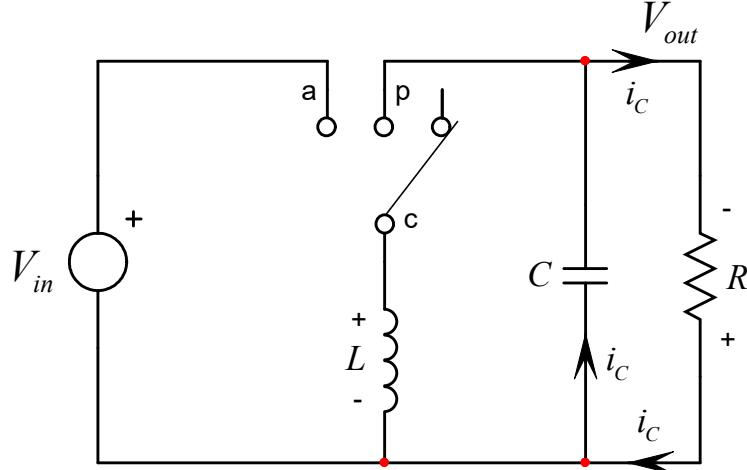
# Transfer Characteristic of the DCM Buck-Boost

- The converter enters the discontinuous conduction mode in light-load conditions
- Both switches are blocked and the capacitor alone feeds the load



During DT or  $D_3 T_{sw}$


$$R_{critical} = \frac{2LF_{sw}}{(1-D)^2}$$



$R < R_{critical} \rightarrow \text{CCM}$

$R = R_{critical} \rightarrow \text{BCM}$

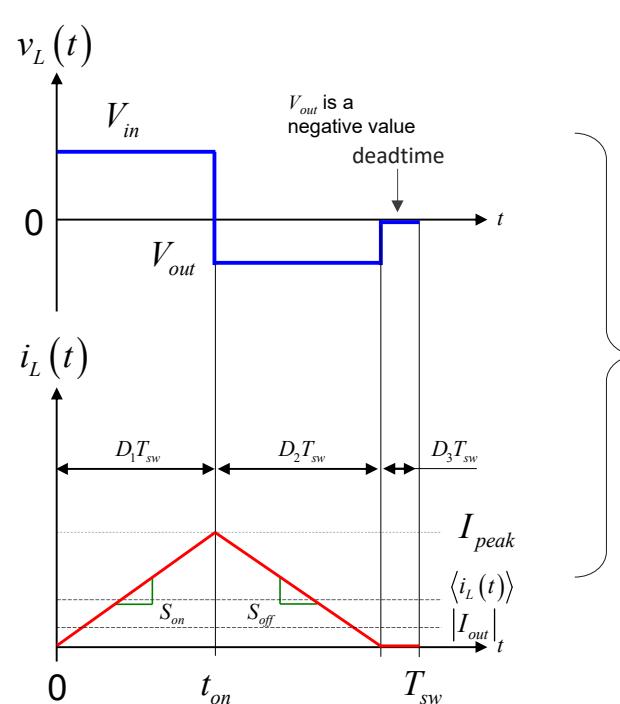$R > R_{critical} \rightarrow \text{DCM}$




$$M = -D_1 \sqrt{\frac{1}{2\tau_L}}$$

- ✓ Depends on  $F_{sw}$
- ✓ Depends on  $R$
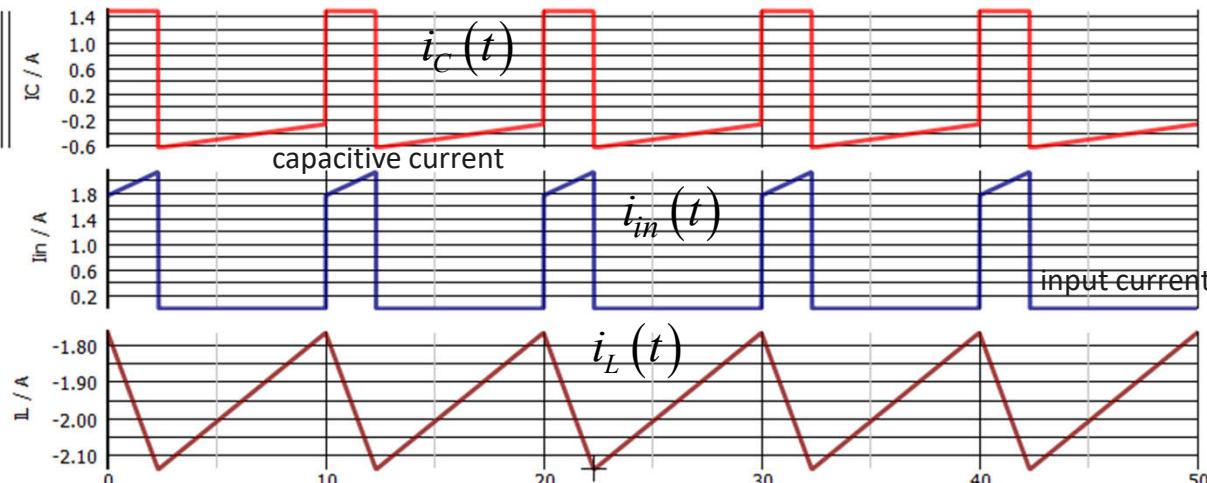
# Input and Output Currents

- The buck-boost is the worst of all basic switching cells
- The inductor is ground referenced and connects alternatively to the input or the output
- ✓ Input and output current are *pulsating* and highly discontinuous: high rms component





- ✓ The output capacitor is highly pulsating and is of strong rms value
- ✓ The input current is also pulsating implying a poor EMI signature
- ✓ The inductor current is a smooth triangular waveform

- The buck-boost converter is noisy on the input and noisy on the output

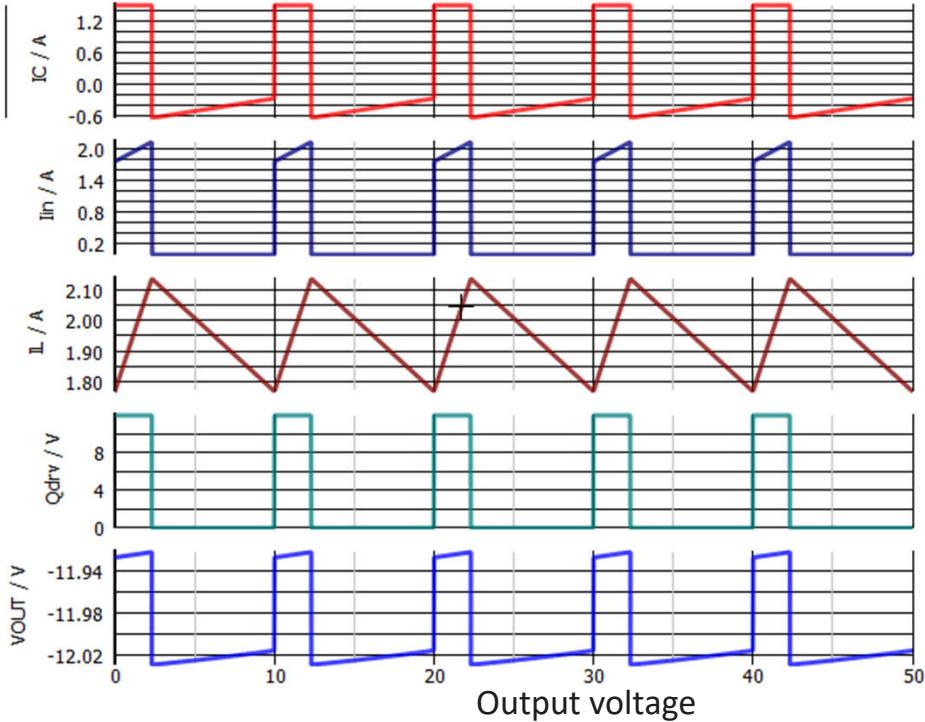
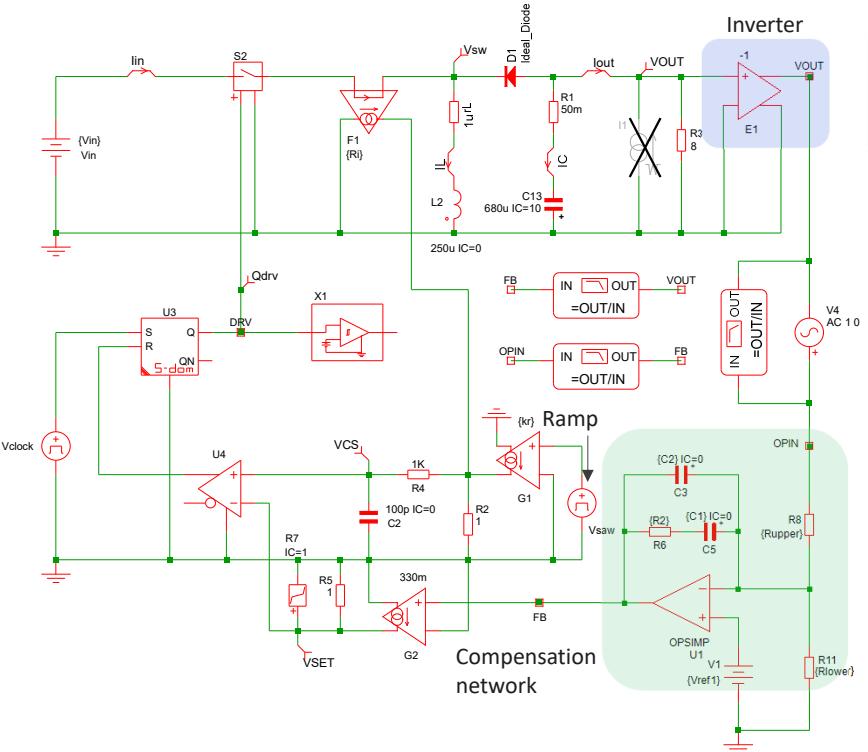
# Simulation of a Buck-Boost Converter

- The negative output requires an inversion for proper regulation
- This is a current-mode-controlled application featuring slope compensation




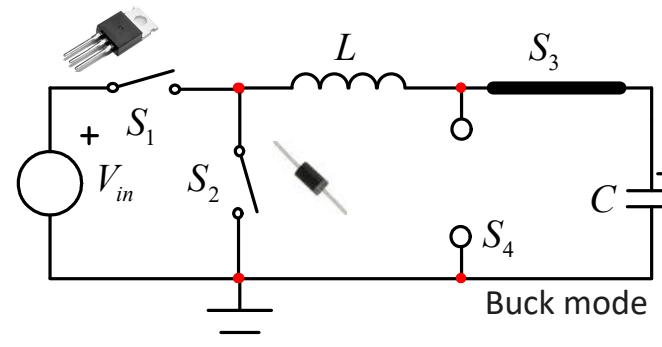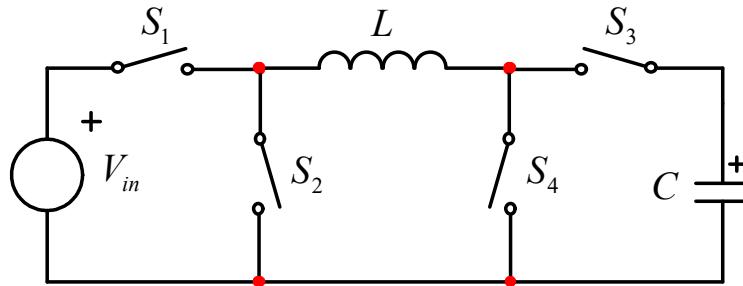
# Four-Switch Buck-Boost Version

- A 4-switch version operates in buck or boost and no longer inverts the output
- The control requires a more complicated control logic



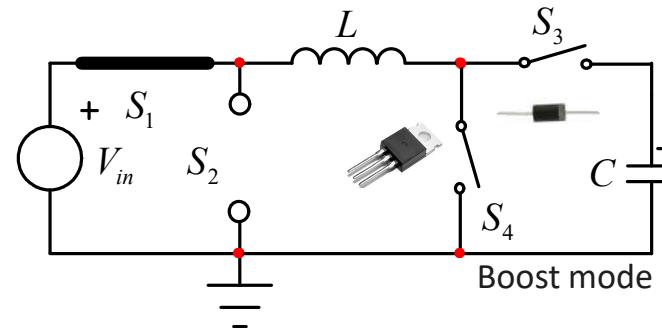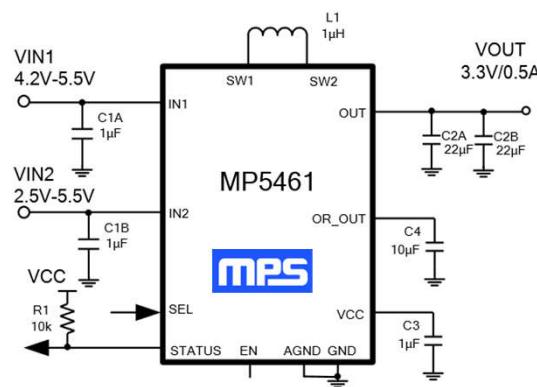
- ✓  $S_1$  and  $S_2$  are acting in buck mode
- ✓  $S_3$  and  $S_4$  are respectively on and off.



- ✓  $S_1$  and  $S_2$  are respectively on and off.
- ✓  $S_3$  and  $S_4$  are actuated in boost mode.
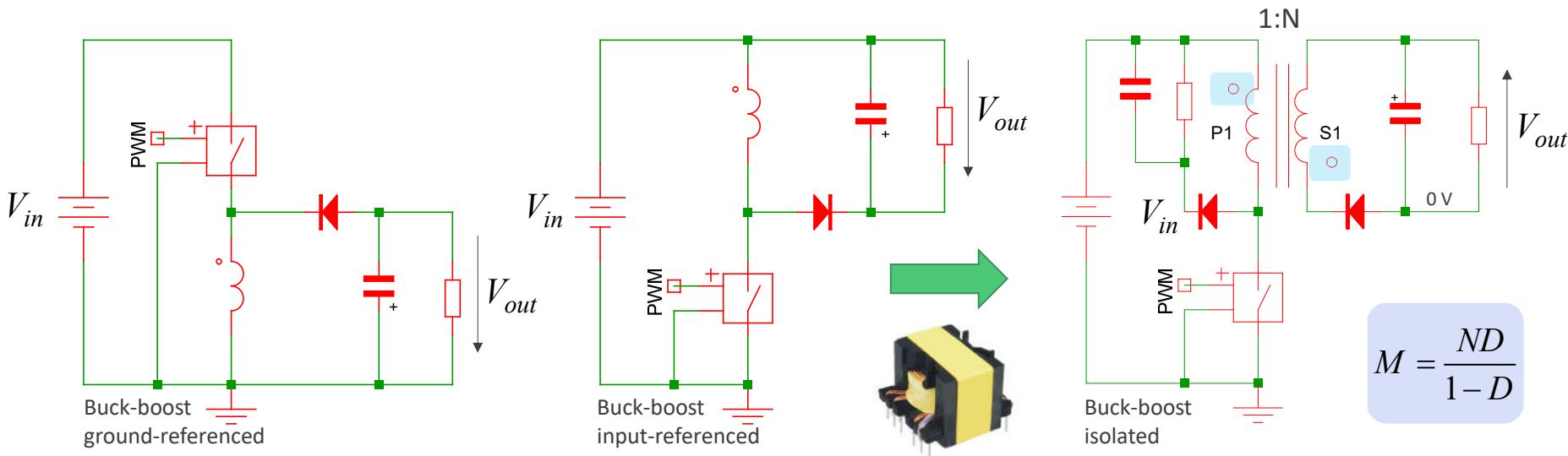
# The Flyback Converter

- Adding a transformer brings galvanic isolation: flyback converter
- The converter can now deliver positive or negative levels, increase or decrease  $V_{in}$



- The flyback converter can be identified with its winding dots located in opposite ends
- ✓ A clamping network is necessary to protect the power switch


# Agenda

---


- Power Conversion Mechanisms
- Switching Cells and Control Schemes
- The Buck
- The Boost
- The Buck-Boost
- Introduction to Control Loop Design
- EMI Filter Interaction
- Introduction to Simulation
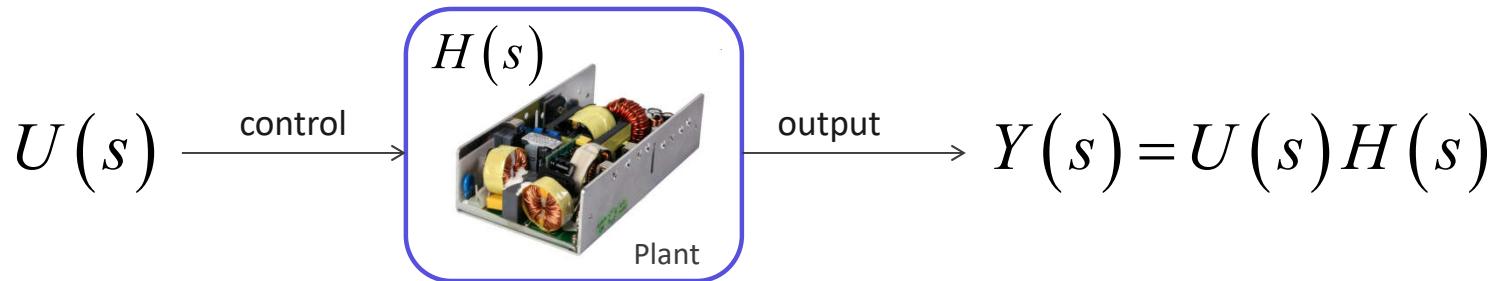
# What is a Control System?

- An open-loop system links an output with a control variable




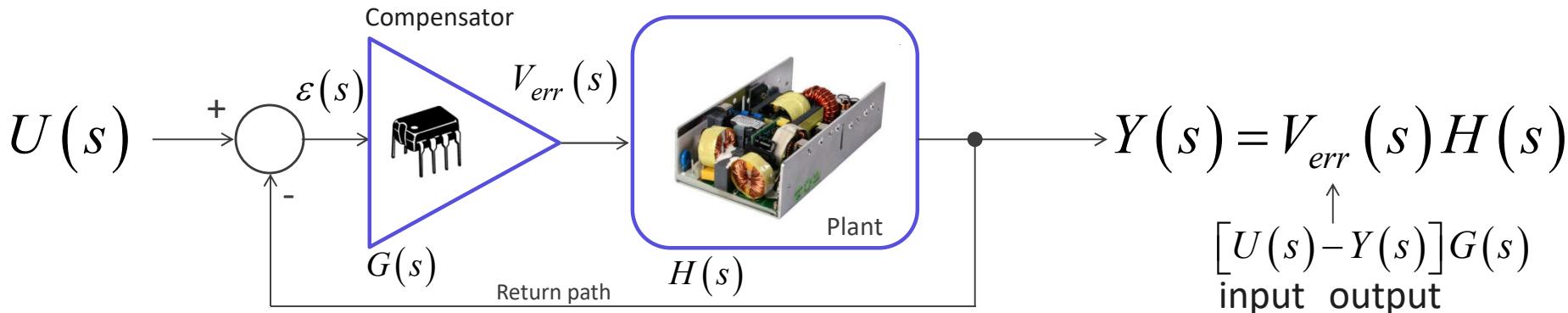- A control system observes the output and minimizes the error by closing the loop


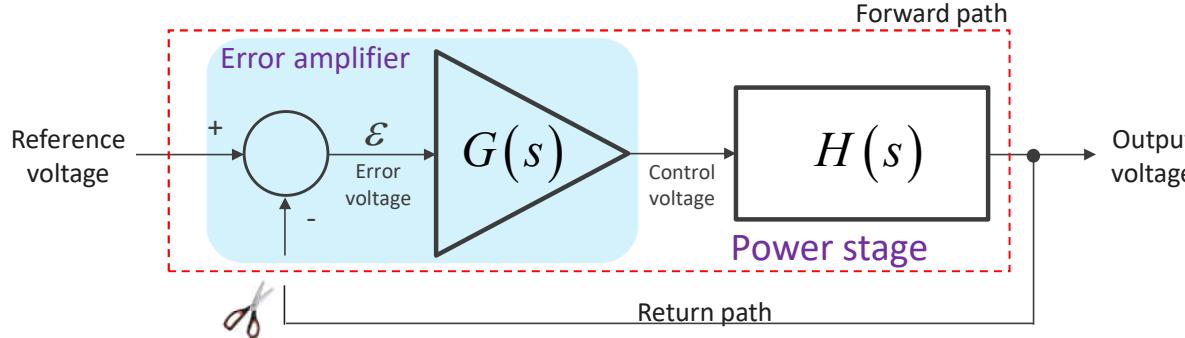
# What is Loop Gain?

- The error amplifier and the power stage define the system *loop gain*
- Its value affects the stability and robustness or susceptibility of the circuit



- The loop gain designated as  $T$  is defined as  $T(s) = G(s)H(s)$



$$\frac{V_{out}(s)}{V_{ref}(s)} = \frac{H(s)G(s)}{1 + H(s)G(s)} = \frac{T(s)}{1 + T(s)}$$

If  $T \gg 1$   $V_{out}(s) = V_{ref}(s)$

$$1 + T(s) = 0 \rightarrow |T(s)| = 1 \text{ or } 0 \text{ dB} \quad \checkmark \text{ Nyquist stability criterion}$$
$$\angle T(s) = -180^\circ$$
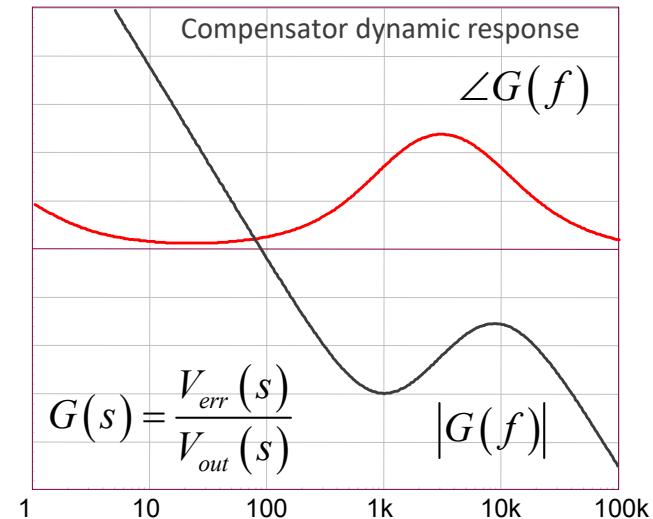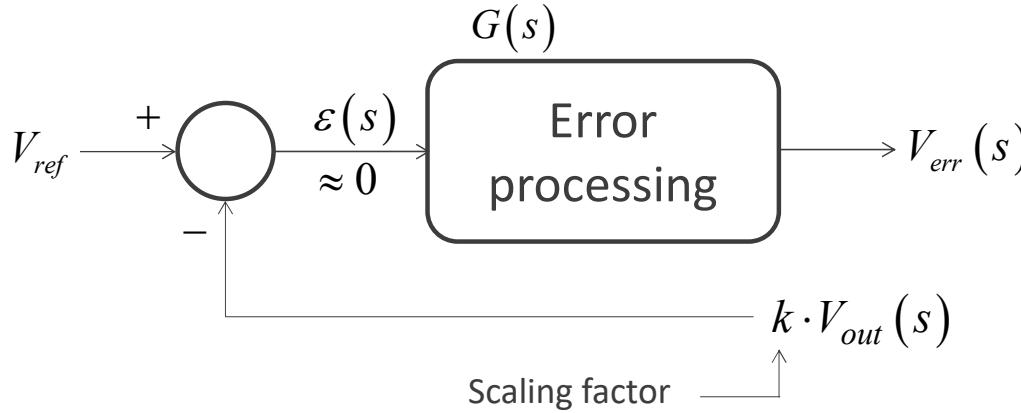
# Shaping the Loop with the Compensator


- The compensator builds the error variable and ensures stability
  - Insert poles and zeros to create the compensation strategy
  - Choose how to cross over at  $f_c$  with phase and gain margins



- The block amplifies and shapes the error  $\varepsilon$  between  $V_{ref}$  and  $V_{out}$
- ✓ Minimize the error between the setpoint and the output


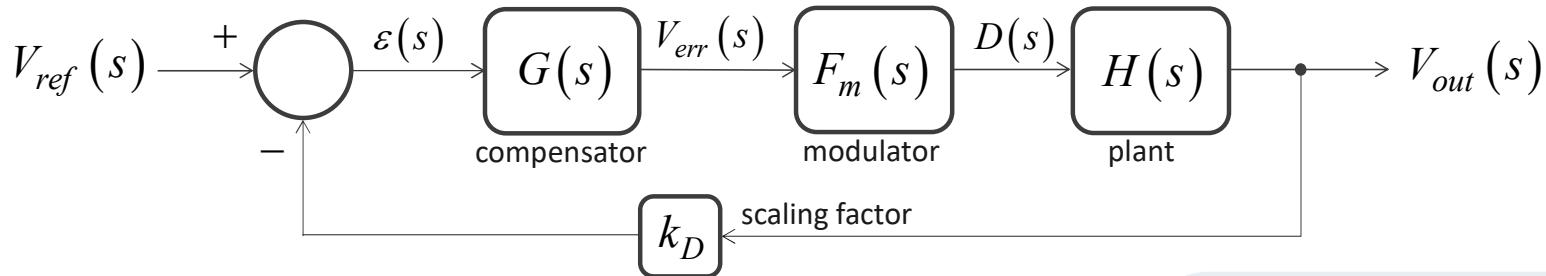
# Building the Compensator – the Analogue Way

- Associate active and passive components to form the compensation chain




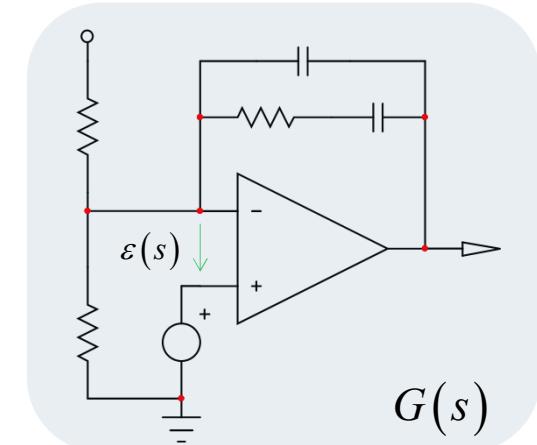
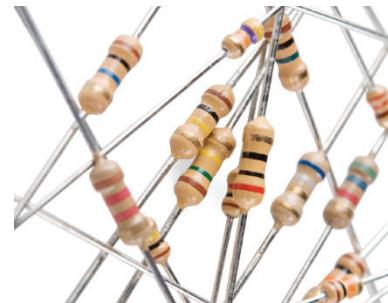
1. Select poles/zeroes placement
2. Calculate components values
3. Solder resistors and capacitors

→ Change in strategy requires new components values


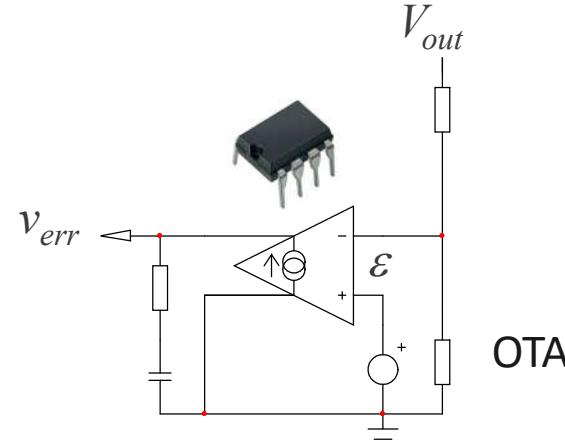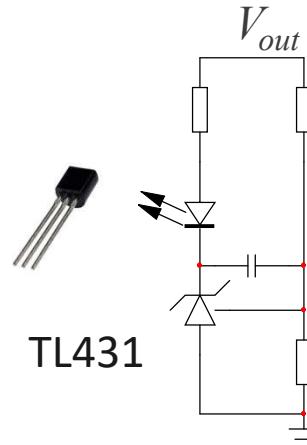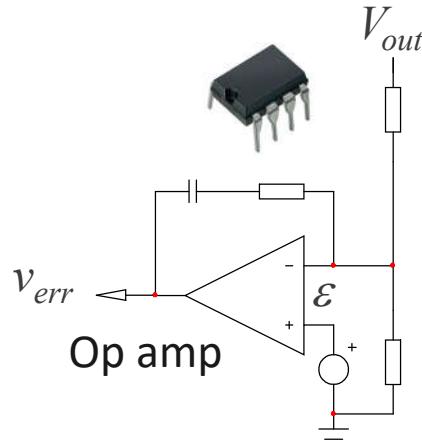
# How do you Build an Analogue Compensator?

- A compensator can be a passive or active filter shaped for a specific response




- ✓ Passive components suffer drawbacks:

  1. Tolerance, aging
  2. Sensitivity to temperature, humidity



- ✓ Active components are not perfect!

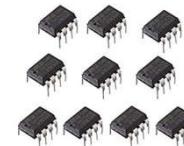
  1. Open-loop gain, bias requirements
  2. Limited in bandwidth, slew-rate
  3. Temperature drift



OTA: operational transconductance amplifier
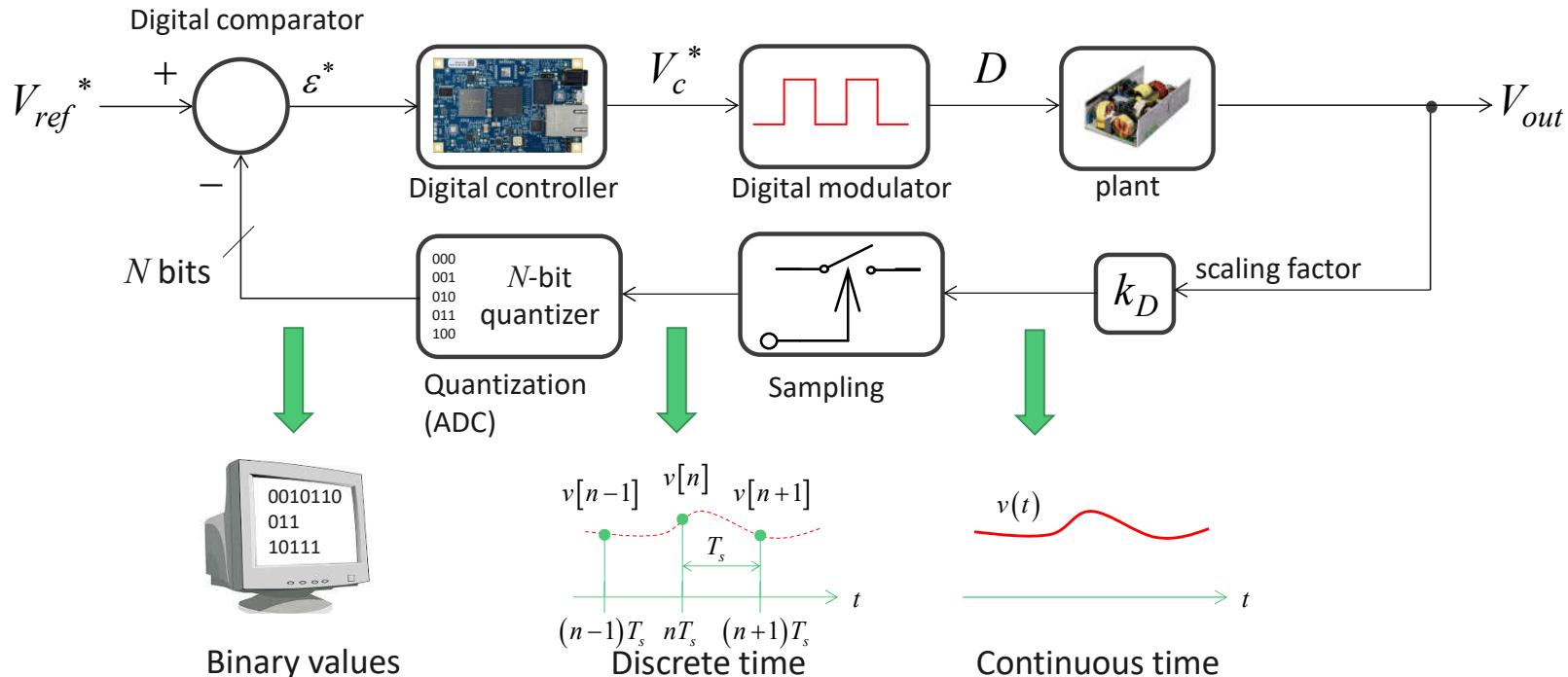
# Building the Compensator – the Digital Way


- A digitally-controlled system mixes sampled and continuous-time data




\* designates a discrete variable
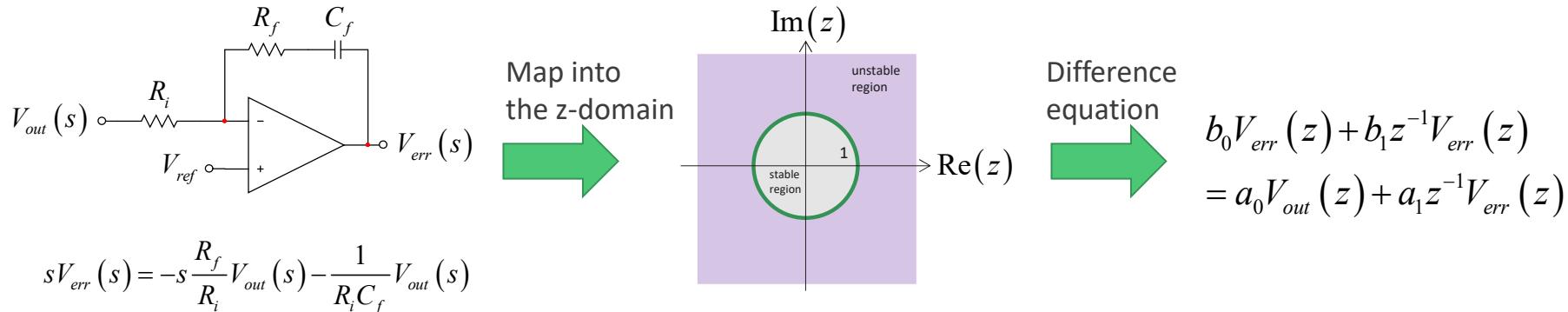
# How do you Build a Digital Compensator?

- You can start from a continuous-time transfer function expressed in  $s$



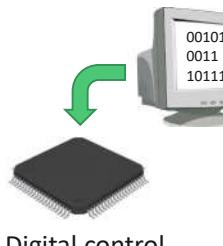- Code the filter equation with a micro-controller or hard-wire it in a FPGA



```

1 import PID
2 import time
3 import os.path
4
5 from OmegaExpansion import AdcExp
6 from OmegaExpansion import pwmExp
7
8 pwmExp.setVerbosity(-1)
9 pwmExp.driverInit()
10 adc = AdcExp.AdcExp()
11
12 targetT = 35
13 P = 10
14 I = 1
15 D = 1

```

- ✓ No tolerance or age issues
- ✓ Flexibility and optimization
- ✓ On-the-fly poles-zeroes changes
- ❖ More complex to analyze
- ❖ Warping occurs during mapping
- ❖ Lower crossover systems

Learning  
curve




# Why do we need to Close the Loop?

- You need to compensate the power stage deficiencies to obtain:

- Speed
- Precision
- Robustness




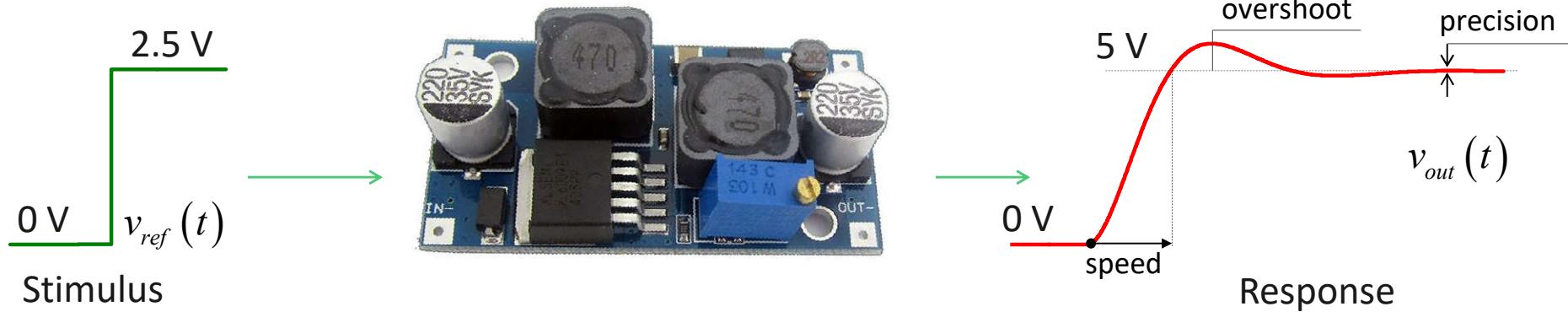
- ✓ High bandwidth
- ✓ Large dc gain
- ✓ High gain below  $f_c$



What compensation strategy?

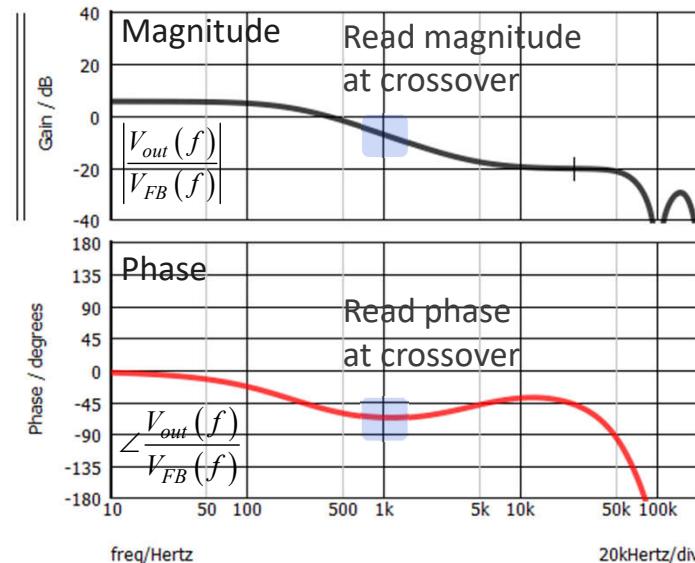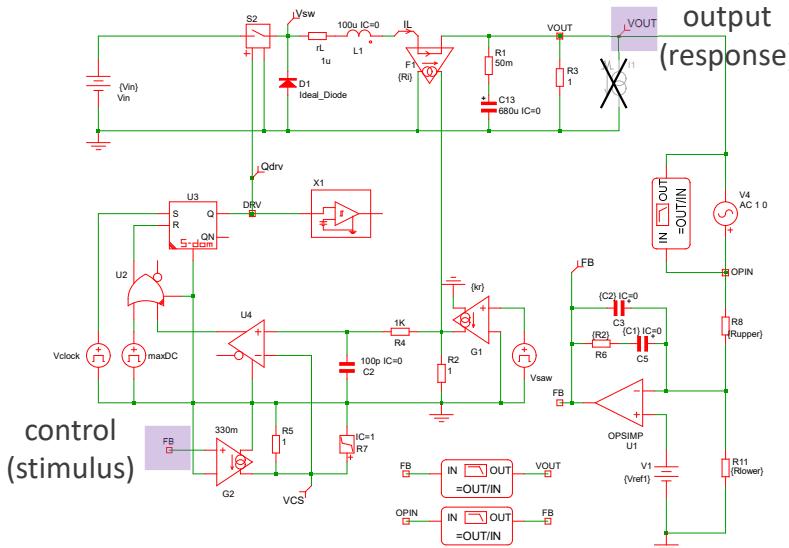
# Power Stage Transfer Function

- The control-to-output transfer function is the starting point:
- ✓ Use a frequency-response analyzer (FRA) to extract it
- ✓ Run a simulation with an averaged model to obtain a Bode plot
- ✓ Determine the transfer function analytically with small-signal analysis



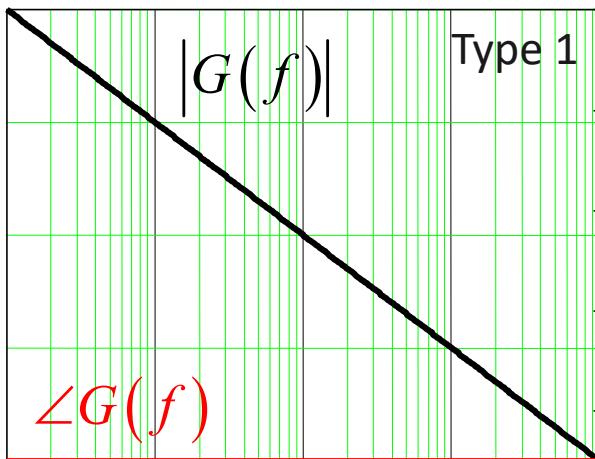
# Compensator Types


- Poles, zeroes and gain are your tools to shape the compensator response
- ✓ Phase margin depends on the wanted transient response
- ✓ Crossover depends on the expected reaction speed



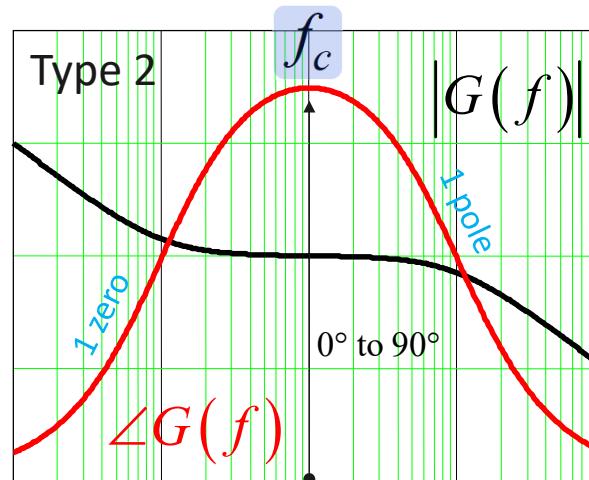0° phase boost  
1 pole at the origin only




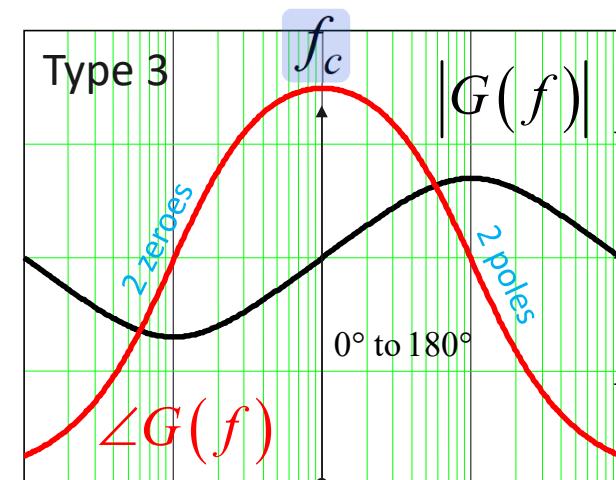
Up to 90° phase boost  
1 pole at the origin  
1 zero and 1 pole



Up to 180° phase boost  
1 pole at the origin  
2 zeroes and 2 poles
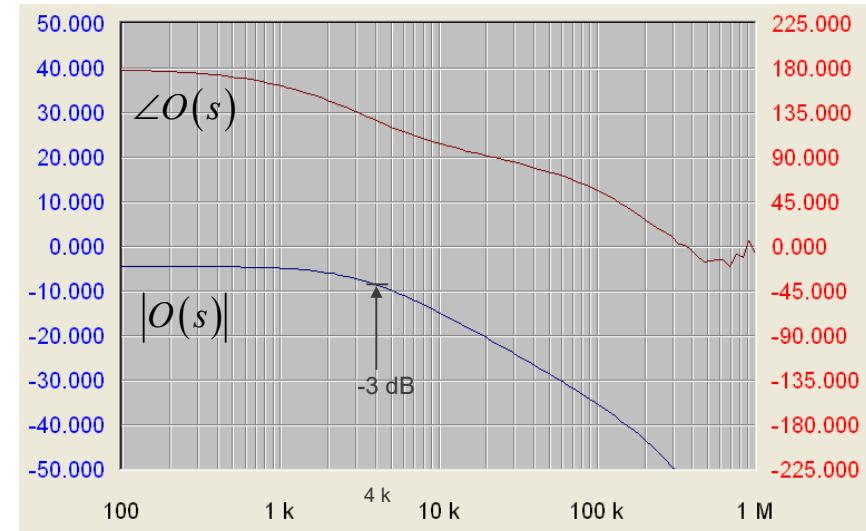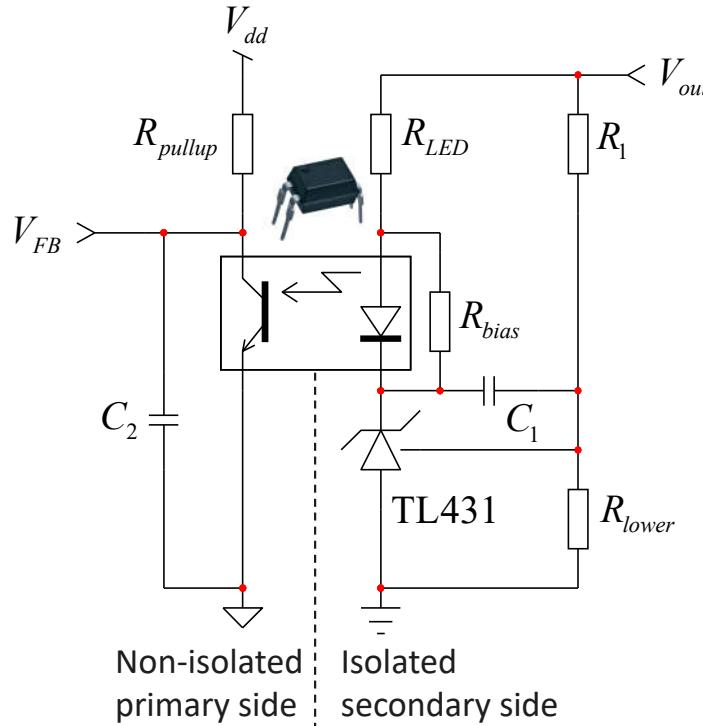
# Isolated Feedback



- An optocoupler brings the isolated output voltage image to the primary side
- This component degrades the compensator response and must be characterized



- The optocoupler features a low-frequency pole
- ✓ Characterize it carefully
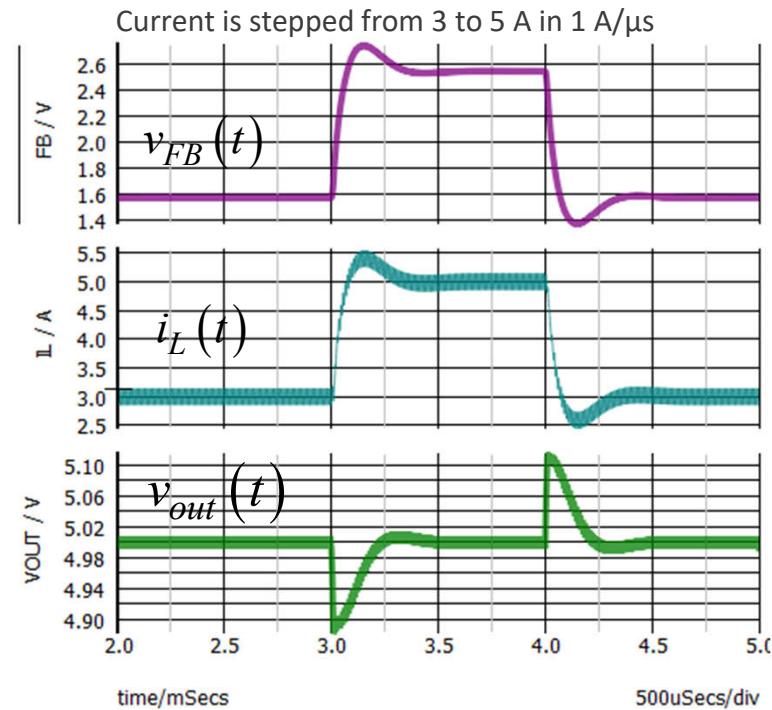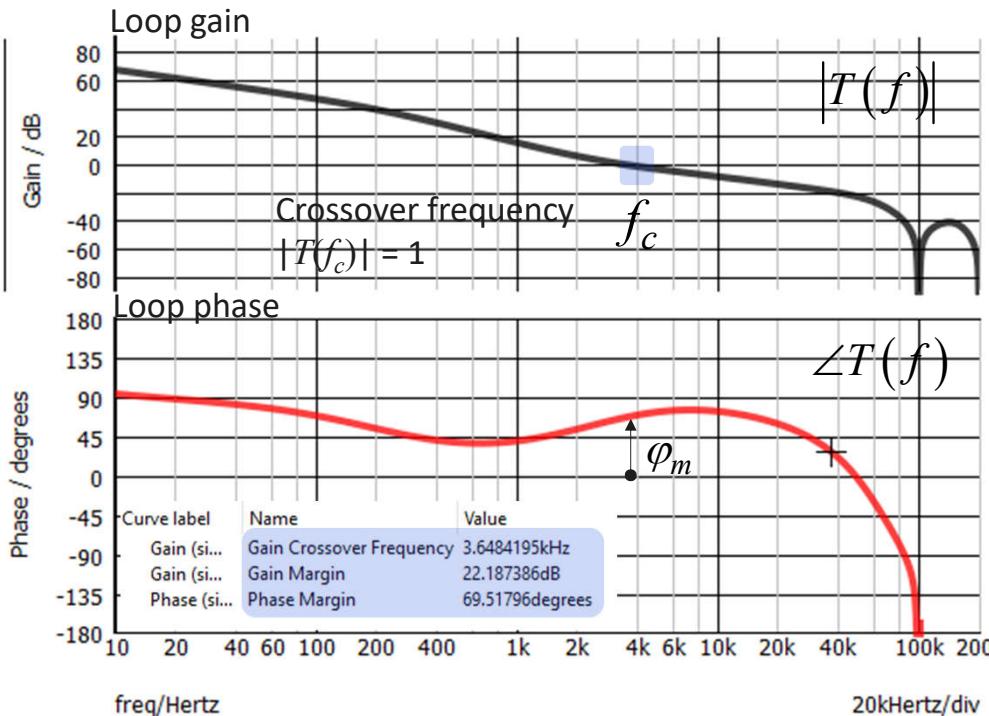
# Compensated Converter

- Check the loop gain and make sure phase and gain margins are within safe limits
- A transient step will tell you if the undershoot meets the specs




# Agenda

---

- Power Conversion Mechanisms
- Switching Cells and Control Schemes
- The Buck
- The Boost
- The Buck-Boost
- Introduction to Control Loop Design
- EMI Filter Interaction
- Introduction to Simulation
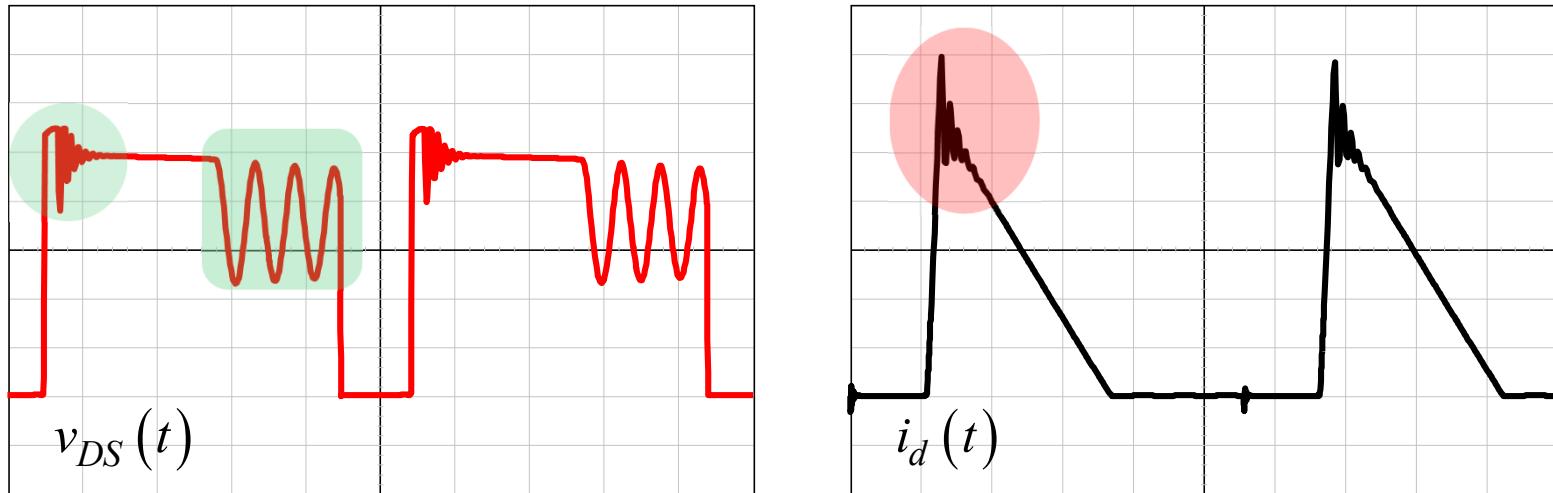
# A Noise Source


- A switching converter is a noise generator in essence
- ✓ Abrupt voltage changes impose circulating currents in parasitic capacitors
- ✓ Rapid current changes excite parasitic networks and generate ringing




→ High-current loops are naturally radiating noise and must be treated
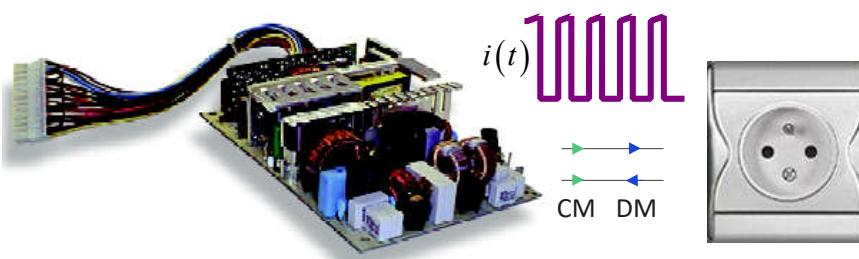
# Radiated or Conducted?

- Noise can be injected in the supply cables and return to the source
- ✓ This is so-called *conducted* parasitic noise
- Noise is coupled in the air through various mechanisms and disturb equipment
- ✓ In this case, we talk about *radiated* noise




Conducted noise  
150 kHz – 30 MHz

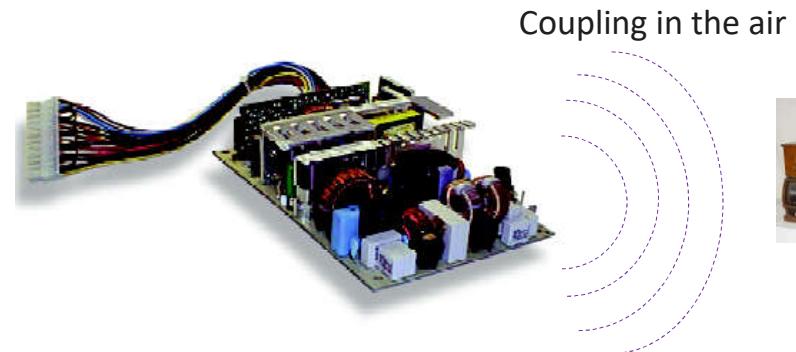


Radiated noise  
30 MHz – 1 GHz

# The Importance of the Loops

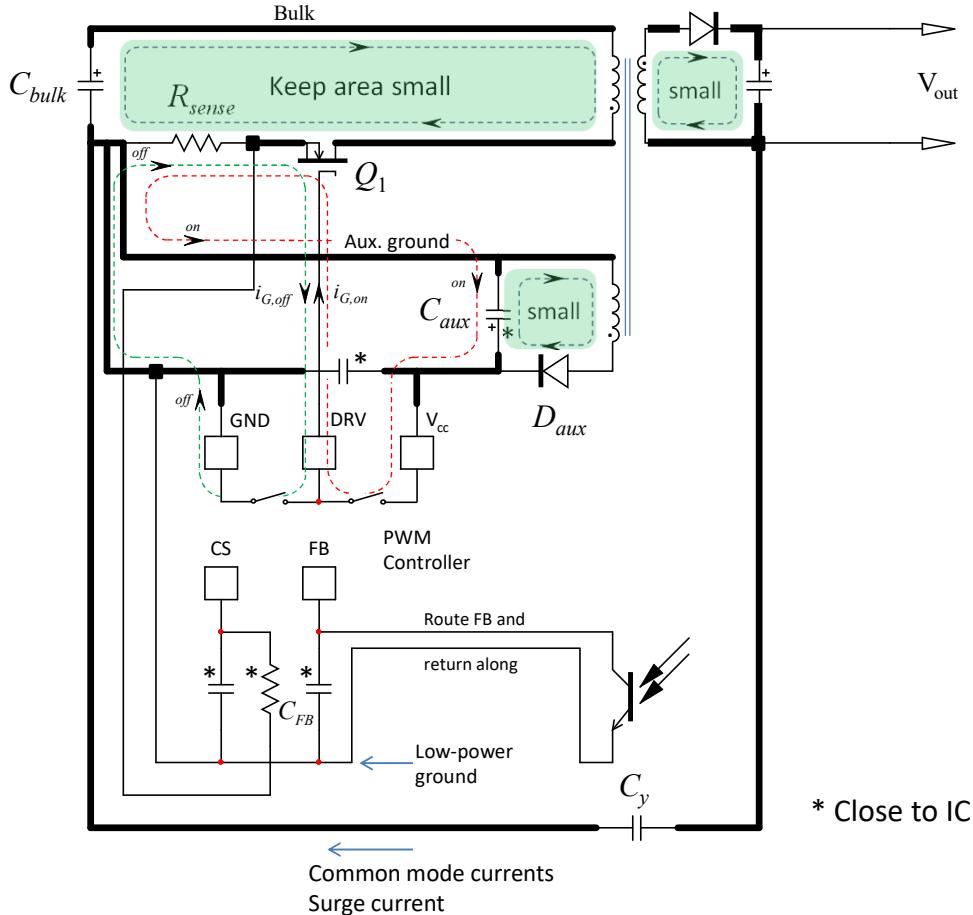


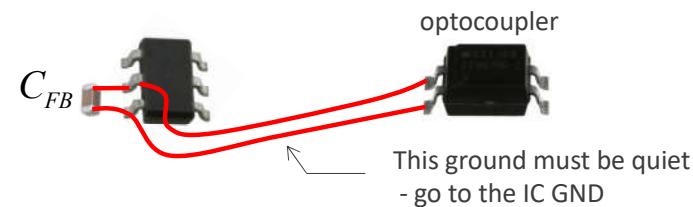- ✓ Identify the high-current switching paths and keep connections short
- ✓ Reduce the area enclosed by the circulating currents to minimize radiated noise
- ✓ Pay attention to the routing and how you select your return grounds
- ✓ Decoupling components must be located closely to the controller
- ✓ Star-cabling around the bulk capacitor is recommended for surge performance



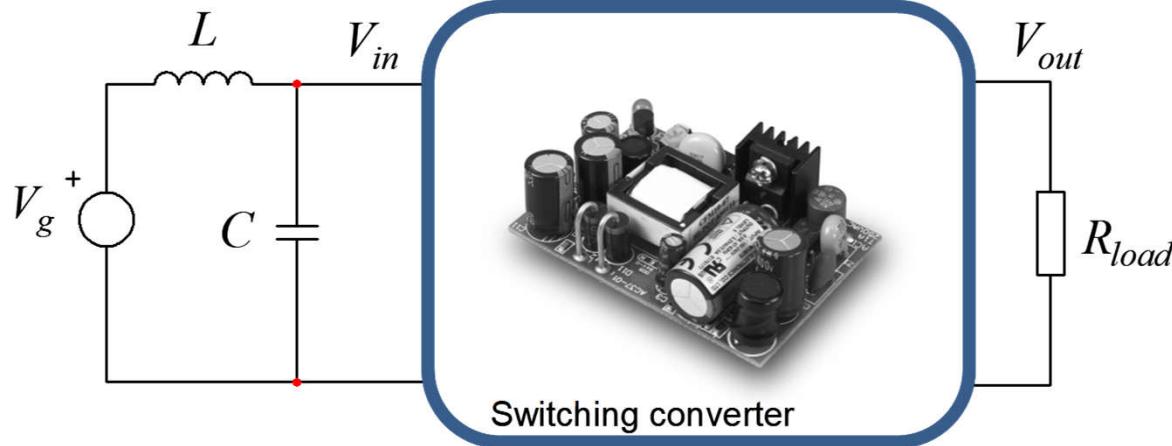
# Filtering the Conducted Noise

- A  $LC$  filter is selected to block high-frequency emissions back to the source
- The attenuation is calculated depending on the current to be filtered



Assume a 50-dB  
attenuation at 100 kHz
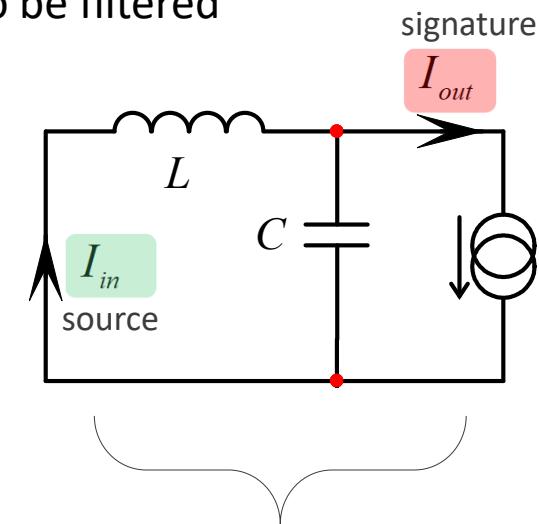
$$\rightarrow f_0 = \sqrt{A_{filter}} \cdot f_{SW} = \sqrt{3m} \times 100k \approx 17 \text{ kHz}$$




$$\frac{I_{in}}{I_{out}} \approx \left( \frac{\omega_0}{\omega} \right)^2$$
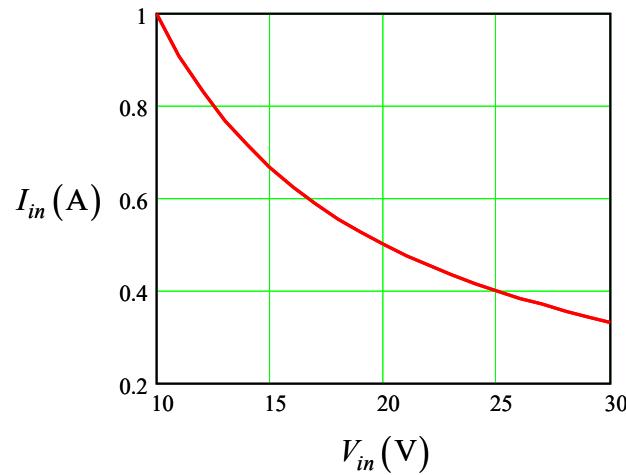
# Watch for the Interaction with the Filter

- The incremental input resistance of a switching converter is negative
- When loading an  $LC$  filter, deleterious interaction is likely to occur
-  Filter damping is an absolute necessity to stay away from troubles


$$\begin{aligned} P_{out} &= P_{in} \\ \downarrow \\ I_{in}V_{in} &= I_{out}V_{out} \\ \downarrow \\ I_{in}(V_{in}) &= \frac{P_{out}}{V_{in}} \end{aligned}$$



$$\frac{dI_{in}(V_{in})}{dV_{in}} = \frac{d\left(\frac{P_{out}}{V_{in}}\right)}{dV_{in}} = -\frac{P_{out}}{V_{in}^2}$$

The incremental input resistance is negative

$$R_{in} = -\frac{V_{in}^2}{P_{out}}$$

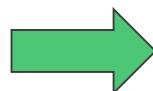 Negative incremental resistance occurs because of closed-loop operation



# A Negative Resistance Oscillator

- A negative load for the  $LC$  filter can compensate insertion losses
- Damped or sustained oscillations occur depending on resulting damping

$$H(s) = H_0 \frac{1 + s/\omega_z}{\frac{s^2}{\omega_0^2} + \frac{s}{\omega_0 Q} + 1} \quad Q = \frac{1}{2\zeta}$$



If ohmic losses are gone, the damping ratio is zero,  $Q$  is infinite.

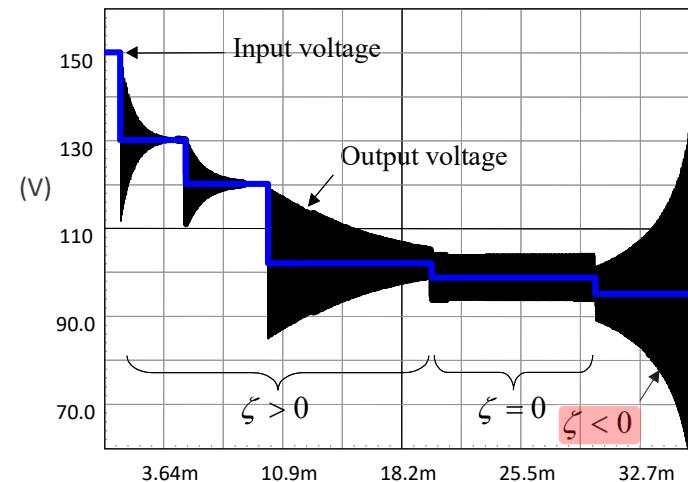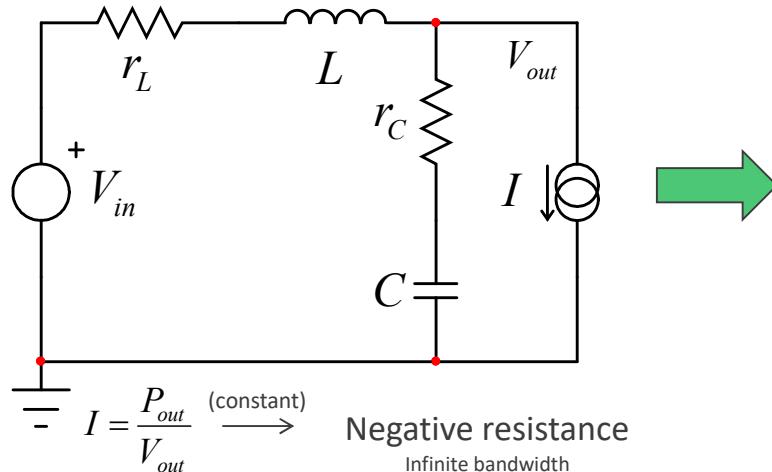- ✓ The poles can jump in the right half-plane and instability occurs!


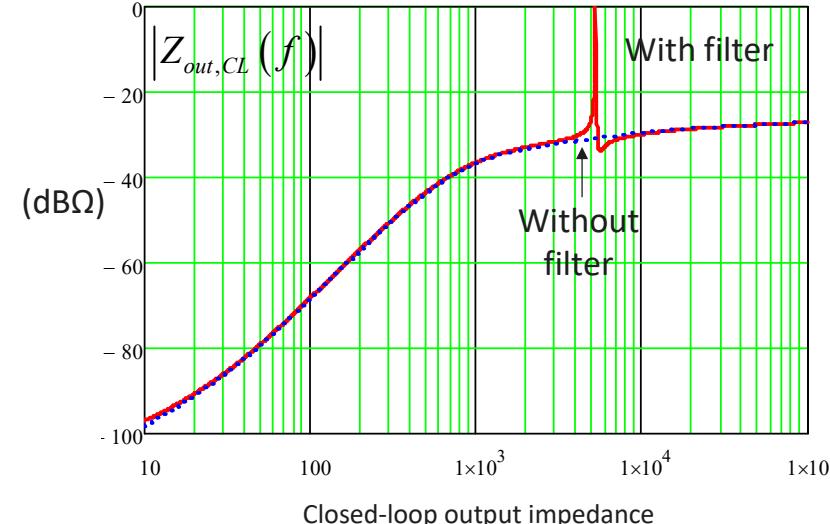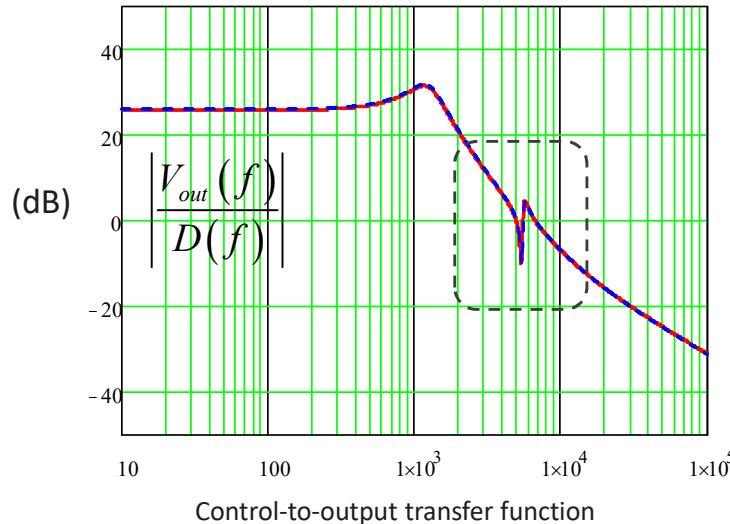
# The Filter Affects the Transfer Function


- Inserting a front-end filter can potentially bring instability to the converter
- ✓ Power stage response and output impedance can be altered by the *LC* network



- ✓ Magnitude distortion and severe output impedance peaking are observed


# Keep the Filter Output Impedance Low

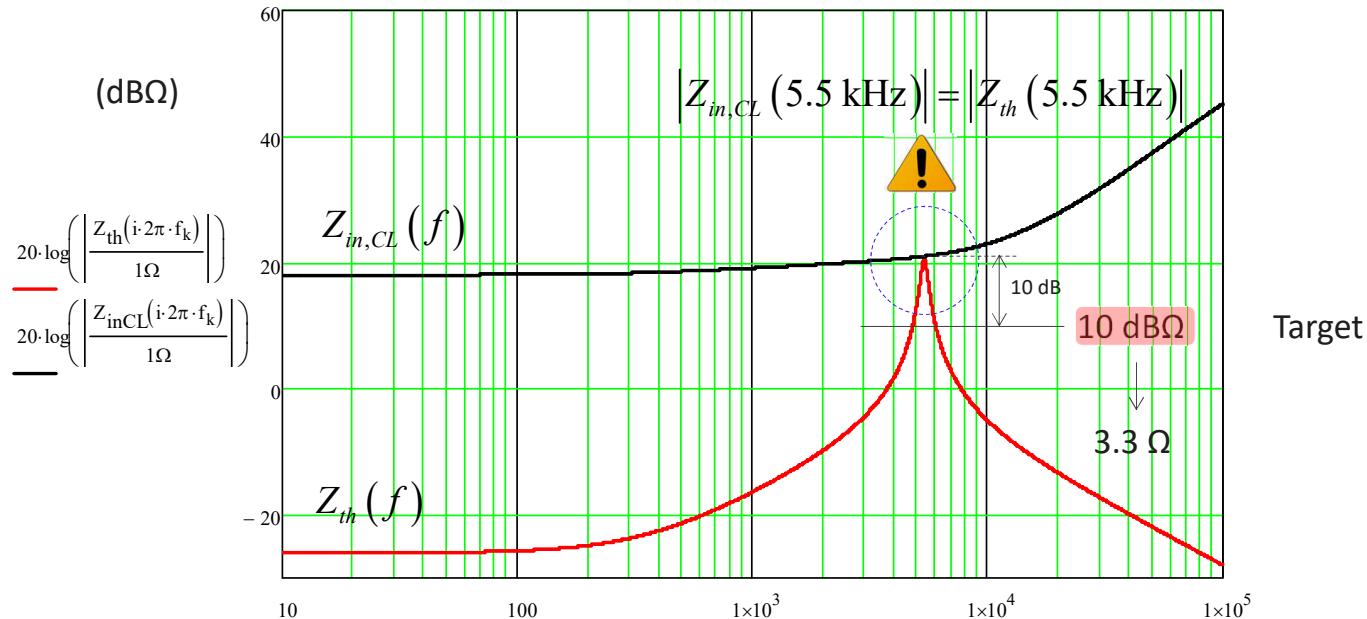1. Plot the input impedance of the compensated converter
  2. Add the output impedance of the EMI filter
- ✓ Any overlap represents a possible condition for instabilities


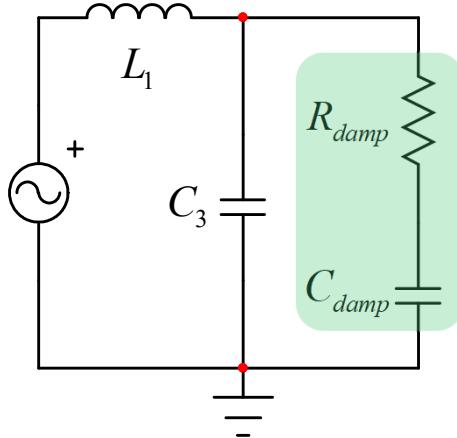
# Losses in the Filter Participate to Damping

- Damping consists of adding extra losses to dissipate power
- The series connection of a capacitor and a resistor offers a simple solution
- The resistor and the capacitor can be optimally determined



$$\begin{aligned}
 R_0 &= \sqrt{\frac{L_f}{C_f}} \\
 \frac{|Z_{out}|_{mm}}{R_0} &= \sqrt{\frac{2(2+n)}{n^2}} \\
 Q_{opt} &= \sqrt{\frac{(4+3n)(2+n)}{2n^2(4+n)}}
 \end{aligned}
 \quad \left. \right\}$$

$$n = \frac{R_0 \left( R_0 + \sqrt{R_0^2 + 4(|Z_{out}|_{mm})^2} \right)}{(|Z_{out}|_{mm})^2} = 3.5$$

target


$$\begin{aligned}
 R_{damp} &= R_0 Q_{opt} \\
 C_{damp} &= n C_f
 \end{aligned}$$



- An electrolytic capacitor with its ESR can do the job
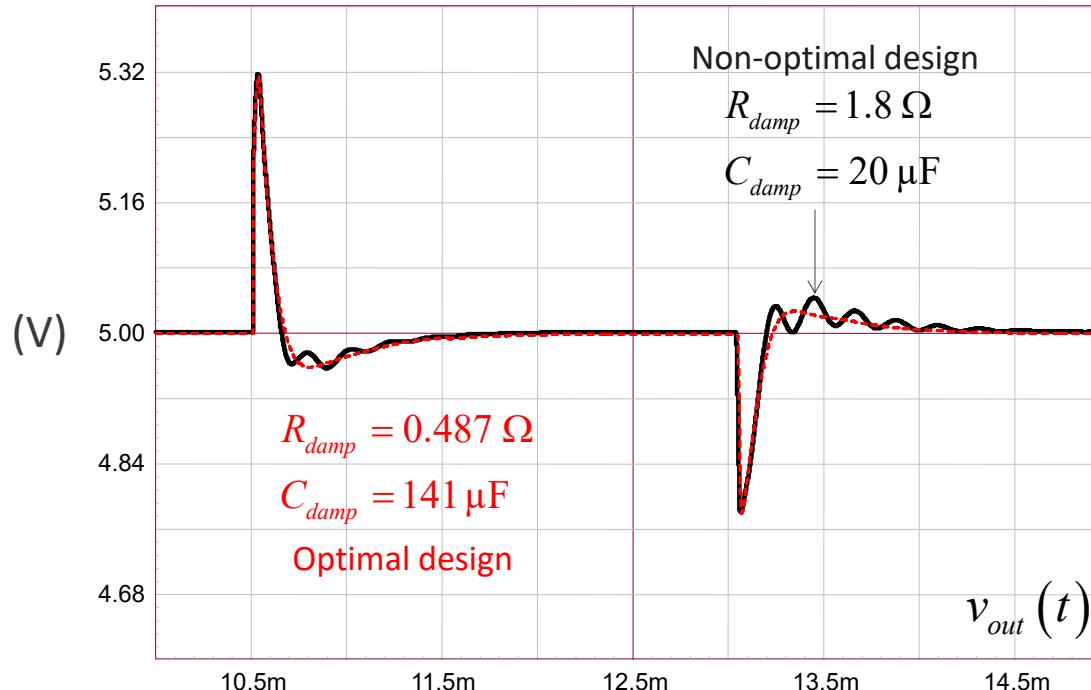
# Testing the Transient Response

- It is important to check the response to a load step once damping is done
- Two different damping combinations bring different responses in this case



- ✓ In one **case**, the filter has been studied together with the converter for an optimal combination
- ✓ In the second case, filter was damped after compensation strategy was designed

# Agenda


---

- Power Conversion Mechanisms
- Switching Cells and Control Schemes
- The Buck
- The Boost
- The Buck-Boost
- Introduction to Control Loop Design
- EMI Filter Interaction
- Introduction to Simulation
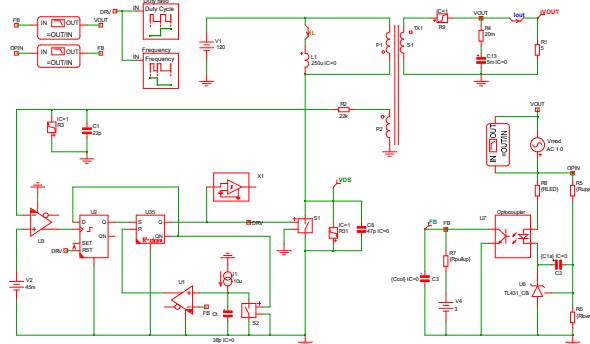
# Why Simulating Switching Power Converters?

- Check if the converter works on the computer before a prototype is built
  - ✓ Are operating voltages and currents within expected safe limits before power on?
  - Power libraries do not blow and let you explore many *What If?* scenarios
- Easily check impacts of parameters variations such as load, input voltage, ESRs etc.
- Work a compensation strategy easily with the ability to draw Bode plots
- ✓ Stabilize the converter with the simulator and confirms margins on the bench

→ Simulations do **NOT** replace experiments: always build a hardware prototype






Jim Williams - LT


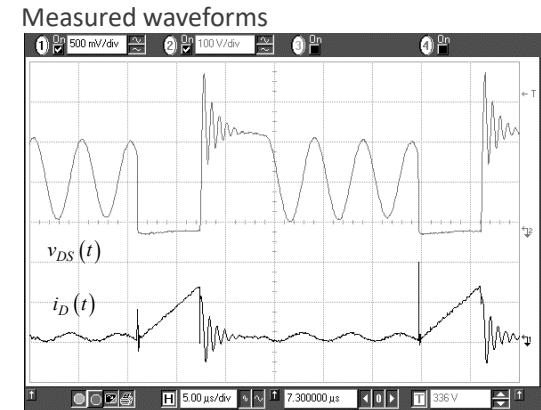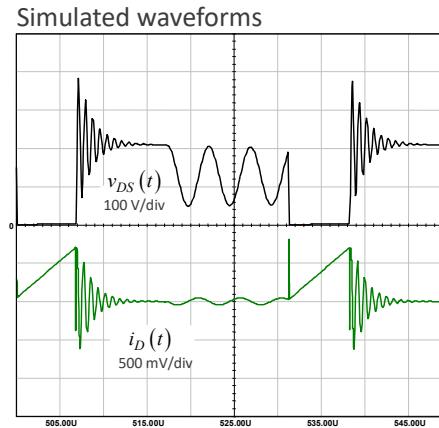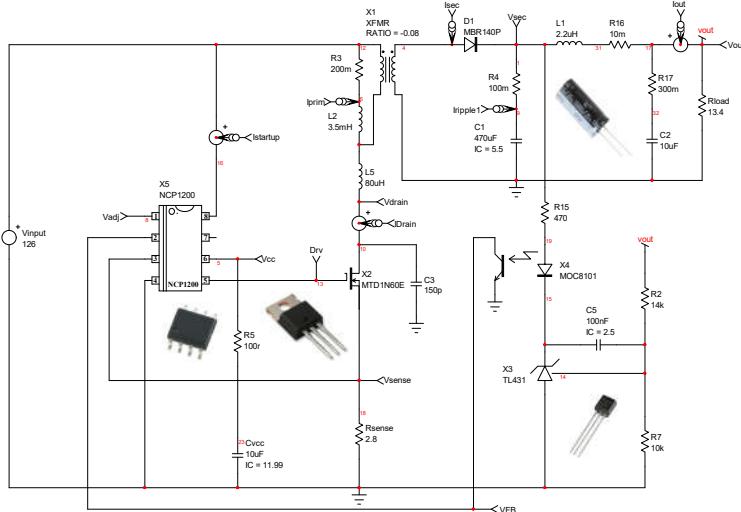
# Switching Models



- A cycle-by-cycle model represents the entire switching power converter
- ✓ Include parasitic terms and obtain excellent correlation with bench results
- ❖ Simulation time can be long and prone to convergence issues
- ❖ No access to ac response for loop stabilization




Simulation **really** works!
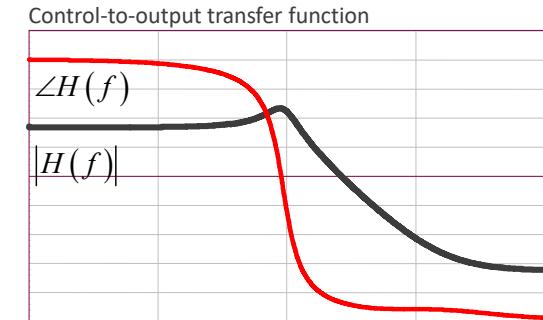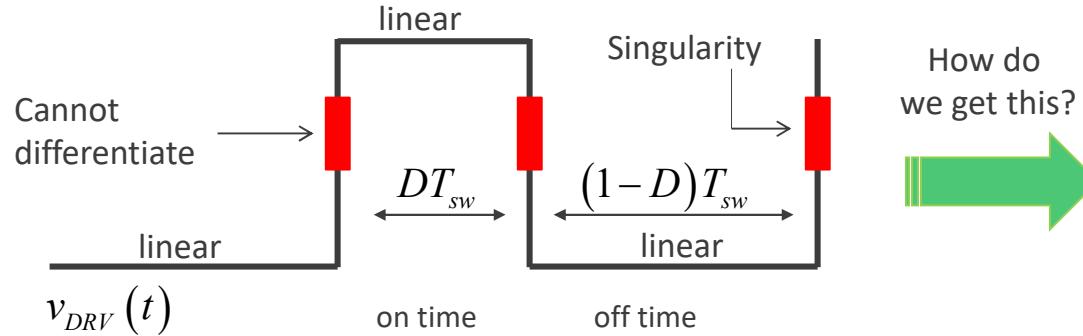
# Averaged Models

- Modeling the small-signal response of a switching converter is a difficult exercise
- The problem comes from time-discontinuous waveforms



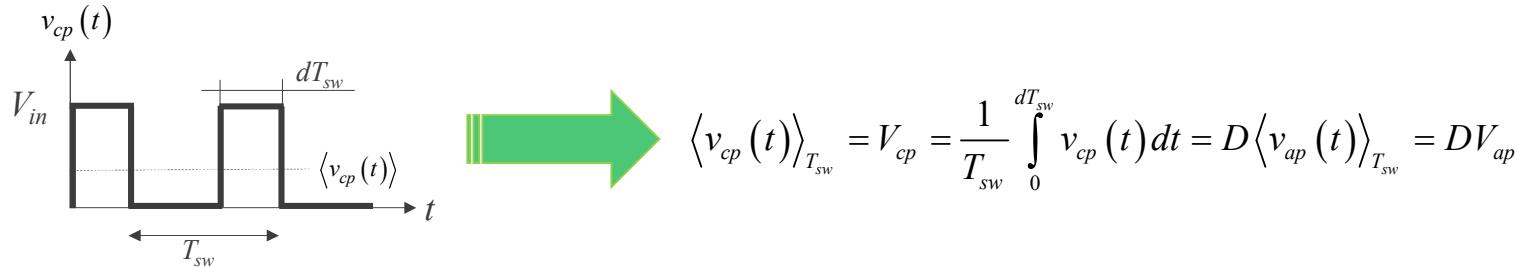- The PWM switch introduced in the 90's by Dr. Vorpérian offers an elegant solution
- ✓ Switching waveforms are *averaged* and described by a time-continuous expression



Small-signal


$$\hat{v}_{cp} = D\hat{v}_{ap} + V_{cp}\hat{d}$$

$$V_{cp} = DV_{ap}$$

Dc equation

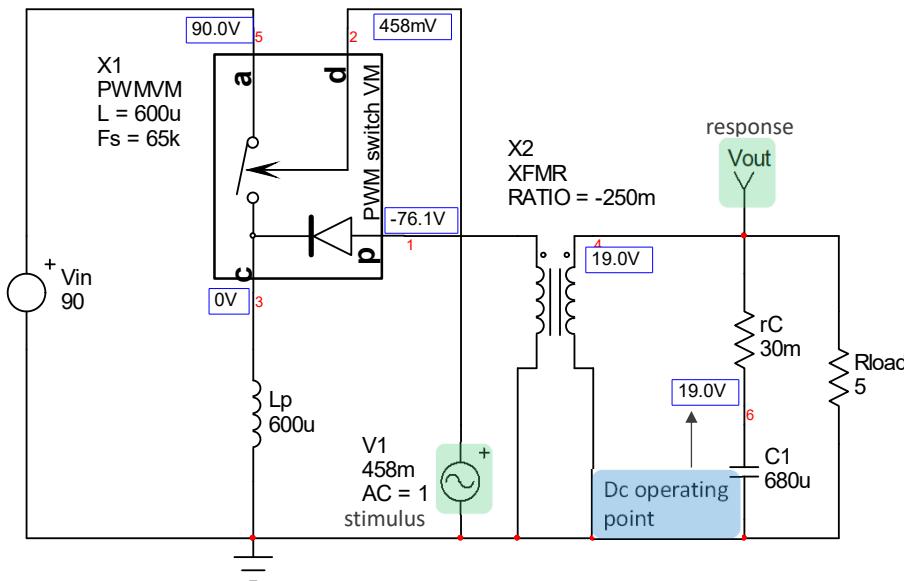
# Ac Analyses with Averaged Models

- Averaged models are free of switching component and simulate fast
- They work in transient and ac analyses: small-signal response is immediate
- ❖ There is no averaged model for the LLC converter


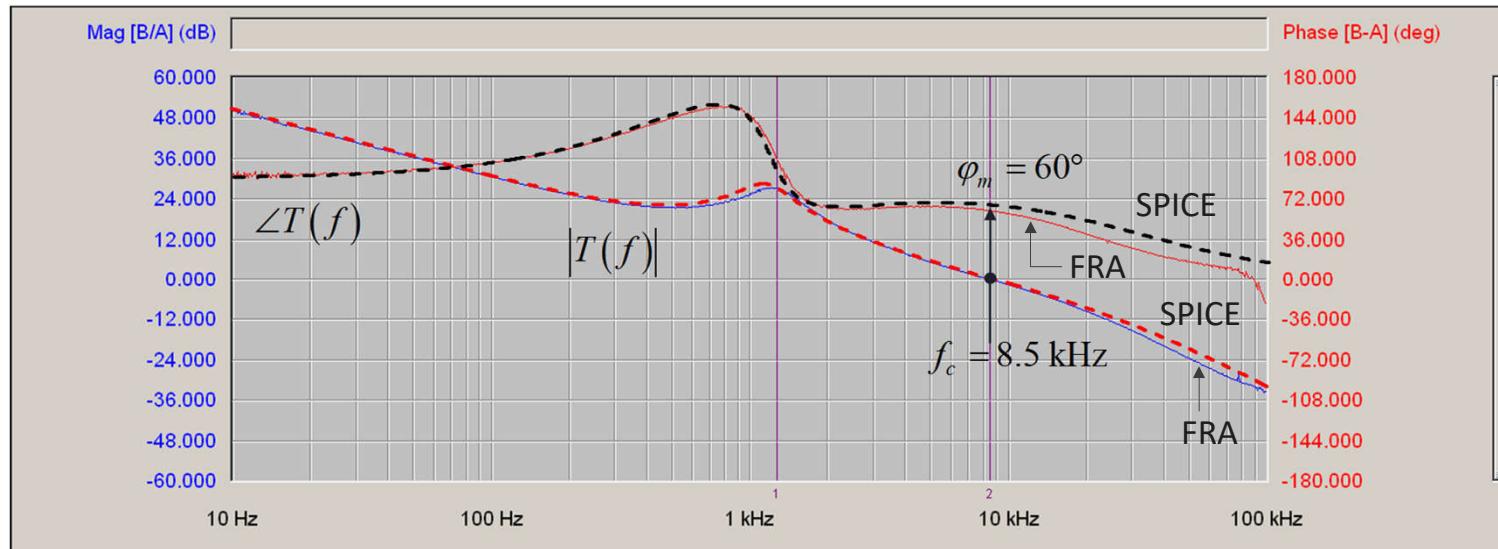
# Simulation Results you can Trust


- Simulation matches with hardware when parasitics are well extracted from components
- ✓ Run and test the compensation strategy and confirm bench measurements are ok




- When the computed model is validated you can run in-depth analyses with Monte Carlo
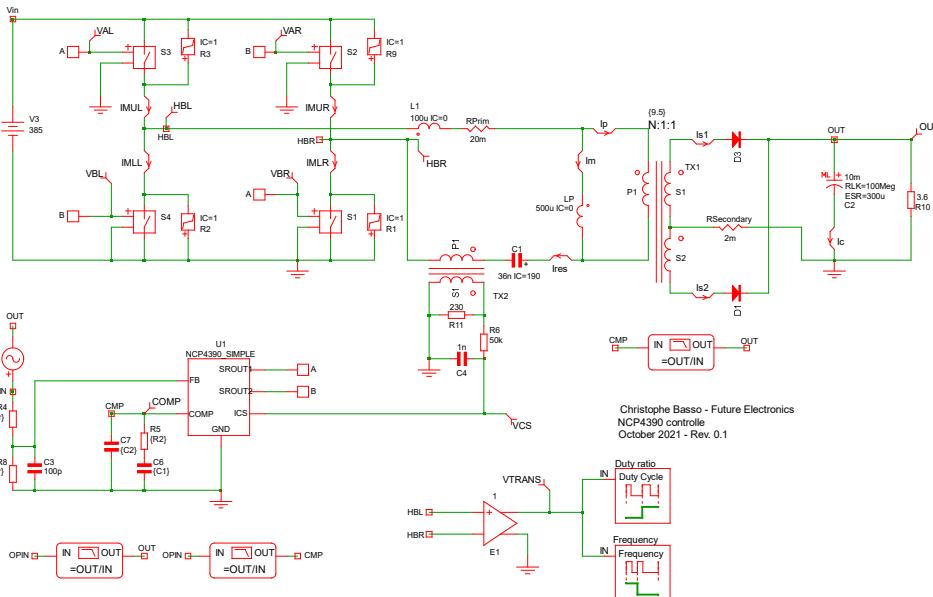
# Piece-Wise Linear Simulation Engine

- Piece-wise linear simulators can extract the ac response from a switching converter
- ✓ Build the circuit using classical switching components and run an ac analysis
- ✓ It works with any converter structure and there is no need for average model




A full-bridge LLC with NCP4390

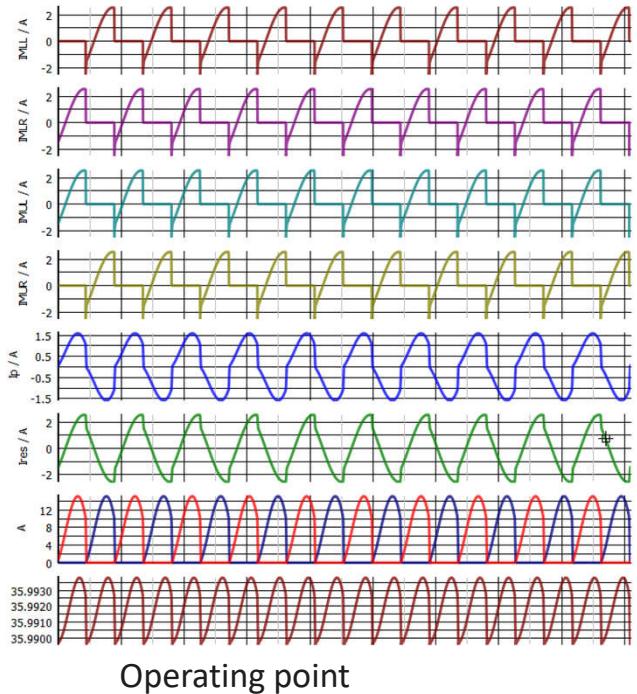
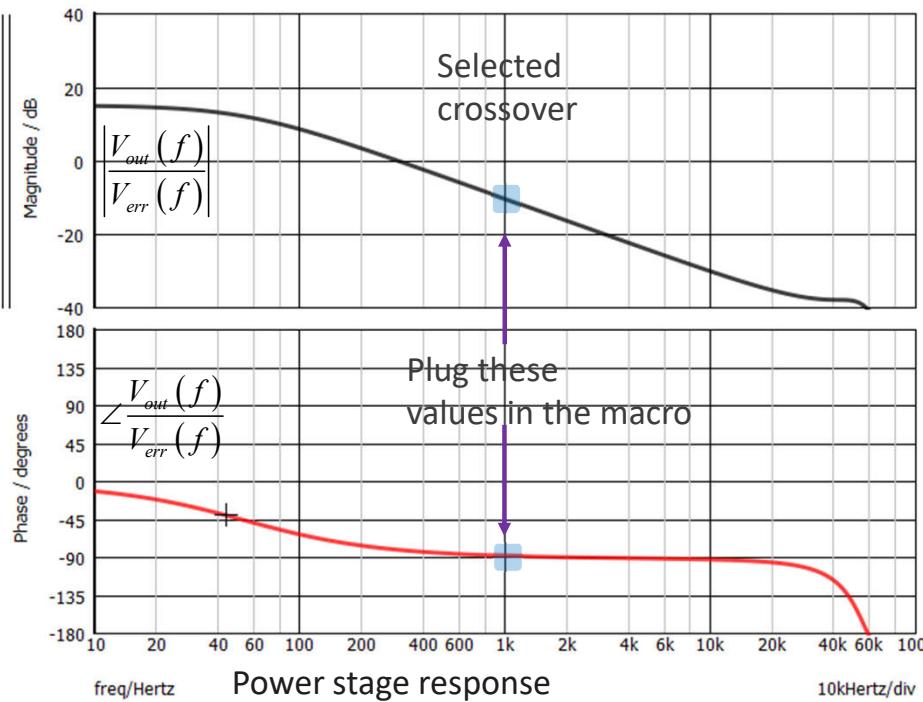
# Ac Analyses from a Switching Circuit

- The engine ac-sweeps the converter and delivers the control-to-output transfer function
- Determine the compensation strategy and automate components calculations



```



.Var Gfc=-10 * magnitude at crossover *
.Var PS=90 * phase lag at crossover *
*
* Enter Design Goals Information Here *
*
.Var fc=1k * targeted crossover *
.Var PM=70 * choose phase margin at crossover *
*
* Enter the Values for Vout and Bridge Bias Current *
*
.Var Vout=36
.Var Ibias=1m
.Var Vref=2.4
.Var Rlower={Vref/Ibias}
.Var Rupper={(Vout-Vref)/Ibias}
*
* Choose OTA characteristics *
*
.Var gm=300u * transconductance in Siemens *
*
.Var R2=(a/b)*(fp*G)*(Rlower+Rupper)/((fp-fz)*Rlower*gm)
.Var C1=1/(2*pi*R2*fz)
.Var C2=(Rlower*gm/(2*pi*fp*G*(Rlower+Rupper)))/(b/a)
*
* Do not edit the below lines *
.Var boost=PM-PS-90
.Var G=10^(-Gfc/20)
.Var k=tan((boost/2+45)*pi/180)
.Var fp=fc*k
.Var fz=fc/k
.Var a=sqrt((fc^2/fp^2)+1)
.Var b=sqrt((fz^2/fc^2)+1)
*
* Simpler approach if C2 << C1 *
*
*.Var R2=G*(Rlower+Rupper)/(Rlower*gm)
*.Var C1=1/(2*pi*R2*fz)
*.Var C2=1/(2*pi*R2*fp)
*

```

Components calculations are automated

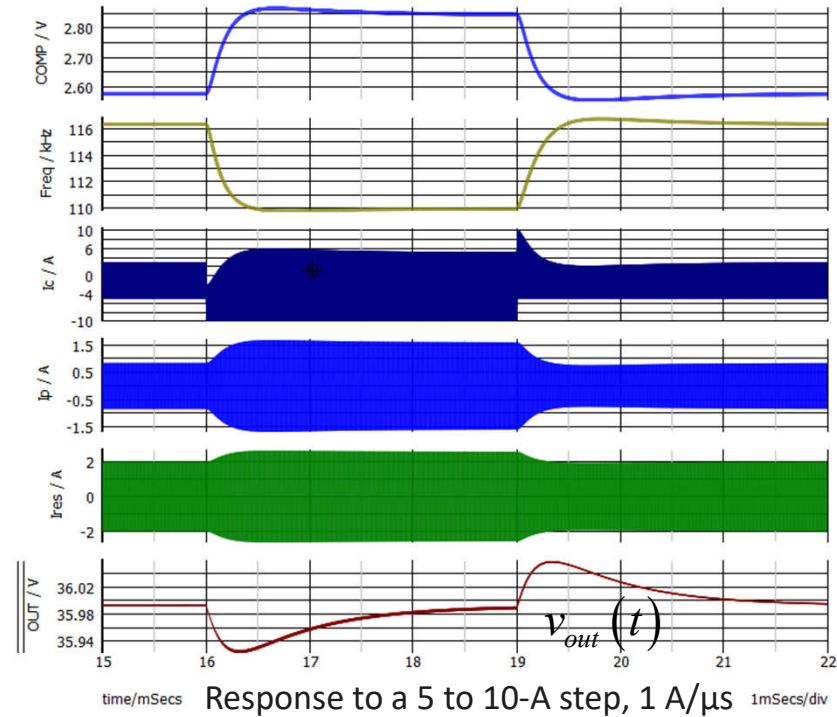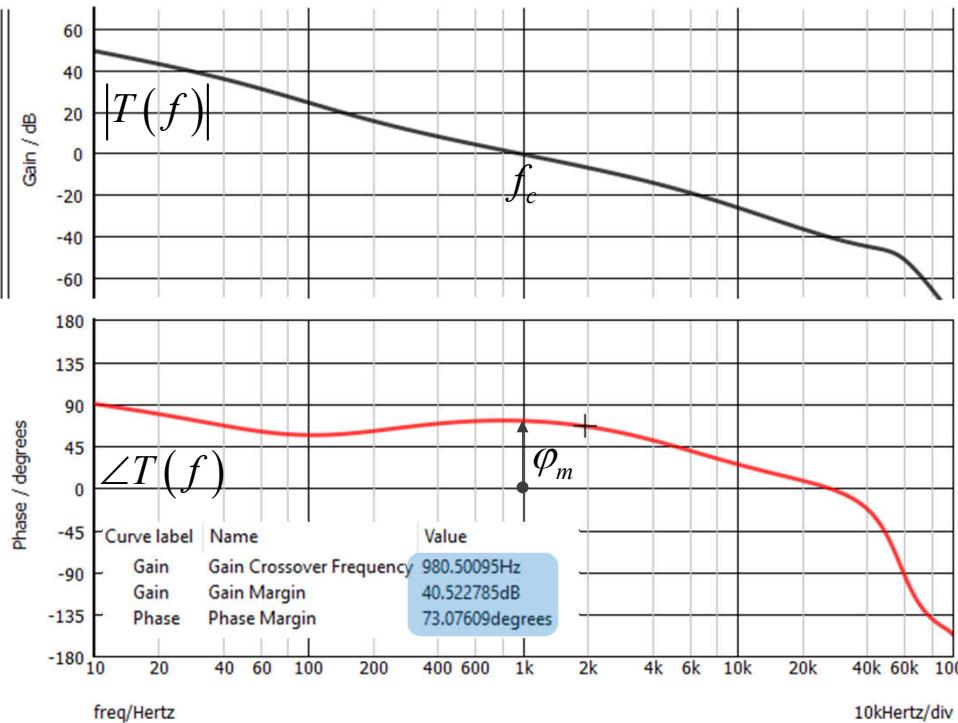
# Check Compensated Response

- The compensated loop gain is immediate and you can check the transient response
- Run various analyses for robustness verifications once model is validated by hardware



# Books on Power Electronics


---

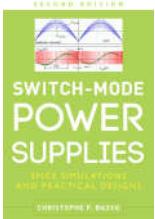

[Switch-Mode Power Supplies: SPICE](#)  
[Simulations and Practical Designs](#), 2<sup>nd</sup> edition  
 Christophe Basso – McGraw-Hill 2014



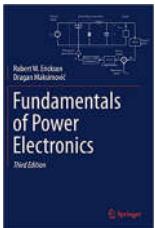[Transfer Functions of Switching Converters](#)  
 Christophe Basso – [Faraday Press 2021](#)



[Fundamentals of Power Electronics](#), 3<sup>rd</sup> edition  
 Robert Erickson, Dragan Maksimovic –  
 Springer 2020



Answering Your Questions About Power Design

[Design Guide](#) [Newsletter](#) [Special Sections](#) [Resources](#) [About Us](#) [Sponsors](#) [Home](#)

[How2Power](#), a free power electronics newsletter



[Designing Control Loops for Linear and](#)  
[Switching Power Supplies](#)  
 Christophe Basso – Artech House 2012

My personal webpage with all my APEC seminars and  
 lot of power electronics documents to download  
<https://cbasso.pagesperso-orange.fr/Spice.htm>

All the former Unitrode (now TI) seminars  
 are available from this [landing page](#)



# Conclusion

- ❑ Compared to linear regulators, switching converters excel in efficiency
  - ❖ Switching converters are noisy in essence
- ❑ There are 3 basic switching cells made of a controlled switch and a diode
  - ✓ Some of these cells can be extended to versions featuring isolation
  - ✓ Different input/output characteristics are observed and must be understood
  - ❖ Input/output currents can be smooth or pulsating and impact capacitors
- ❑ Loop control is an essential part of the design and cannot be neglected
- ❑ EMI filter are necessary to keep noise within accepted limits
  - ❖ Their insertion can severely affect the converter performance
- ❑ Simulation offers a great way to test the converter on the computer
  - ❖ Use it extensively while always using engineering judgment on the results